

Duration: 03 HoursTotal Marks assigned to paper: 80 Marks


Instruction to candidate:-

1. Question 1 is compulsory.
2. Attempt any three from remaining five questions.
3. All questions carry equal marks.
4. Assume suitable data wherever necessary.

Q1. Attempt all [20 Marks]

Q1.a Determine the common mode output voltage for an OpAmp circuit with CMRR= 65db,  $A_d = 10$  and  $V_{cm} = 5 \text{ mV}$ 

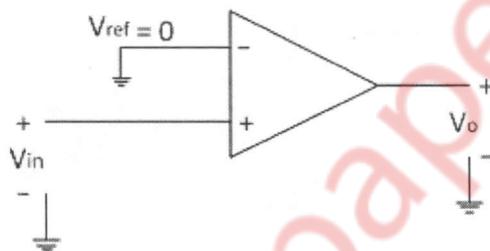
Q1.b Explain operation of following comparator circuit. Consider input as sine wave of 10 V.




Q1.c Explain centre tapped full wave rectifier.

Q1.d With an example explain operation of transistor as a switch.

Q1.e Explain crossover distortion in class B power amplifier. How it is overcome.

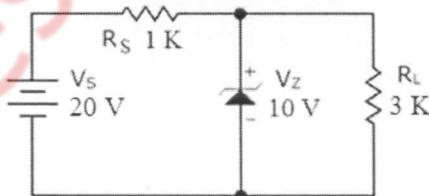Q2.a For the Zener diode network, determine  $V_L$ ,  $V_R$ ,  $I_Z$ , and  $P_Z$ . [8 Marks]

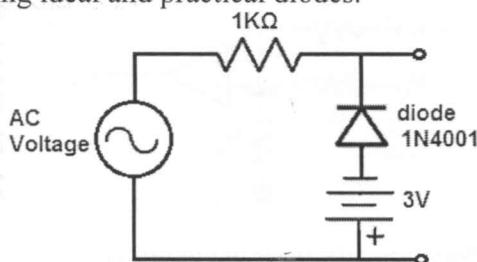Q2.b Determine output voltage. Assume, input to be sine wave of 5 V peak. Draw waveform considering ideal and practical diodes. [8 Marks]




Q2.c Compare BJT and FET. [4 Marks]


- Q3.a Determine operating point and  $V_{DS}$  for an FET self biasing circuit with  $V_{DD} = 12$  V,  $R_D = 2.2$  K,  $R_S = 1.6$  K,  $R_G = 1$  M,  $I_{DSS} = 6$  mA and  $V_P = -6$  V [8 Marks]
- Q3.b BJT transistor with voltage divider bias circuit has following values,  $V_{CC} = 20$  V,  $R_1 = 68$  K,  $R_2 = 10$  K,  $R_C = 6.2$  K,  $R_E = 1.1$  K,  $\beta = 50$ . Determine operating point and  $V_{BC}$ . [8 Marks]
- Q3.c Explain working of D-MOSFET [4 Marks]
- Q4.a Explain working of Schmitt trigger. [8 Marks]
- Q4.b Explain Weinbridge oscillator. [8 Marks]
- Q4.c Give typical values for OpAmp IC 741. [4 Marks]
  1. Open loop gain
  2. Input impedance
  3. Slew rate
  4. Offset voltage
- Q5.a Derive the expression of stability factor for emitter stabilized biasing circuit. [8 Marks]
- Q5.b Draw and explain series voltage regulator. [8 Marks]
- Q5.c Compare class A, class B and class C power amplifier based on, [4 Marks]
  - a) Output waveform for collector current
  - b) Linearity
  - c) Distortion
  - d) Efficiency
- Q6.a Derive the expression for output and hence determine the output voltage. Consider,  $R_1 = R_2 = R_f = R_g = 10$  K and  $V_1 = V_2 = 2$  V. [5 Marks]
- 
- Q6.b Explain weighted summation amplifier using OpAmp. [5 Marks]

- Q6.c** Identify the circuit diagram. Derive the expression for output voltage. Consider,  $R_2 = 30\text{ K}$ ,  $V_{IN} = 100\text{ mV}$ ,  $V_O = 3.1\text{ V}$ . What value of input resistance is needed in the given circuit to produce the given output voltage?

[5 Marks]

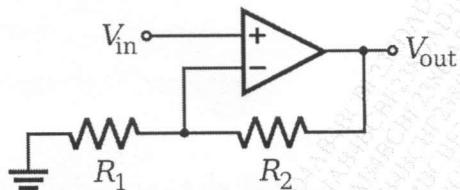

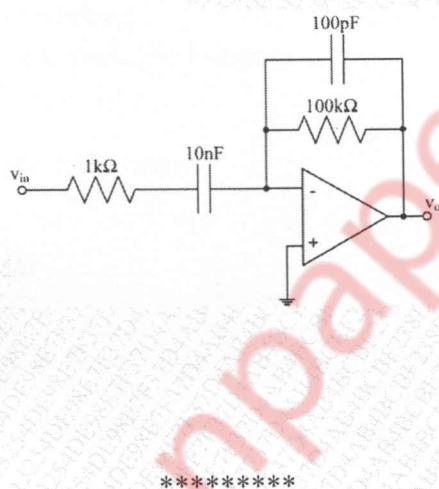- Q6.d** Identify the circuit diagram. Derive the expression for output voltage. [5 Marks]



\*\*\*\*\*