

INST

SE/III / INST / CBGS] electri N/W Analysis & Synthesis

05-06-15

Q.P. Code : 4856




(3 Hours)

[Total Marks : 80]


- N.B: (1) Question No. 1 is compulsory
(2) Attempt any three from the remaining.

1. (a) Find I_x

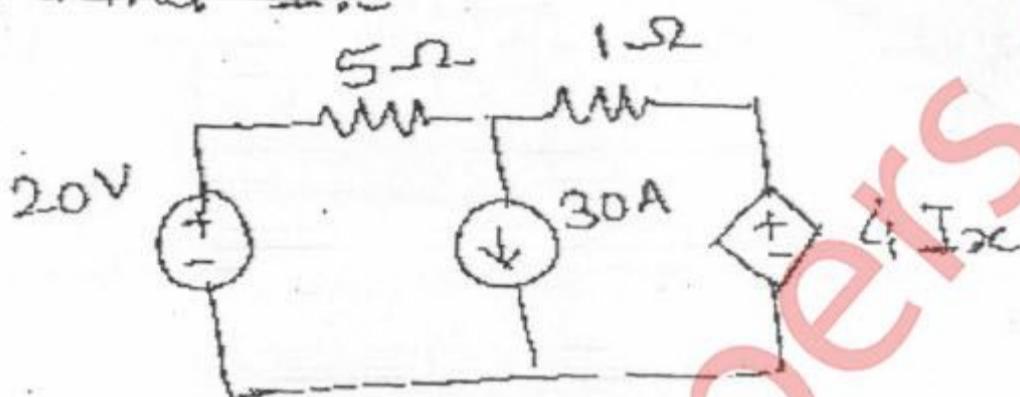


20

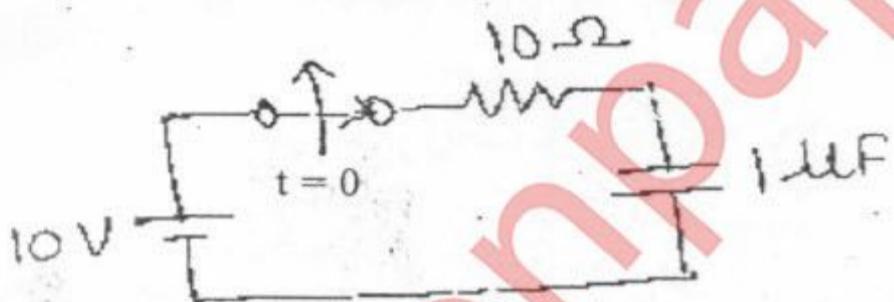(b) Find $i(O^-)$, $i(O^+)$ for the network shown below.




(c) Find Z_{21} for the network

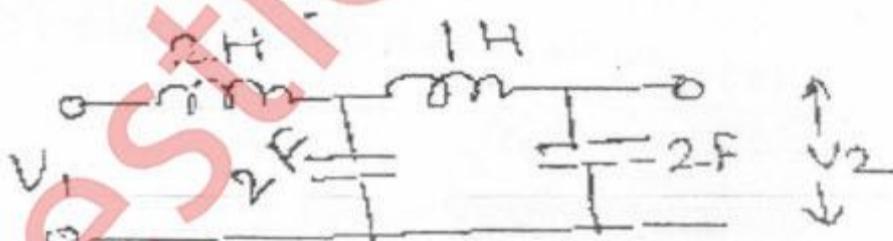


(d) Check the positive realness of the following functions.

- (1) $F(s) = s^2 + 2s + 4$
(2) $F(s) = s^2 + 2s / (s^2 + 1)$

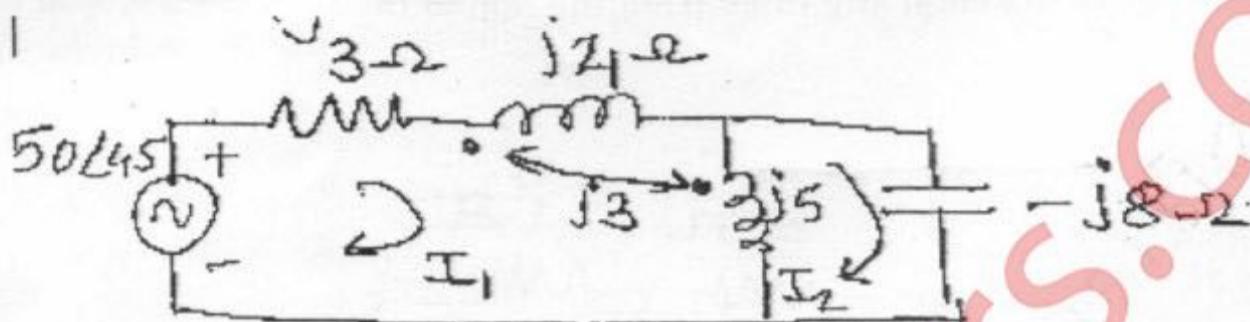2. (a) Find current I_2 using mesh analysis.




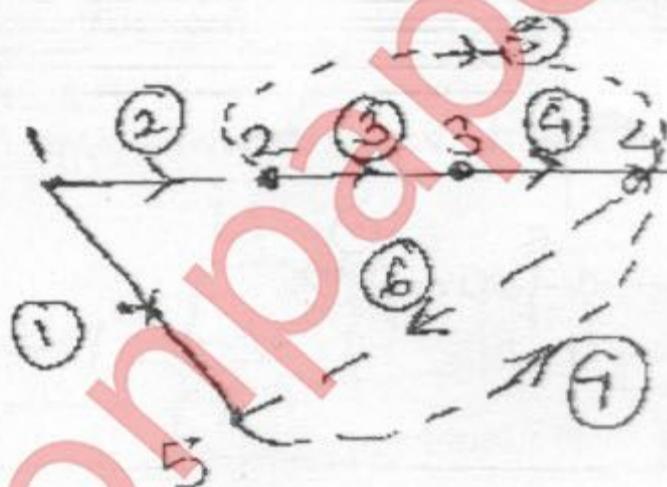- (b) For the graph shown, write incidence matrix, tieset matrix and f-cutset matrix. 10




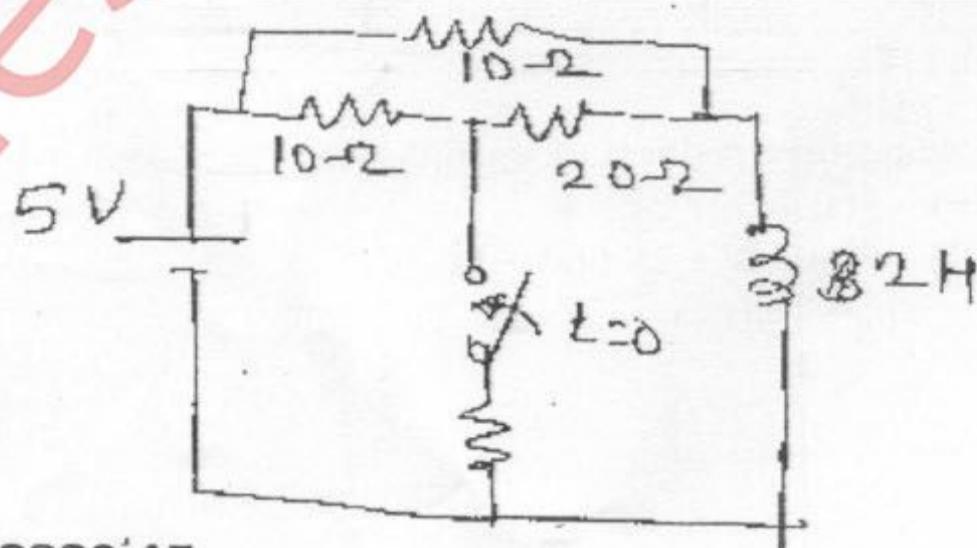3. (a) In the n/w shown, steady state is reached with s/w open. At $t=0$, the s/w is closed. For the element values given, det the vaoues of. 10

$V_a(O^-)$, $V_b(O^-)$ &
 $V_a(O^+)$, $V_b(O^+)$




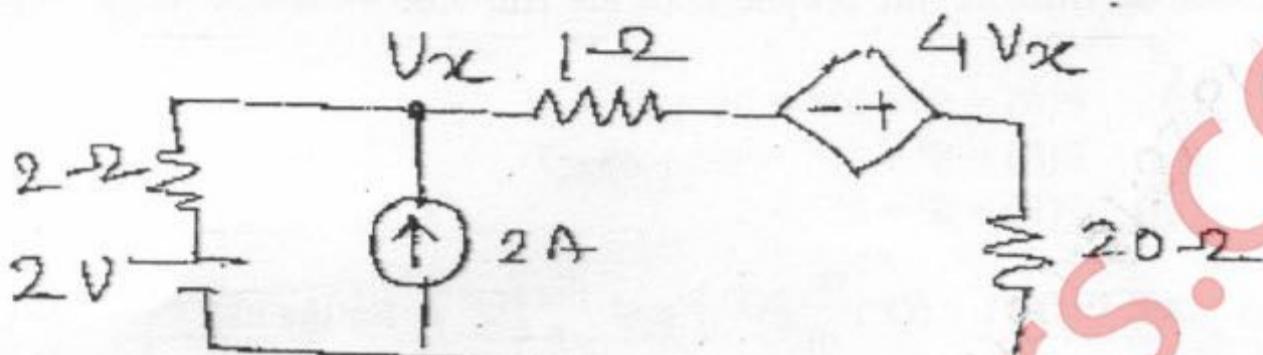- (b) Find current in 20Ω branch using thevenin's theorem.



4. (a)


10

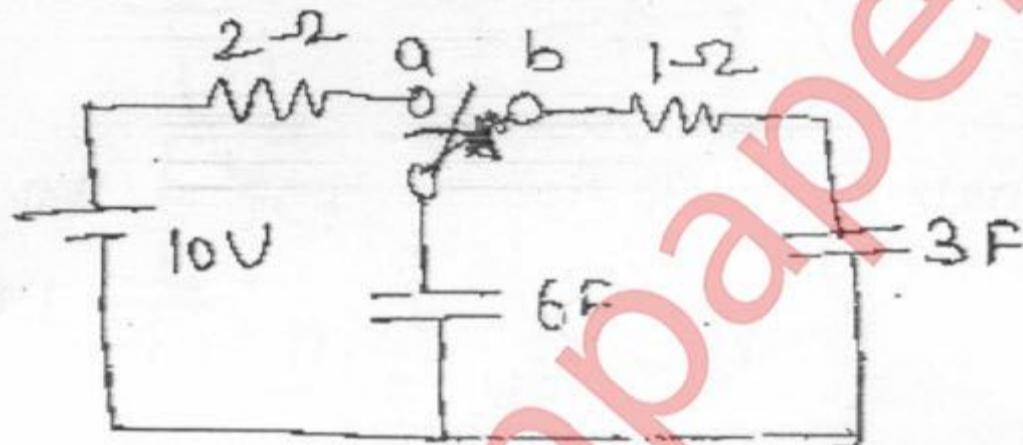

For the shown ckt; s/w is moved from a to b det.
 $i(t)$ and $V_c(t)$

- (b) Obtain z parameters for the network shown.

10

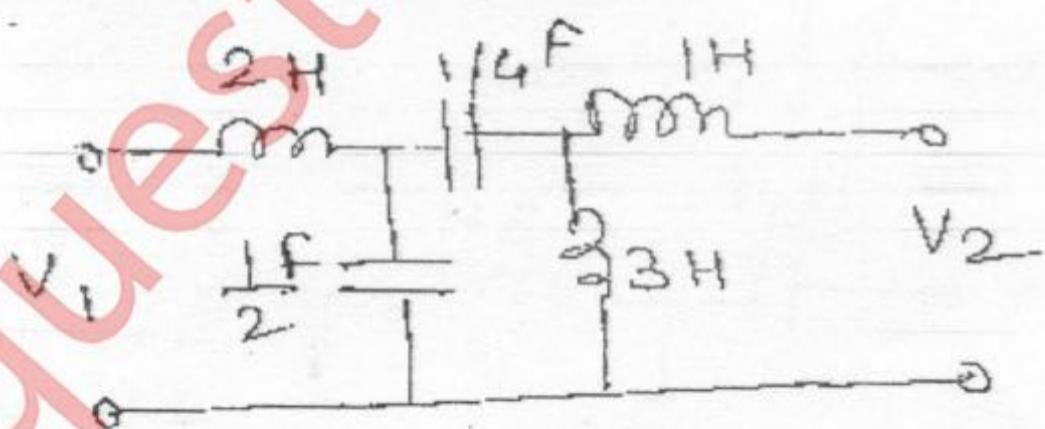


5. (a) State and explain properties of Hurwitz polynomial.
 (b) State whether the polynomials are Hurwitz.

5

- (i) $P(S) = S^3 + 2S^2 + 4S + 2$
 (ii) $P(S) = S^4 + 3S^3 + 4S^2 + 2S + 3$
 (iii) $P(S) = S^5 + 2S^3 + 3$
- (c) Det. $V_c(O^+)$, $i_1(O^+) \frac{di_1}{dt}(O^+)$ and $\frac{di_2}{dt}(O^+)$ for the ckt.

10

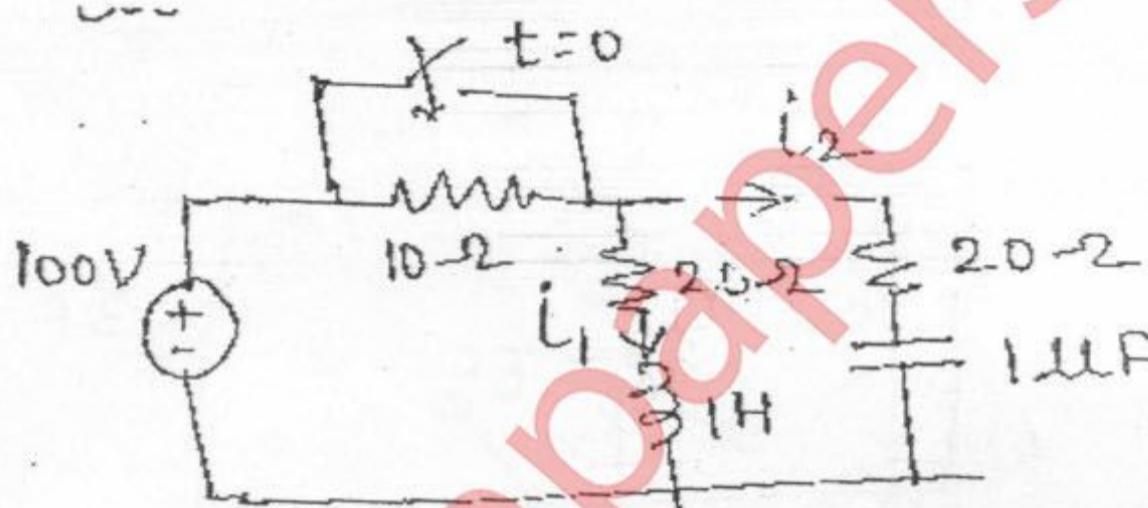


6. (a) Synthesize the following function in Foster I and Foster II.

10

$$Z(s) = \frac{6s^4 + 42s^2 + 48}{s^5 + 18s^3 + 48s}$$

- (b) Cal for the $\frac{V_2}{V_1}, \frac{I_2}{I_1}, \frac{V_1}{I_1}, \frac{V_2}{I_1}$ for the

10

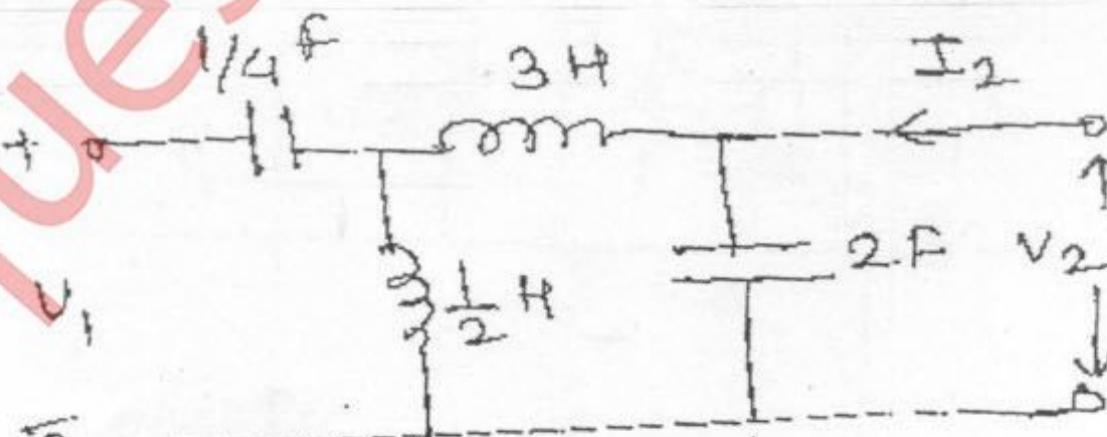

Course: S.E. (SEM. III) (CBSGS) (INSTRUMENTATION
ENGG.)(prog- 740 TO 754)

Q.P Code: 4856

Correction:

In Q.1 (a) find I_x : I_x is current through 5 ohms resistance flowing towards the node

In Q. 3 (a) resistance value is 10 ohms and Inductor value is 2 H ; point a and point b are on two sides of 20 ohms branch (point a above the switch and point b above the inductor)

Query Update time: 05/06/2015 04:27 PM