

CMOS VLSI D.  
(CMOS VLSI Design)

Q.P.Code: 37945

Time: 3 Hours

Max Marks: 80

- N.B. 1) Question No.1 is compulsory  
2) Solve any three questions from the remaining questions.  
3) Assume suitable data if necessary.

- 1 Solve any four of the following.
- (a) Explain behavior of  $g_m$  as function of below parameters 5
    - i. Overdrive voltage with W/L constant.
    - ii. Overdrive voltage with  $I_D$  constant.
  - (b) What are different second order effects in NMOS? 5
  - (c) Explain the concept of switched capacitor circuit 5
  - (d) Compare performance of various op-amp topologies 5
  - (e) Explain active current mirror circuit 5
- 2 (a) For  $W/L=50/0.5$  and  $I_D=0.5mA$ , calculate the transconductance and output impedance of both NMOS and PMOS device. Also find the intrinsic gain. 10
- (b) What is a bandgap reference? Describe methods of implementation of band gap references. 10
- 3 (a) For common source stage with diode connected load, if the variation of  $r_o = g_{mb}/g_m$  with the output voltage is neglected. Prove that the gain is independent of bias current and voltages. 10
- (b) Derive equation of differential gain, common mode gain and CMRR of differential amplifier. 10
- 4 (a) Explain the concept of clock feed through in charge pump. Charge injection, charge sharing in charge pump. 10
- (b) Derive expression for voltage gain  $A_V$  and output resistance  $R_o$  of source follower stage. 10
- 5 Design two stage operational amplifiers that meet the following specifications 20  
with a phase margin of 60. Assume the channel length is to be  $1\mu m$ ,  
 $K_N=100\mu A/V^2$ ,  $K_P=20\mu A/V^2$ ,  $V_{TN}=|V_{TP}|=0.5V$ ,  $\lambda_N=0.06V^{-1}$ , and  $\lambda_P=0.08V^{-1}$   
 $A_V>5000v/v$ ,  $V_{dd}=2.5V$ ,  $V_{ss}=-2.5V$ ,  $GB=5MHz$ ,  $CL=10pf$ ,  
 $SR>10v/\mu sec$ ,  $V_{out} range = \pm 2V$ ,  $ICMR = -1$  to  $2V$ ,  $P_{diss} \leq 2mw$ .
- 6 Write short note on any four 5
- (a) Types of Noise of CS stage 5
  - (b) Cascode current mirror circuit. 5
  - (c) Advantage and disadvantages of DLL 5
  - (d) Comparison of full custom design and semi custom design 5
  - (e) Performance parameters of VCO 5