

Basic Electrical Engineering



Q.P. Code :803301

(3 Hours)

[ Total Marks : 80

- N.B. :** (1) Question No.1 is compulsory.  
 (2) Answer any **THREE** questions from remaining five questions.  
 (3) **Figures** to right indicate **full** marks.  
 (4) Assume suitable data if required.


1. A) State Maximum Power Transfer Theorem 2
- B) Derive the formula to convert a delta circuit into an equivalent star 4
- C) Define Average value and RMS value of an alternating quantity 4
- D) Prove that power in a 3-phase delta connected system is 3 times that of a star connected system. 4
- E) Explain the working principle of a single phase transformer. 4
- F) What is the use of commutator in a DC machine. 2

2. A) Obtain current through  $1\ \Omega$  resistance by using Super position theorem, in fig 2.A. 10




- B) A coil is connected across a non-inductive resistance of  $120\ \Omega$ . When a  $240\ \text{V}$ ,  $50\ \text{Hz}$  supply is applied to this circuit the coil draws a current  $5\ \text{A}$  and total current is  $6\ \text{A}$ . Determine the power and power factor of
  - i) the coil
  - ii) the whole circuit10

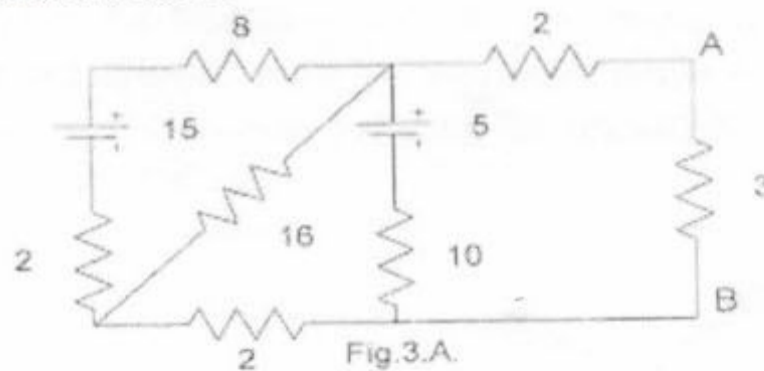3. A) Obtain Norton's equivalent circuit of the network shown in fig. 3.A, across the terminals A and B 10




[ TURN OVER ]

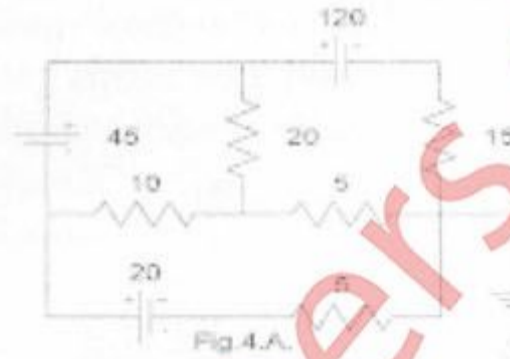- B) A series RLC circuit, if  $\omega_0$  is the resonant frequency,  $\omega_1$  and  $\omega_2$  are the half power frequencies, prove that  $\omega_0 = \sqrt{\omega_1 \omega_2}$  5
- C) Derive the equivalent circuit of a 1-phase transformer. 5
4. A) Obtain current through  $15 \Omega$  resistance by nodal analysis in fig.4.A. Take reference node as marked. 10



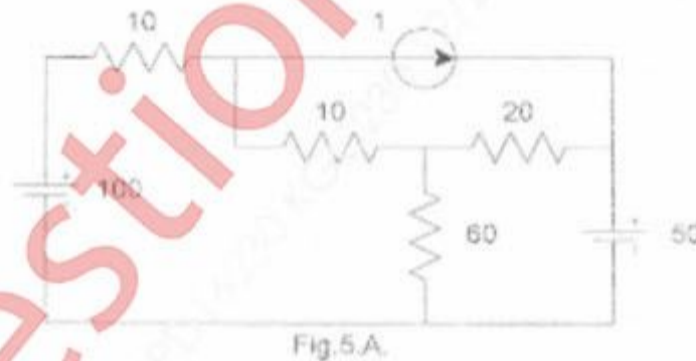- B) In a balanced 3 phase, star connected system, a wattmeter is connected with its current coil in series with Y line and pressure coil between Y and R lines. Draw a neat circuit diagram showing the above wattmeter connection. Assuming a lagging power factor, draw the corresponding phasor diagram and derive the wattmeter reading in terms of line voltage, line current and phase angle. 10
5. A) Obtain current through  $60 \Omega$  resistance by Mesh analysis in fig.5.A. 6



- B) Develop the phasor diagram of a single transformer supplying to a resistive load. 8
- C) Derive the emf equation of a DC generator. 6
6. A) A resistor and a pure reactance are connected in series across a 150 V ac supply. When the frequency is 40 Hz, the circuit draws 5 A. When the frequency is increased to 50 Hz, the circuit draws 6 A. Find the value of resistance and the element value of the reactance. Also find the power drawn in the second case. 10

B) A single phase 10 KVA, 500 V/250 V, 50 Hz transformer has the following 10 constants.

Resistance : primary = 0.2 ohms, secondary = 0.5 ohms

Reactance : primary = 0.4 ohms, secondary = 0.1 ohms

Resistance of equivalent exciting circuit w.r.t. primary = 1500 ohms

Reactance of equivalent exciting circuit w.r.t. primary = 750 ohms

What will be the reading of the instruments placed in primary side when the transformer is connected for OC and SC tests ?

-----