

Con. 5918-13

GX-10011

(Revised Course)


(3 Hours)

[Total Marks : 80

- N.B. :** (1) Question No. 1 are compulsory.
 (2) Solve any **three** questions out of the remaining five questions.
 (3) Assume data if required , clearly stating the assumptions.

1. (a) Using source transformation find I.

3

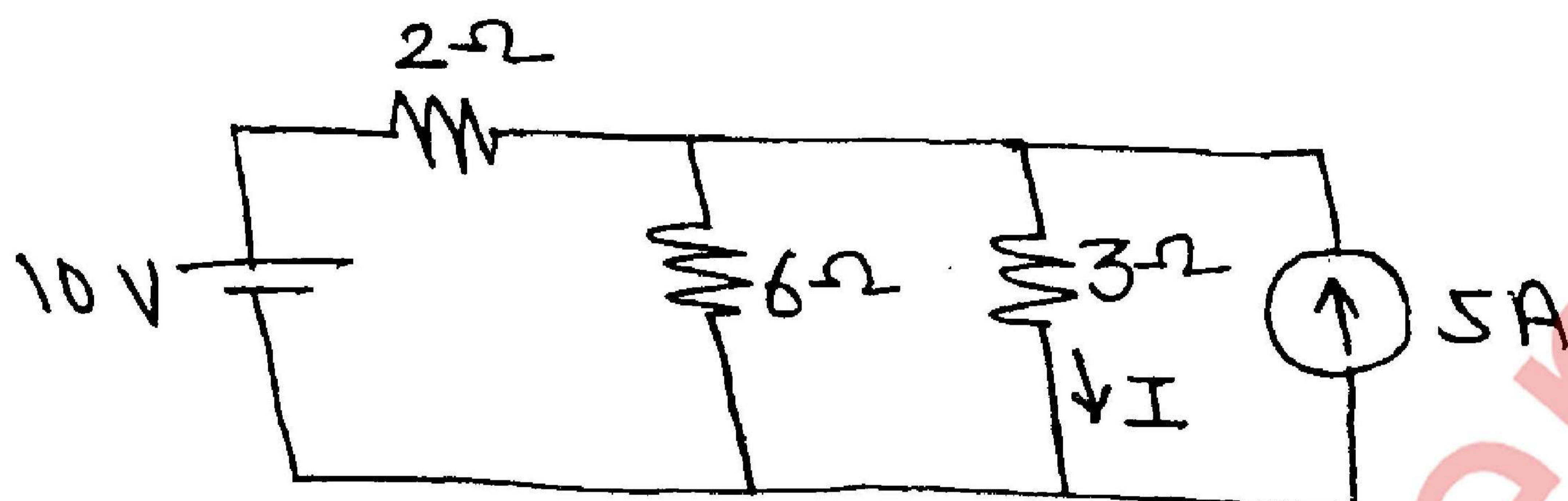

(b) State and Explain Norton's theorem.

3

(c) Derive an expression for the average value of a sinusoidally varying current in terms of Peak Value.

3

(d) Derive the condition for resonance in a series circuit.

3

(e) Give relation between line current and phase current, line voltage and phase voltage in balanced star and delta connected load.

2

(f) What are assumptions for an ideal transformer ?


4

(g) Draw and explain circuit diagram for half wave rectifier.

2

2. (a) Find the currents I_1, I_2, I_3 in the given circuit by node voltage method.

6

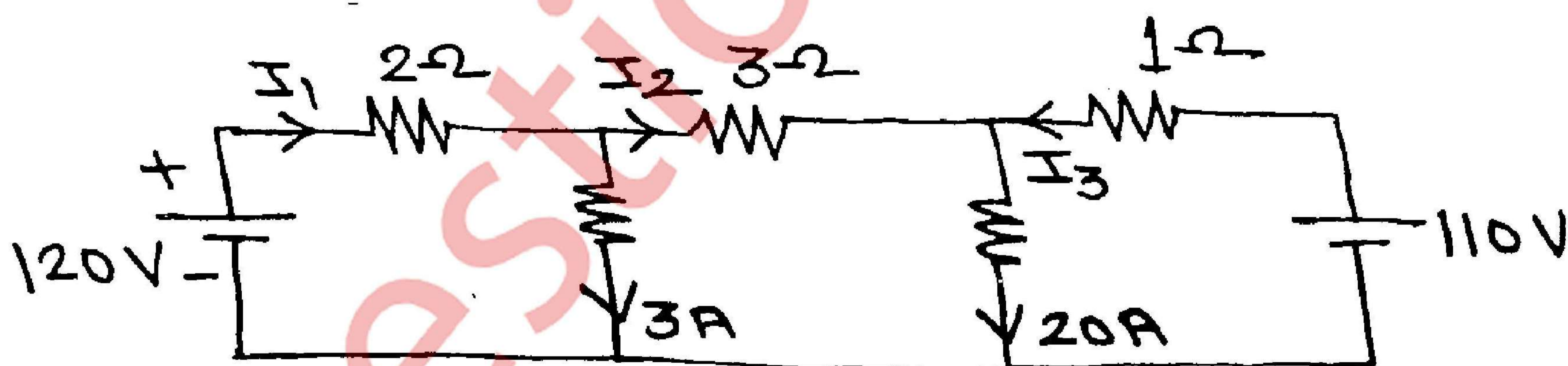


(b) For the circuit shown determine the

8


(i) Supply frequency (f).

(ii) Coil resistance (r)


(iii) Supply voltage (v)

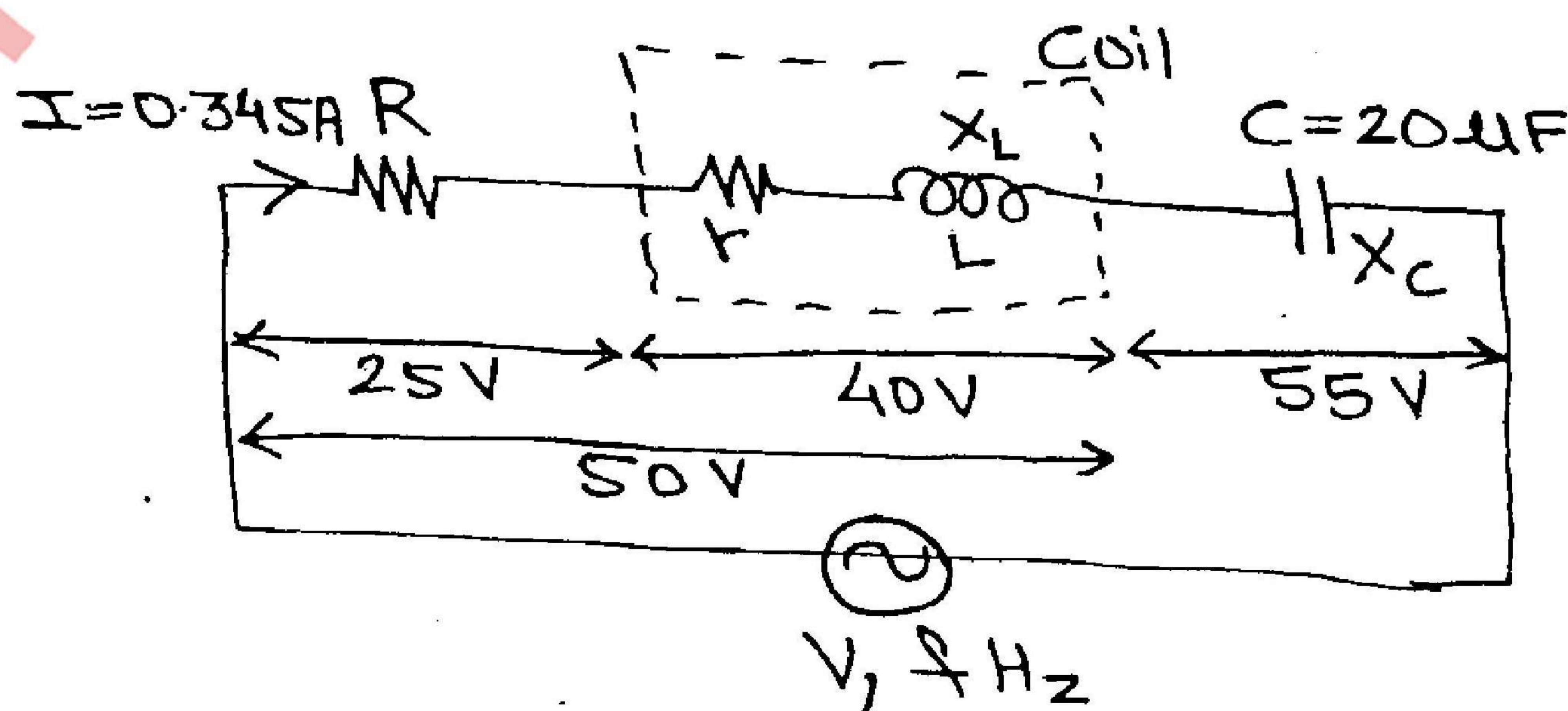

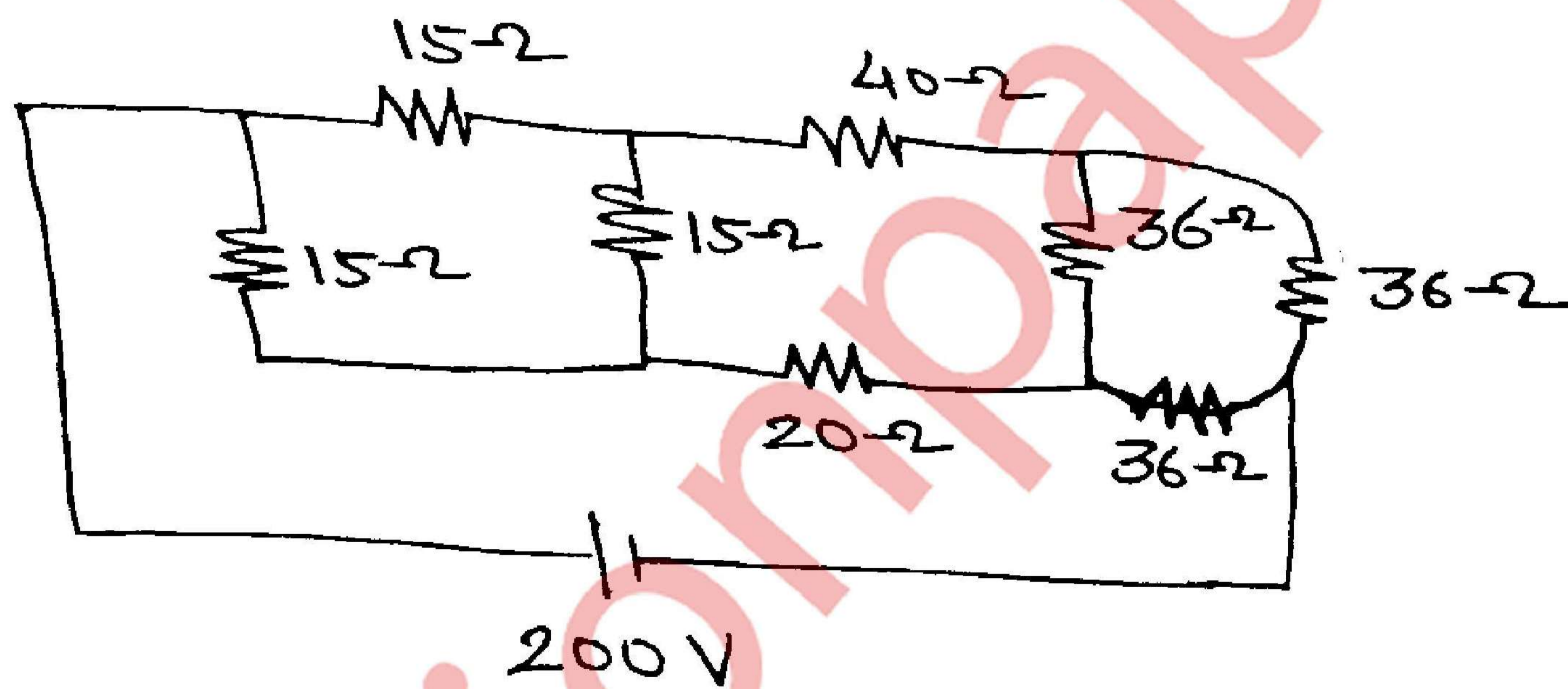
- (c) Draw and explain Phasor diagram of 1-Phase practical transformer when 6
- (i) on no load
- (ii) Leading power factor load.
3. (a) Find the values of circuit elements and reactive voltampere drawn for a balanced 3 phase load connected in delta and draws a power of 12kW at 440V. The power factor is 0.7 leading. 8
- (b) The following results were obtained on a 40 KVA, 2400/120 V transformer. 6
 O. C. test : 120V, 9.65A and 396 W (on L.V. side)
 S. C. test : 92V, 20.8A and 810 W (on H.V. side)
 Calculate the parameters of approximate equivalent circuit referred to H. V. side.
- (c) Explain series inductor filter. 2
- (d) Explain circuit diagram and working of CE configuration of BJT. 4
4. (a) Determine current through 20Ω resistor in the following circuit. 7



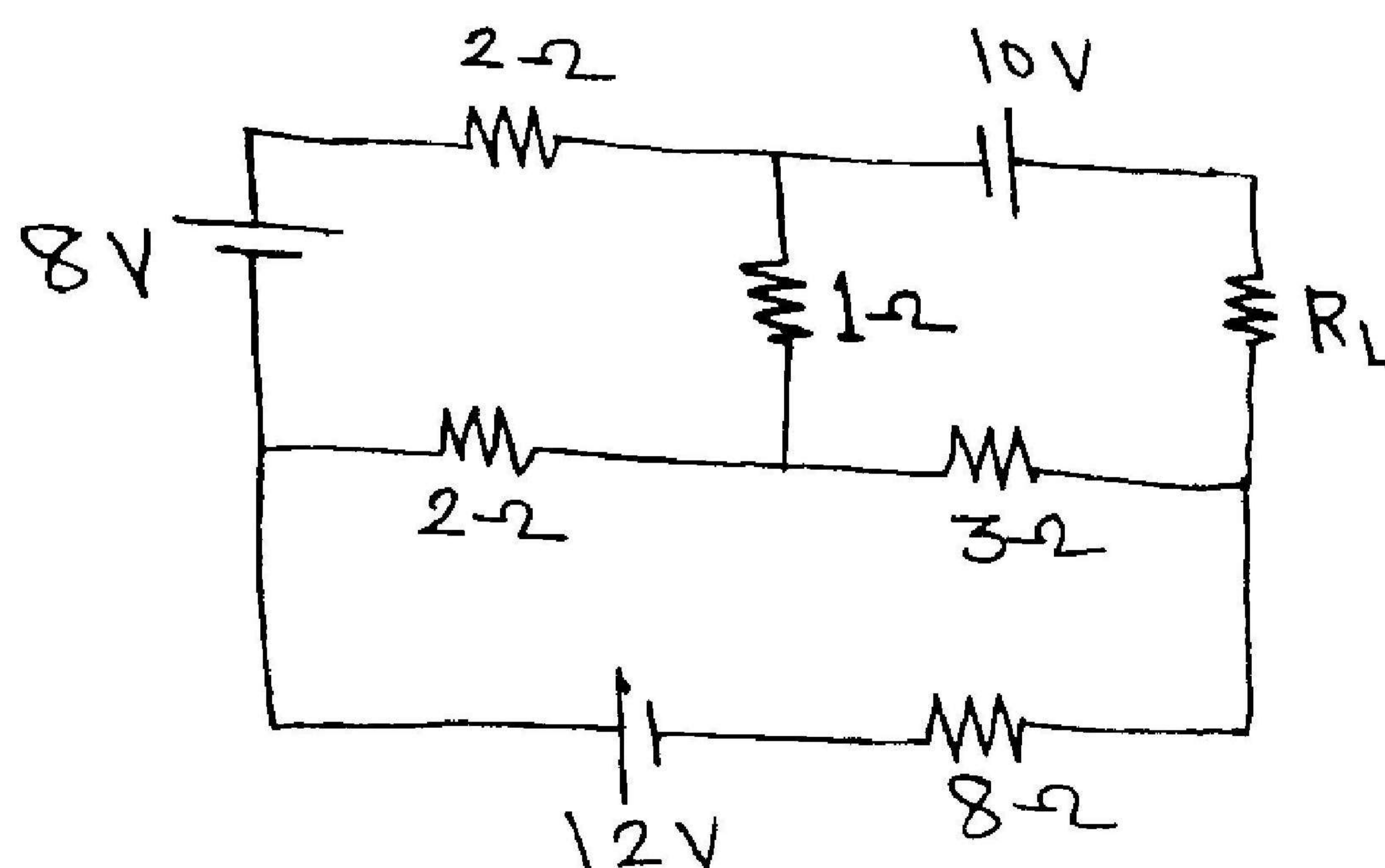- (b) Two currents are represented by $I_1 = 15\sin\left(\omega t + \frac{\pi}{3}\right)$ and $I_2 = 25\sin\left(\omega t + \frac{\pi}{4}\right)$. These currents are fed into common conductor. Find the total current. If the conductor has resistance 50Ω , what will be energy loss in 10 hours. 5
- (c) In a three phase power measurement by two wattmeter method, both the wattmeters read the same value. What is the power factor of the load? Justify your answer. 4
- (d) Explain the circuit diagram and waveforms of Bridge rectifier. 4
5. (a) For the given circuit find the value of ' R_L ' so the maximum power dissipated in it. Also find P_{max} . 8



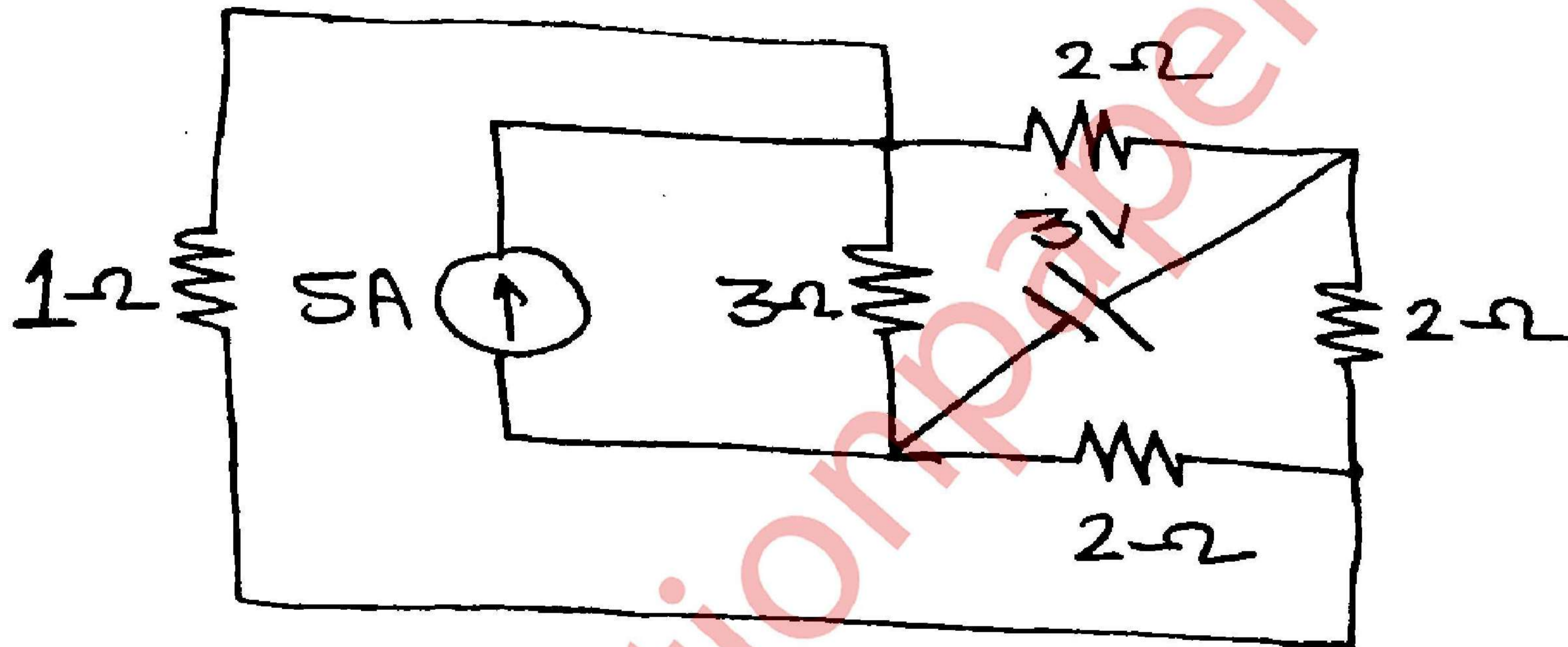- (b) With proper phase diagrams, explain behaviour of a pure capacitor in an AC circuit. 4
 - (c) Derive condition for maximum efficiency of a transformer. Also derive equation for load at maximum efficiency. 8
6. (a) Determine current in 1Ω resistor using superposition theorem. 7



- (b) An inductive coil of resistance 10Ω and inductance $0.1H$ is connected in parallel with $150\mu F$ capacitor to a variable frequency, $200V$ supply. Find the resonance frequency at which the total current taken from supply is in Phase with supply voltage. Also find value of this current. Draw the phasor diagram. 7
- (c) Two wattmeters are connected to measure power in a three phase circuit. The reading of one of the wattmeter is 7 kW when load power factor is unity. If the power factor of the load is changed to 0.707 lagging without changing the total input power, calculate the readings of the two wattmeters. 6