

TOTAL MARKS: 80


TIME: 3hrs

NB

- 1) Question No. 1 is compulsory.
- 2) Answer any three questions out of remaining five questions.
- 3) Assumption made should be clearly stated.
- 4) Answer to questions should be grouped together and written together.


- Q1 a. Find current through $2\ \Omega$ resistor using star delta transformation

3

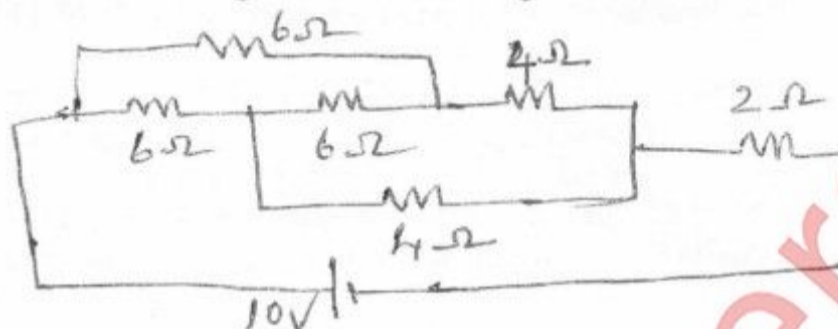

- b. Find Thevenin's equivalent circuit across AB


3

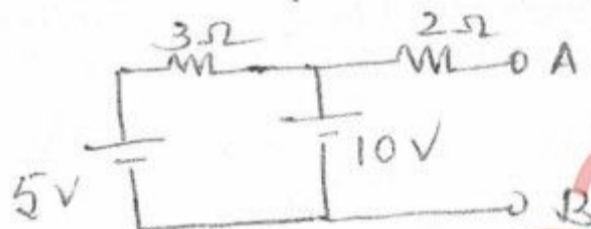

- c. An alternating voltage is represented by $v = 141.4 \sin 377t$, find frequency, time period and time at which voltage is 100 V for the first time
- d. Prove that for a pure capacitor average power drawn over one complete cycle is zero
- e. Draw a three phase delta connected load connected across a three phase supply, mark phase voltage, phase current, line voltage and line current
- f. Derive the induced emf equation of a single phase transformer.
- g. Draw the input and output voltage waveform of a half wave rectifier.


- Q2 a. Using Mesh analysis find current through $2\ \Omega$ resistor.

6

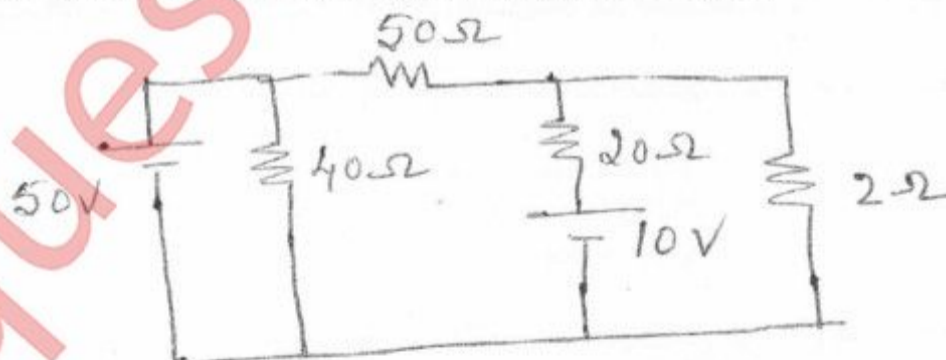

[TURN OVER

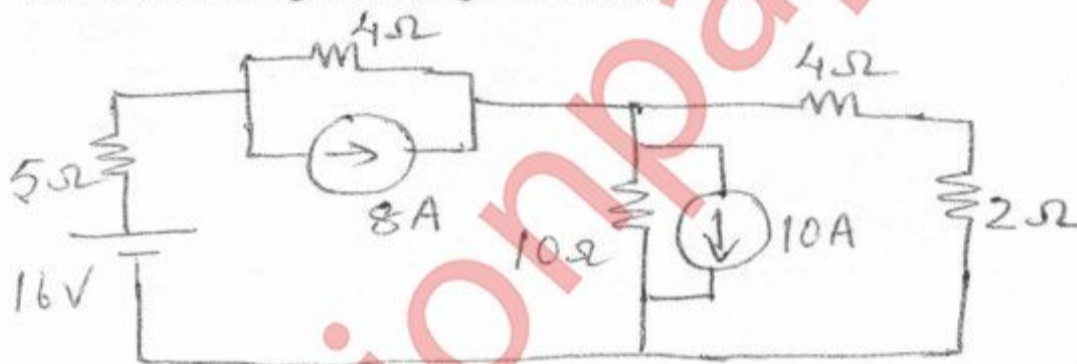
- b. A choke coil of $10\ \Omega$ resistance and $0.1\ \text{H}$ inductance is connected in series with a capacitor of $200\ \mu\text{F}$ across $230\ \text{V}$, $50\ \text{Hz}$ supply. Calculate circuit impedance, current, power factor, power dissipated in the coil and voltage across coil. 8
- c. Draw phasor diagram of a single phase transformer connected to a resistive load. 6
- Q3 a. Three identical impedance are connected in star to a three phase supply of $400\ \text{V}$. The line current is $30\ \text{A}$ and the total power taken from the supply is $14\ \text{kW}$. Calculate resistance and reactance value of each impedance. 8
- b. Open circuit and short circuit test on a $5\ \text{kVA}$, $200/400\ \text{V}$, $50\ \text{Hz}$ single phase transformer gave the following test results.
Open circuit test(L.V side): $200\ \text{V}$, $1\ \text{A}$, $100\ \text{W}$
Short circuit test(with primary short circuited): $15\ \text{V}$, $10\ \text{A}$, $85\ \text{W}$
Find the equivalent circuit parameters and draw it referred to primary side. 6
- c. Illustrate with the output characteristics, the active region, saturation region and cut off region of a CE transistor configuration. 4
- d. Compare the performance of capacitor filter with inductor filter 2
- Q4 a. Find current through $2\ \Omega$ using source transformation. 7




- b. Two wattmeter are connected to measure power in a three phase circuit. The reading of one wattmeter is $7\ \text{kW}$ when the load power factor is unity. If the power factor of the load is changed to 0.707 lagging without changing the total input power, calculate the reading of two wattmeters 4
- c. Find the expression for the sum of three voltages in instantaneous form where 5
- $$V_1 = 6 \sin(\omega t + 35^\circ)$$
- $$V_2 = 5 \sin(\omega t - 150^\circ)$$
- $$V_3 = 6 \cos(\omega t + 40^\circ)$$
- d. With neat circuit diagram explain the working of a full wave bridge rectifier. Draw output voltage and current waveform 4

[TURN OVER

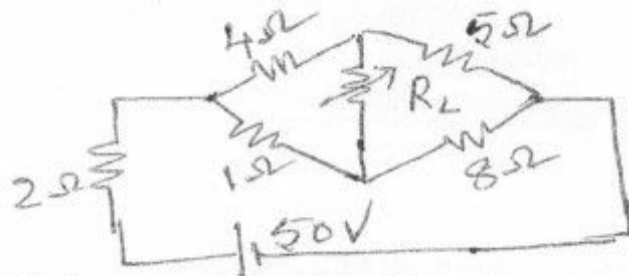- Q5 a. Find the value of R_L for which maximum power get dissipated and also calculate the maximum power 8




- b. Find currents through each branch 4

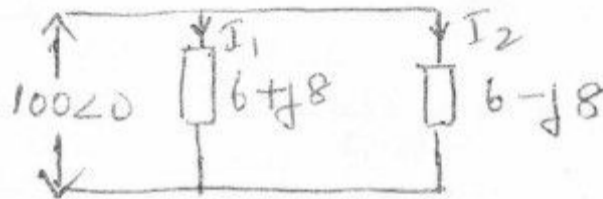

- c. Develop complete equivalent circuit of a single phase transformer 8

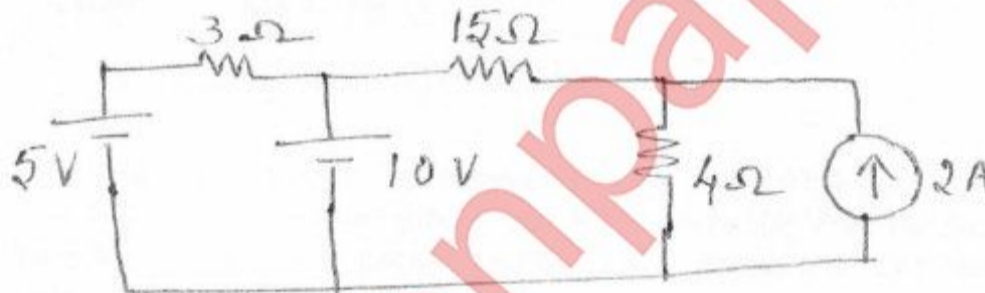- Q6 a. Find current through 15 Ω resistor using superposition theorem. 7



- b. An R-L-C series circuit with a resistance of 10 Ω, inductance of 0.2 H and a capacitance of 40 μF is supplied with a 100 V supply at variable frequency. Find the following with respect to series resonance circuit. 7
1. The frequency at which resonance takes place
 2. Current at resonance
 3. Power and power factor
 4. Q-factor
- c. Derive power and power factor in a balanced three phase star connected circuit under two watt meters measurement in terms of wattmeter reading. Draw relevant connections and phasor diagram. 6