


[3 Hours]

[Total Marks: 80]


- N.B. :** 1. Question 1 is compulsory.  
2. Solve any three from remaining.  
3. Assume suitable data if required and justify it.

**Q.1) Solve** [20]

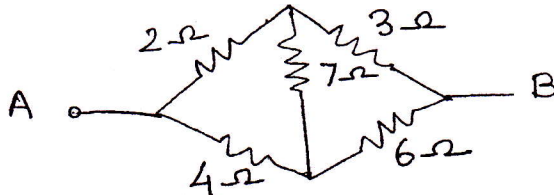
a. Find  $R_{ab}$  using star-delta transformation [3]



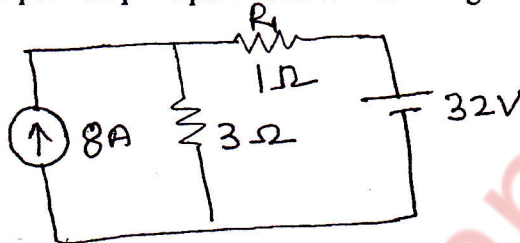b. Use superposition principle to find current through  $R_1$  [3]




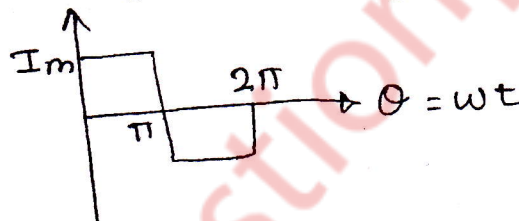- c. An alternating current of frequency 50Hz has a maximum value of 100 A. [3]  
Calculate its value 1/600 seconds after the instant the current is zero & its value decreasing afterwards
- d. Find the average & rms value of the given waveform [3]



- e. Two wattmeters are connected to measure power consumed by a 3-phase star connected load. What is the power factor of load if [2]  
1. Both wattmeters show equal reading  
2. Only one wattmeter shows reading
- f. Compare Ideal & Practical transformer [4]
- g. Draw input & output voltage waveforms of a centre tapped rectifier. [2]

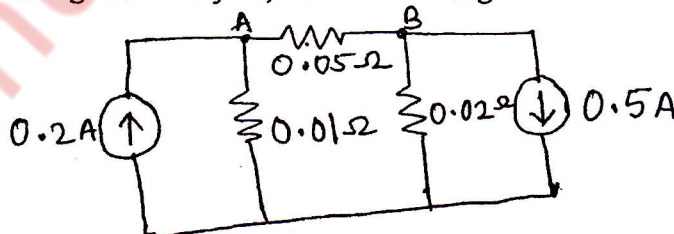**Q.2)** a. Using nodal analysis, find current through  $0.05 \Omega$  [6]




Turn Over

- b. A resistor  $R$  in series with capacitor  $C$  is connected to 50Hz, 240V source. [8]  
Find the value of  $C$  so that  $R$  absorbs 300W. Voltage across  $R$  is 100V
- c. A single phase transformer has 350 primary & 1050 secondary turns. The [6]  
primary is connected to a 400V, 50 Hz supply. If net cross sectional area of core is  $50 \text{ cm}^2$  find i) the max. Value of flux density in the core ii) the voltage induced in secondary winding

Q.3)

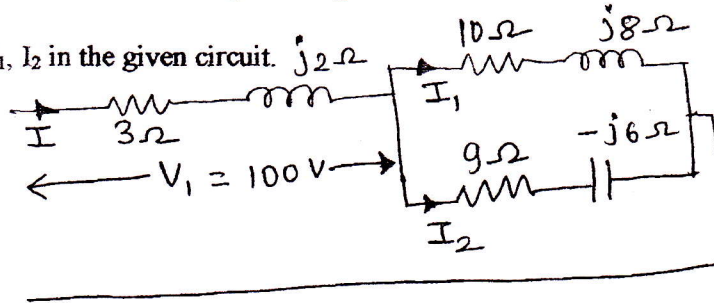- a. Find  $I$ ,  $I_1$ ,  $I_2$  in the given circuit. [8]



- b. Obtain equivalent circuit of a 200/400V, 50Hz single phase transformer [6]  
from the following test data


OC test: 200V 0.7A 70W (on lv side)

SC test: 15V 10A 85W (on hv side)

- c. Draw and explain the output characteristic of CE transistor configuration [4]
- d. Explain capacitor filter. [2]

Q.4)

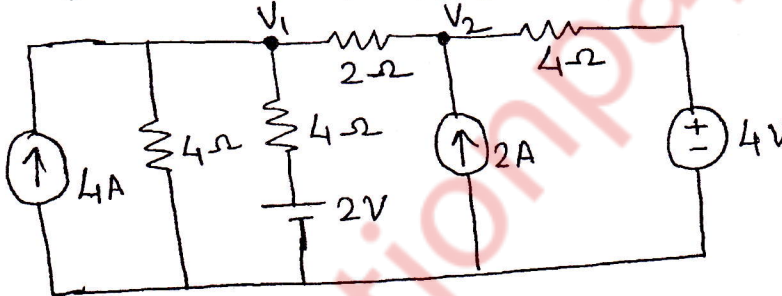
- a. Using source transformation, find  $V_1$ ,  $V_2$  in the circuit shown [7]



- b. A balanced star connected load of  $(8+j6)\Omega$  per phase is connected to a three [4]  
phase 400V supply. Find the line current & power factor.
- c. An iron choke coil takes 4A current when connected to a 20V dc supply & [5]  
takes 5A from 65V, 50Hz ac supply. Determine  $R$  &  $L$  of the coil.
- d. Draw and explain the working of full wave rectifier in detail [4]


Q.5)

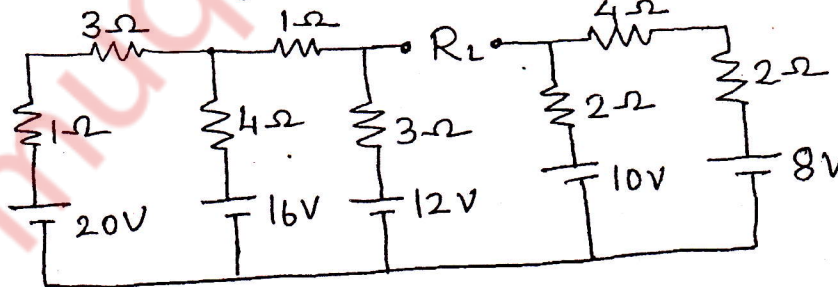- a. Det. The value of  $R_L$  for max. Power at the load. Calculate  $P_{max}$ . [8]



Turn Over

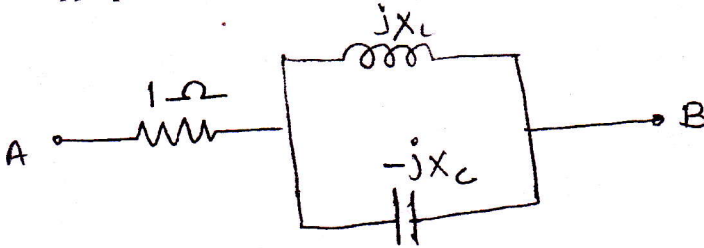
- b. Draw admittance triangle between terminals A & B labelling with its sides [5]  
with appropriate values & units if  $X_L = 4\Omega$   $X_C = 8\Omega$



- c. The wattmeter reads iron losses in OC test & copper losses in SC test of a transformer. Justify. [7]

Q.6)

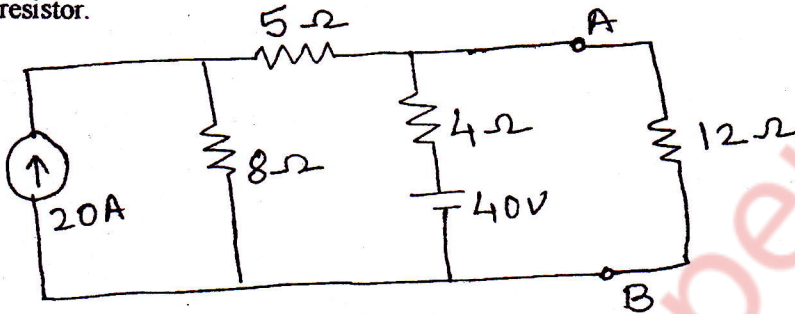- a. Draw Norton's equivalent source across AB & find current through  $12\Omega$  resistor. [7]



- b. A circuit consist of a resistance of  $4\Omega$  & inductance of  $0.5H$  & a variable capacitance in series across a  $100V$ ,  $50Hz$  supply. Calculate [7]  
i) Value of capacitance to produce resonance  
ii) Voltage across capacitor  
iii) Q factor of the circuit
- c. In a 3-phase star connected load, show that  $V_L = \sqrt{3}V_{PH}$  &  $I_L = I_{PH}$  [6]