

QP Code : 30708


(3 Hours)

[Total Marks : 100]


- N. B. : (1) Question No. 1 is compulsory.
 (2) Attempt any three questions from remaining five questions.
 (3) Assume suitable data wherever necessary.



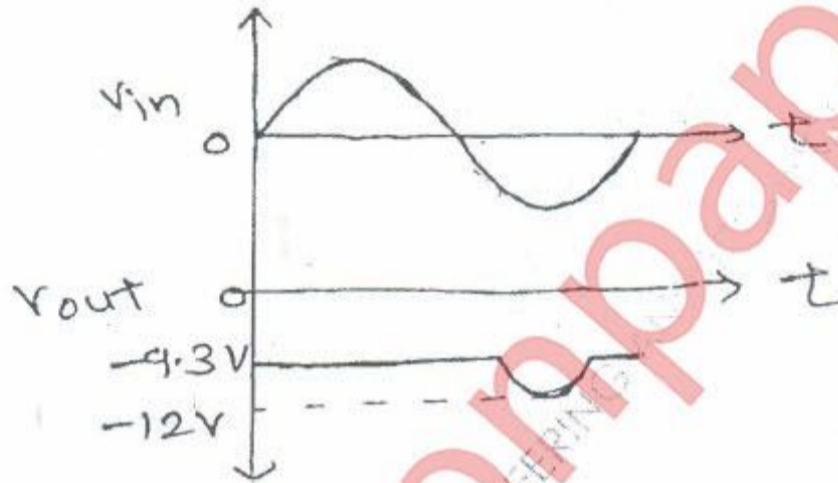1. (a) Compare CE and CS amplifier. 5
- (b) Draw and explain input-output characteristics in CB configuration. 5
- (c) Explain working of enhancement type MOSFET with characteristics. 5
- (d) Discuss Graphical Method of calculating h-parameters. 5
2. (a) Design a circuit which will give the following output wavetern. 5



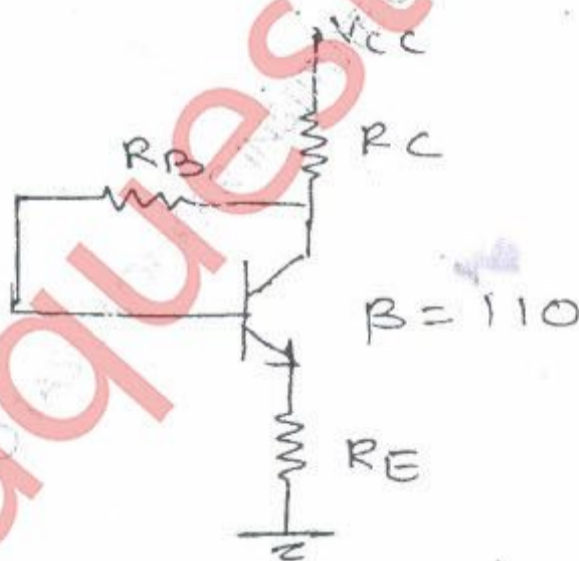- (b) Calculate for the following circuit 5
 - (i) I_B (ii) I_C (iii) V_{CE} (iv) BJT power consumption




$R_C = 2.7 k\Omega$

$R_B = 480 k\Omega$

$R_E = 1.2 k\Omega$

(c) Calculate A_V , R_{in} , R_O and f_L


10

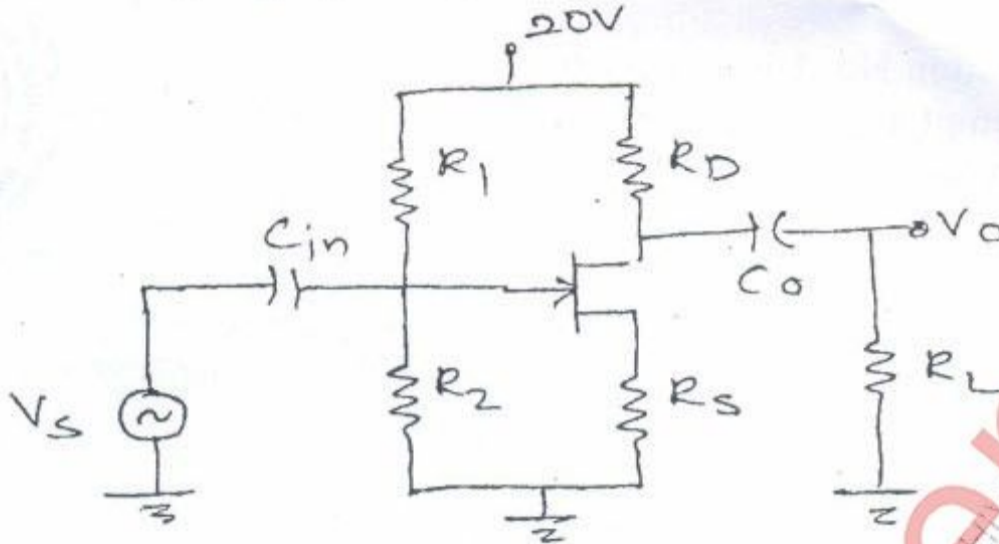

Given : $R_1 = 910\text{k}\Omega$, $R_D = 2.2\text{ k}\Omega$
 $R_2 = 220\text{k}\Omega$, $R_S = 1.2\text{ k}\Omega$
 $C_{in} = 47\mu\text{F}$, $C_O = 10\mu\text{F}$
 $C_S = 1\mu\text{F}$, $R_L = 10\text{ k}\Omega$
 $r_d = \infty$, $g_m = 5.6\text{ m}\Omega$

3. (a) Calculate Z_{in} , Z_O , A_V and V_O


10

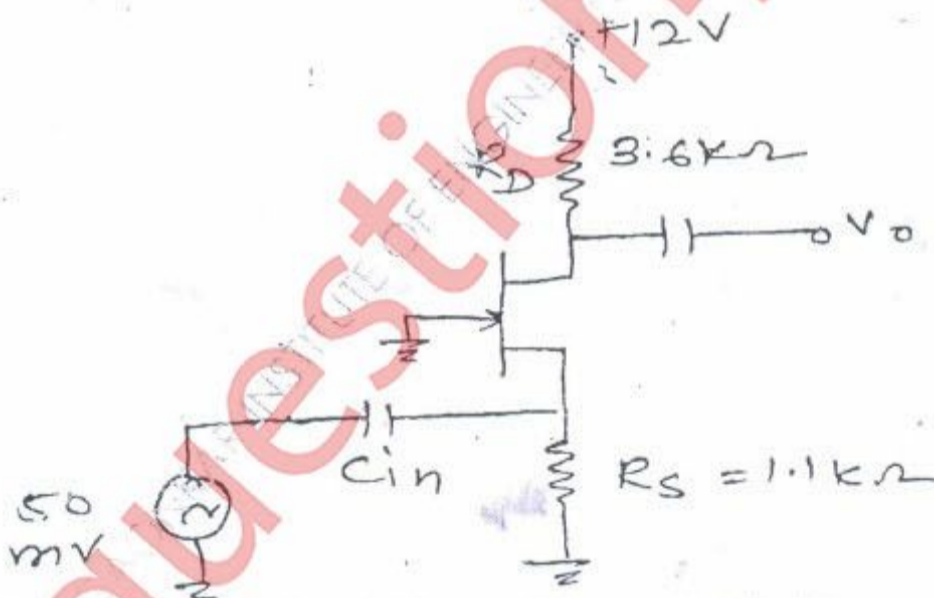

Given : $I_{DSS} = 10\text{mA}$, $V_P = -4\text{V}$, $r_d = 40\text{k}\Omega$, $V_{GSQ} = -2.2\text{V}$

(b) Calculate Q-point, A_v , Z_{in}

10

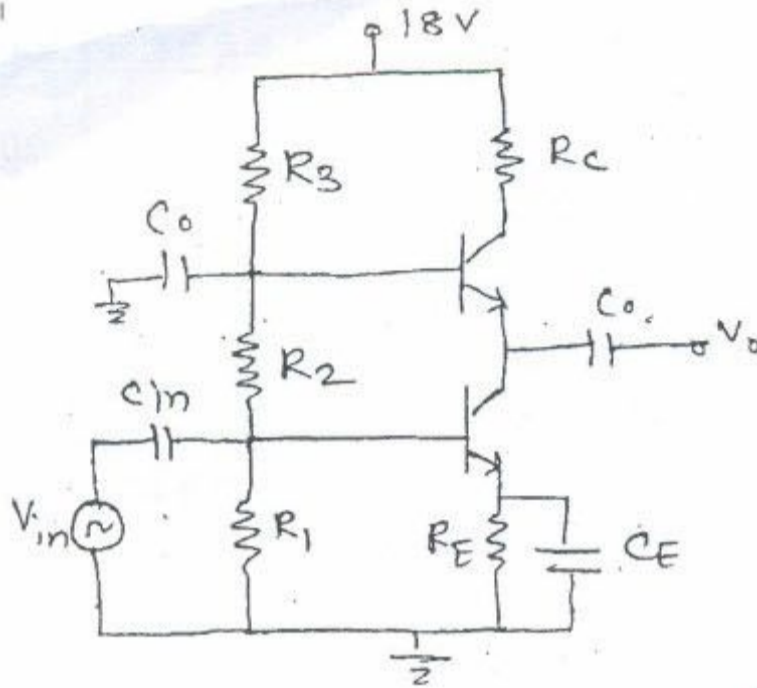

Given!

$V_{BB} = 0.6V$

$R_1 = 4.7k\Omega$

$R_2 = 5.6k\Omega$

$R_3 = 6.8k\Omega$

$R_E = 1.1k\Omega$

$R_C = 1.8k\Omega$

$\beta = 120$

$C_{in} = 5\mu F$

$C_o = 10\mu F$

4. (a) Design a single stage CE Amplifier for audio frequency range with

16


$|A_v| = 220, S \leq 10, V_o = 4V, f_L \leq 20HZ$

(b) For the above designed circuit calculate A_v , R_{in} , R_o

4

5. (a) Calculate A_v , Z_{in} and f_L

10

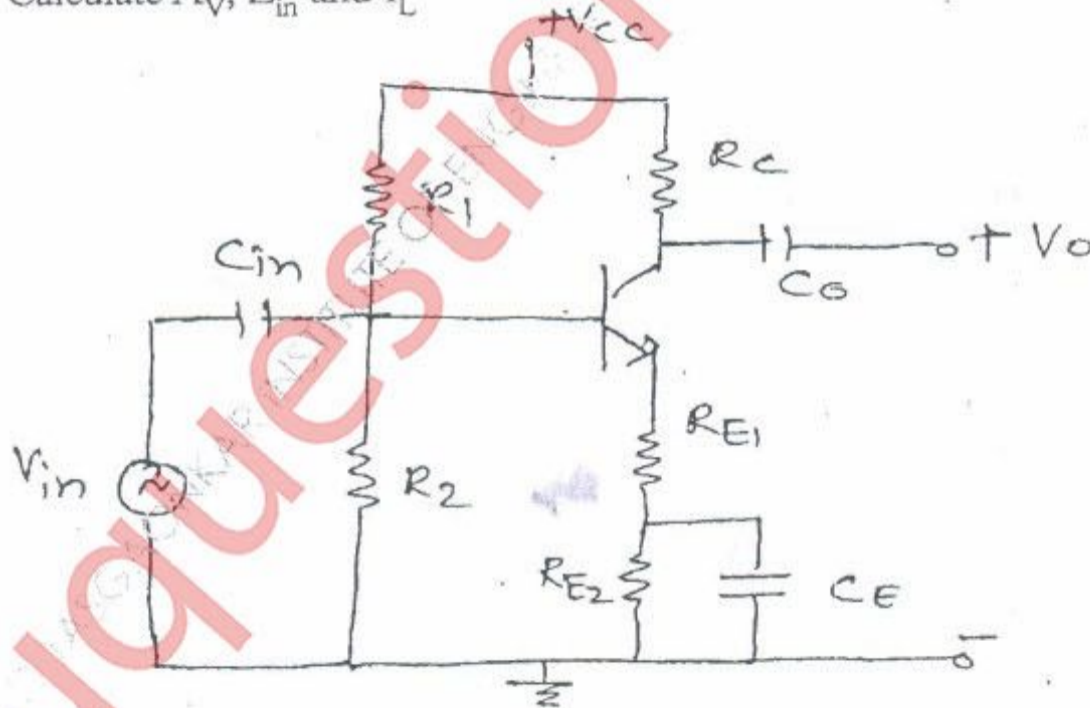

Given : $h_{ie} = 1k\Omega, h_{fe} = 100, R_1 = 47k\Omega$

$R_2 = 10k\Omega, R_C = 3.3k\Omega, R_{E1} = 470\Omega,$

$R_{E2} = 470\Omega, C_{in} = 10\mu F, C_o = 10\mu F, C_E = 4.7\mu F$

[TURN OVER

(b) Draw low frequency and high frequency model of JFET in CS configuration and derive expressions for lower and higher cut-off frequencies. (Consider by-pass capacitor) 10

6. Write short notes on (any two) :- 20

- (a) Discuss Darlington Amplifier with circuit diagram, DC and AC analysis, advantages, disadvantages and applications.
- (b) Draw various biasing schemes of BJT and calculate their stability factor.
- (c) Draw a neat diagram of JFET CG amplifier. Derive expressions for A_v , Z_i , Z_o .

DBEC DATA SHEET

Transistor type	P _{dm} max @ 25°C Watts	I _{cm} max @ 25°C Amps	V _{ce} min Volts	V _{ce} max Volts	V _{ce} (Sus) Volts	V _{ce} (Sus) d.c. Volts	V _{ce} (Sus) d.c. Volts	V _{ce} (Sus) d.c. Volts	V _{ce} (Sus) d.c. Volts	T _j max °C	D.C. current gain		Signal typ.	h _{FE} max.	V _{ec} max.	
											min	max				
2N3055	115.5	15.0	1-1	100	60	70	90	7	200	20	50	70	15	50	120	1-8
ECN055	50.0	5.0	1-0	60	50	55	60	5	200	25	50	100	25	75	125	1-5
ECN149	30.0	4.0	1-0	50	40	—	—	8	150	30	50	110	33	60	115	1-2
ECN100	5.0	0.7	0.5	70	60	65	—	6	200	50	90	280	50	90	280	0-9
BC147A	0.25	0.1	0.25	50	45	50	—	6	125	115	180	220	125	220	260	0-9
2N525(PNP)	0.225	0.5	0.25	85	30	—	—	—	100	35	—	65	—	45	—	—
BC147B	0.25	0.1	0.25	50	45	50	—	6	125	200	290	450	240	330	500	0-9

BFW 11—JFET MUTUAL CHARACTERISTICS

Transistor type	h _{ie}	h _{oe}	h _{re}	a _{ja}	-V _{GS} volts		I _D max		-V _P Volts		r _d		Derate			
					1.5 x 10 ⁻⁴	0.4°C/mw	0.0	0.2	0.4	0.6	0.8	1.0	1.2	1.6	2.0	2.4
BC 147A	2.7 K Ω	18 μ Ω	1.5 x 10 ⁻⁴	0.4°C/mw	10	9.0	8.3	7.6	6.8	6.1	5.4	4.2	3.1	2.2	2.0	1.1
2N 525 (PNP)	1.4 K Ω	25 μ Ω	3.2 x 10 ⁻⁴	—	7.0	6.0	5.4	4.6	4.0	3.3	2.7	1.7	0.8	0.2	0.0	0.0
BC 147B	4.5 K Ω	30 μ Ω	2 x 10 ⁻⁴	0.4°C/mw	4.0	3.0	2.2	1.6	1.0	0.5	0.0	0.0	0.0	0.0	0.0	0.0

N-Channel JFET

Type	V _{DS} max Volts	V _{GS} max Volts	P _D max @ 25°C	T _j max °C	I _D max	g _{fs}	-V _P Volts	r _d	Derate above 25°C
2N3822	50	50	300 mW	175°C	2 mA	3000 μΩ	6	50 KΩ	2 mW/°C
BFW 11 (typical)	30	30	300 mW	200°C	7 mA	5000 μΩ	2.5	50 KΩ	—

UJT type	P _D max @ 25°C	I _B max	I _P	V _{BS} max	V _{BS} min	T _j max	η	r _{BB} KΩ	I _P max
2N2646	300mW	50mA	2Amp.	30	35	125°C	0.56	4.7	9.1