

Q.P. Code :24699

18

[Marks:80]


[Time: 3 Hours]

Please check whether you have got the right question paper.

N.B:


1. Question No. 1 is compulsory.
2. Attempt any three questions out of the remaining five.
3. Assume suitable data if required.
4. Figures to the right indicate full marks.

Q.1 a) Find voltages V_1 and V_2

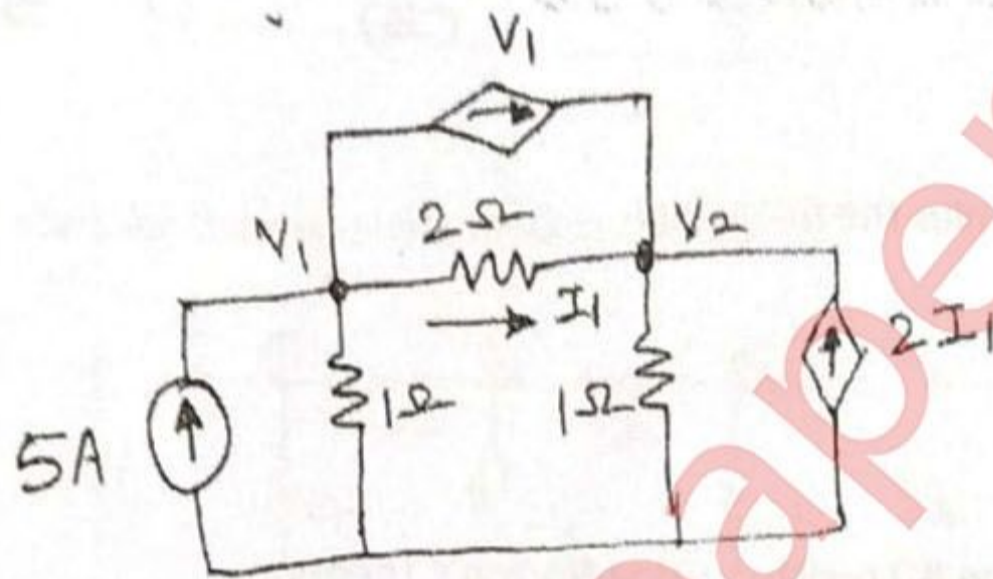


05

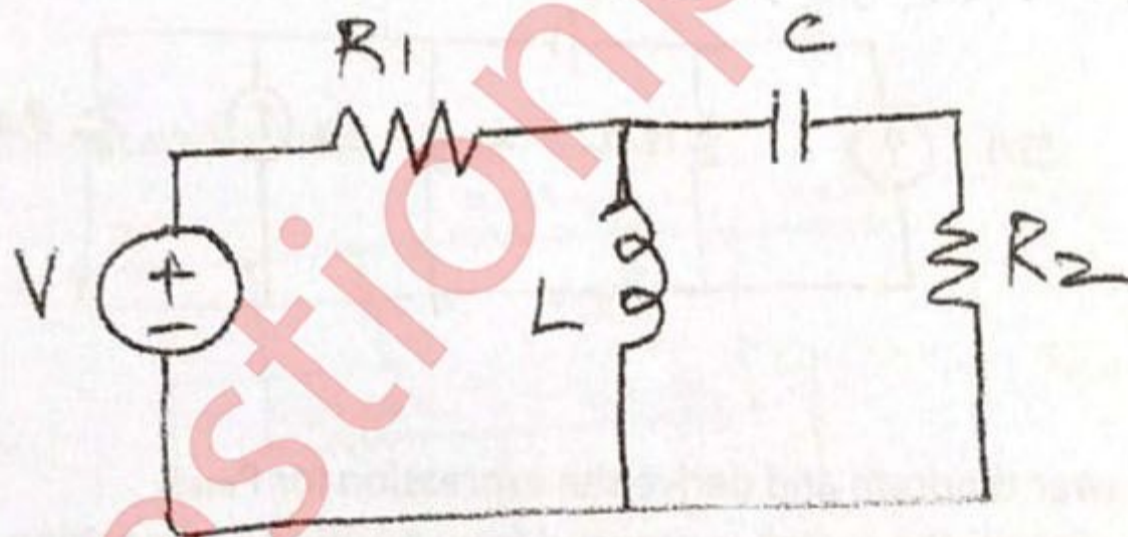b) Draw the dual of the following network.



05

c) Find the current in the 5Ω resistor.

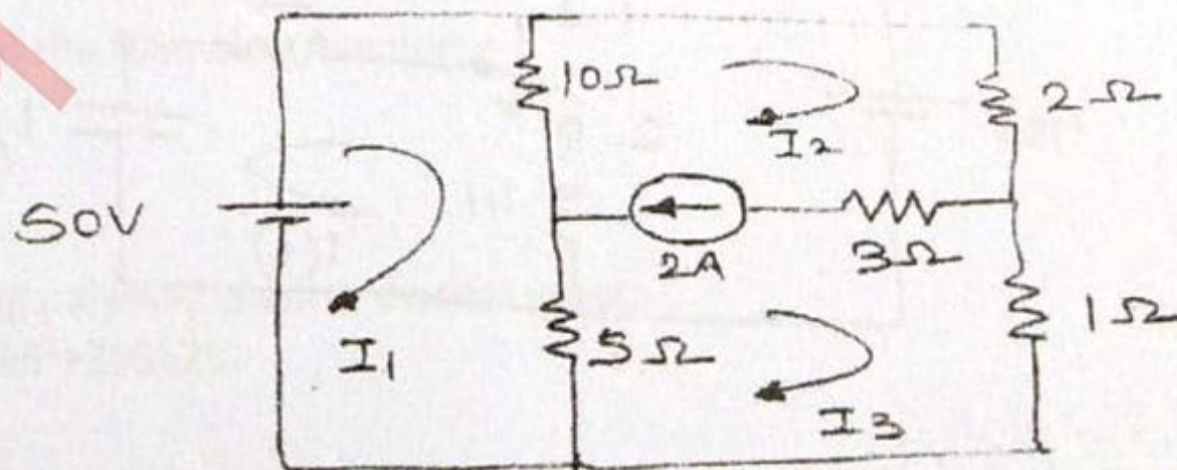

05


d) Write a short note on Initial conditions and its significance

05

81

Q.P. Code :24699

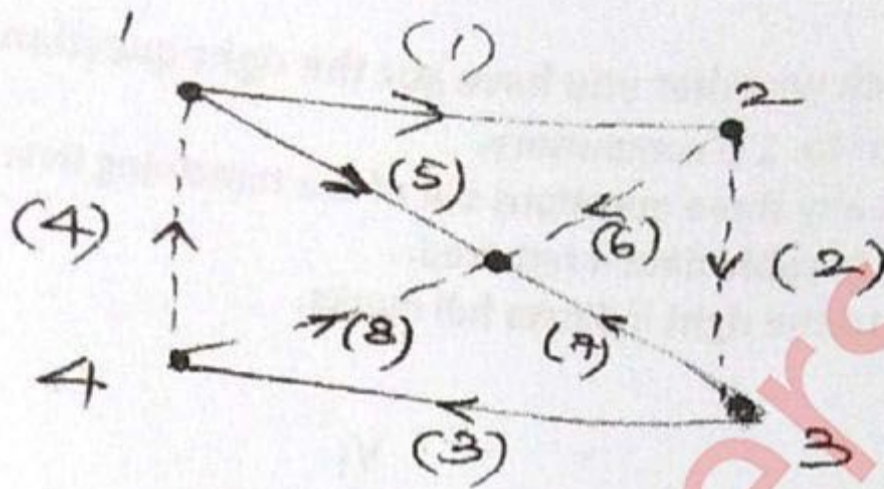
Q.2 a) For the graph shown, write the incidence matrix, tieset matrix and f-cutest matrix.



b) Define with suitable examples the following:-


- i) Planar graph.
- ii) Non-planar graph.
- iii) Tree
- iv) Co-tree.

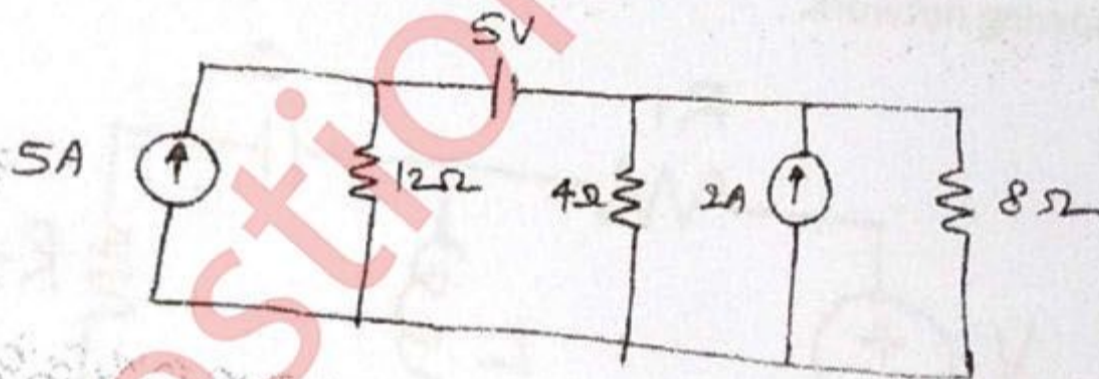Q.3 a) Find the current through the 8Ω resistor, using Norton's Theorem.



b) Derive the maximum power theorem and derive the expression for P_{max} .

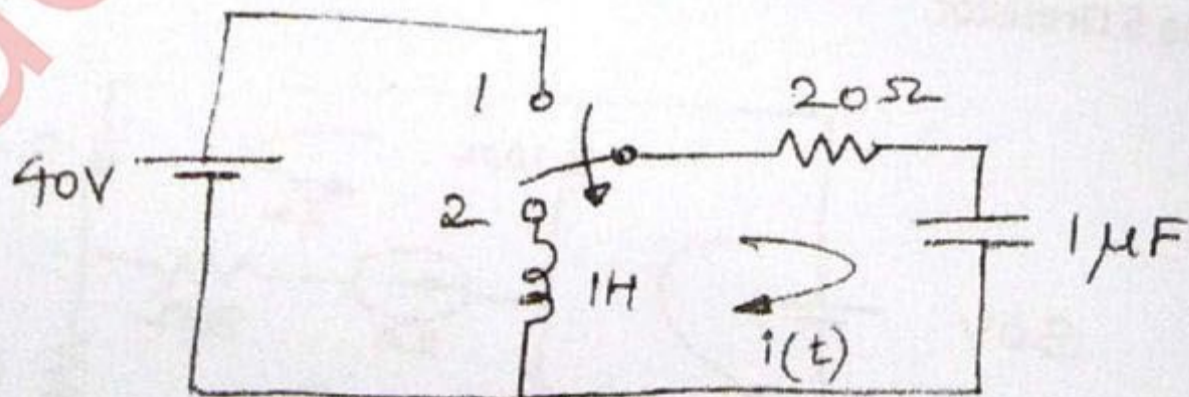
c) In the network shown in figure, the switch is changed from position 1 to position 2 at $t=0$, steady condition having reached before switching. Find the values of i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t=0^+$



Q.P. Code :24699


a) In a network shown the switch is closed at $t=0$. Determine $i_2(t)$

10

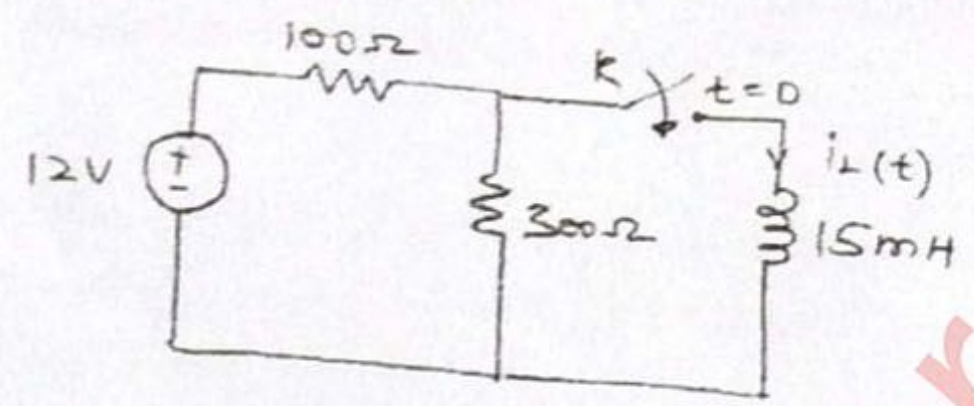


b) Determine the Y and Z parameters for the network shown in the fig.

10

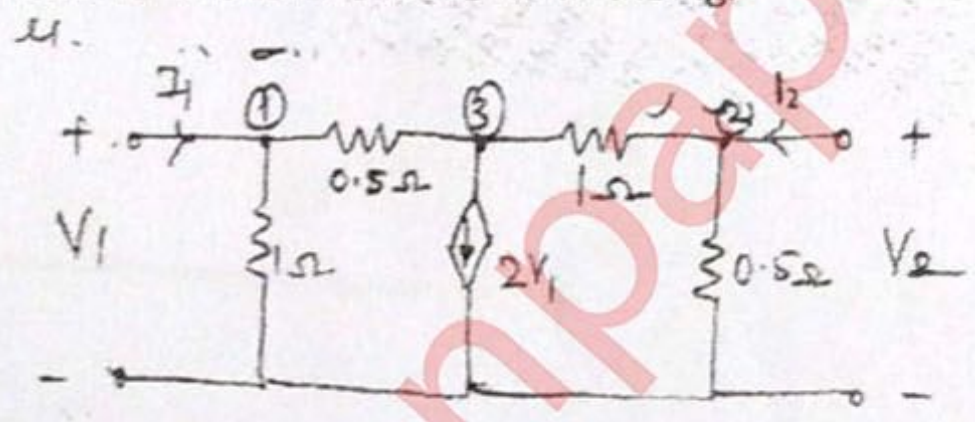

a) Find the Y parameters of the network shown.

10

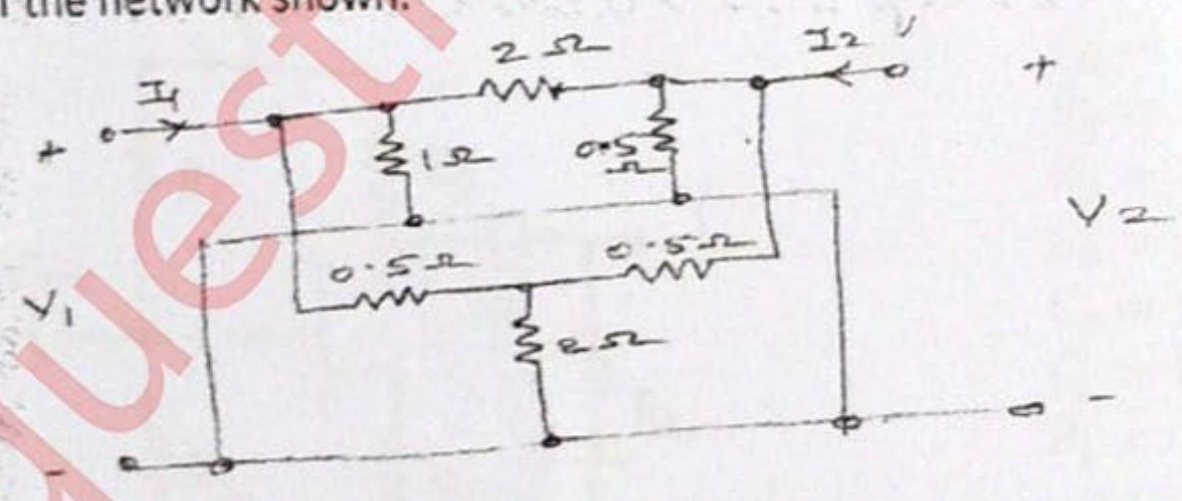

b) Define transmission parameters and find their condition of reciprocity and symmetry.

10

Q.6 a) Realize the foster forms of the following function:-

10

$$z(s) = \frac{2(s+2)(s+4)}{(s+1)(s+3)}$$

b) Check whether following polynomials are rewrite or not:-

10

i) $P(s) = 2s^6 + s^5 + 13s^4 + 6s^3 + 56s^2 + 25s + 25$

ii) $P(s) = s^8 + 5s^6 + 2s^4 + 3s^2 + 1$