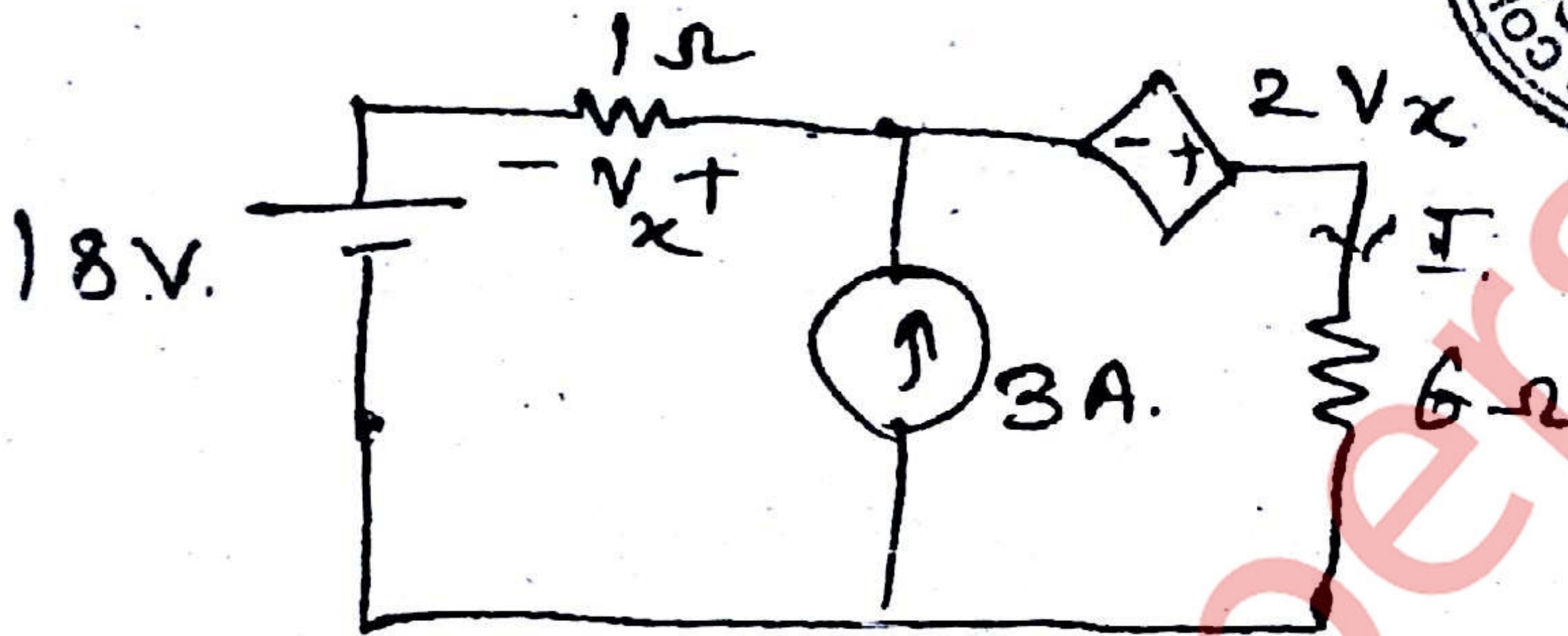


- N.B. : (1) Attempt any four questions out of six questions.  
 (2) Figures to the right indicate full marks.  
 (3) Assume data wherever necessary.



1. (a) Find the current in  $6\Omega$  resistor :-




(b) Test whether  $P(s) = s^4 + 7s^3 + 6s^2 + 21s + 8$  is Hurwitz or not.

5

(c) Draw the dual of the following network :-

5

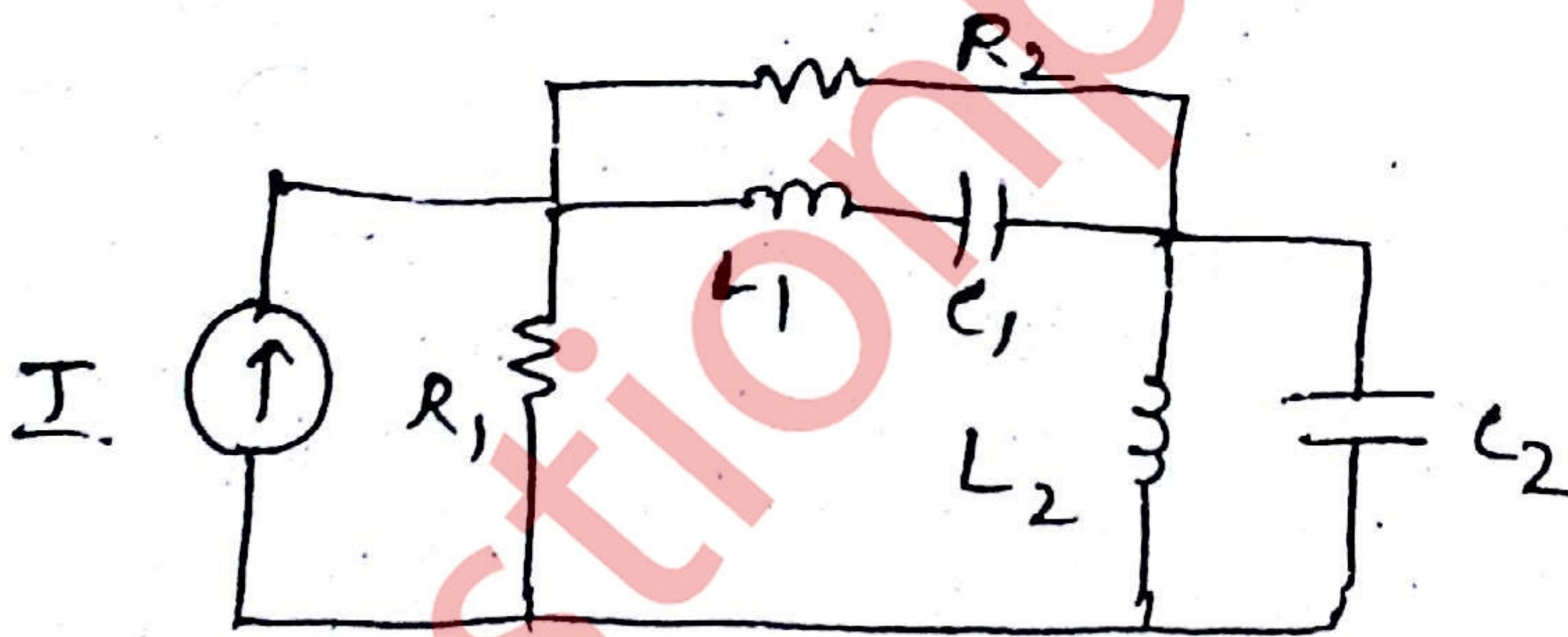


(d) Write a short note on initial condition and its significance.

5

2. (a) Find current  $i$  :-


10

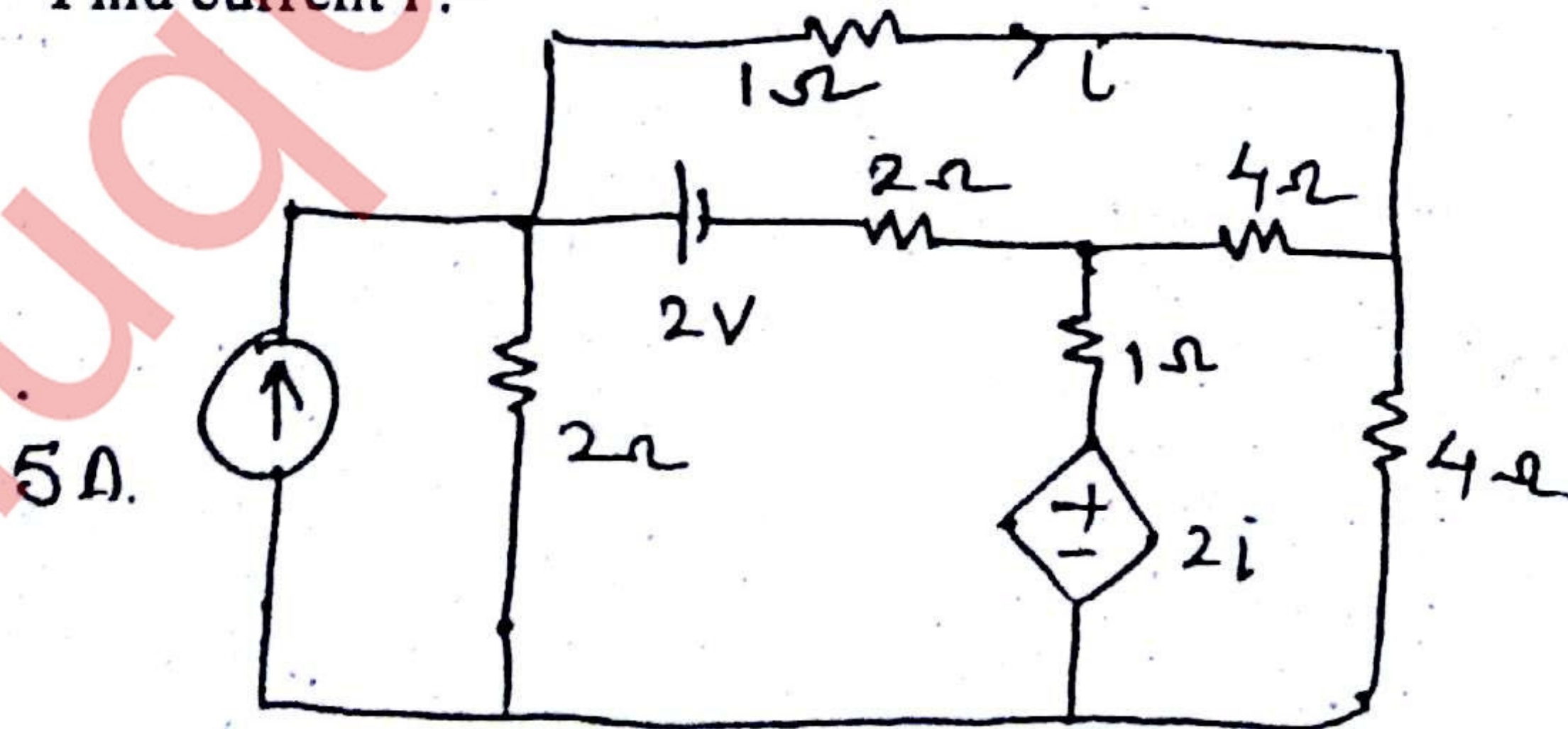




(b) Find  $V_o$  by superposition theorem :-

10

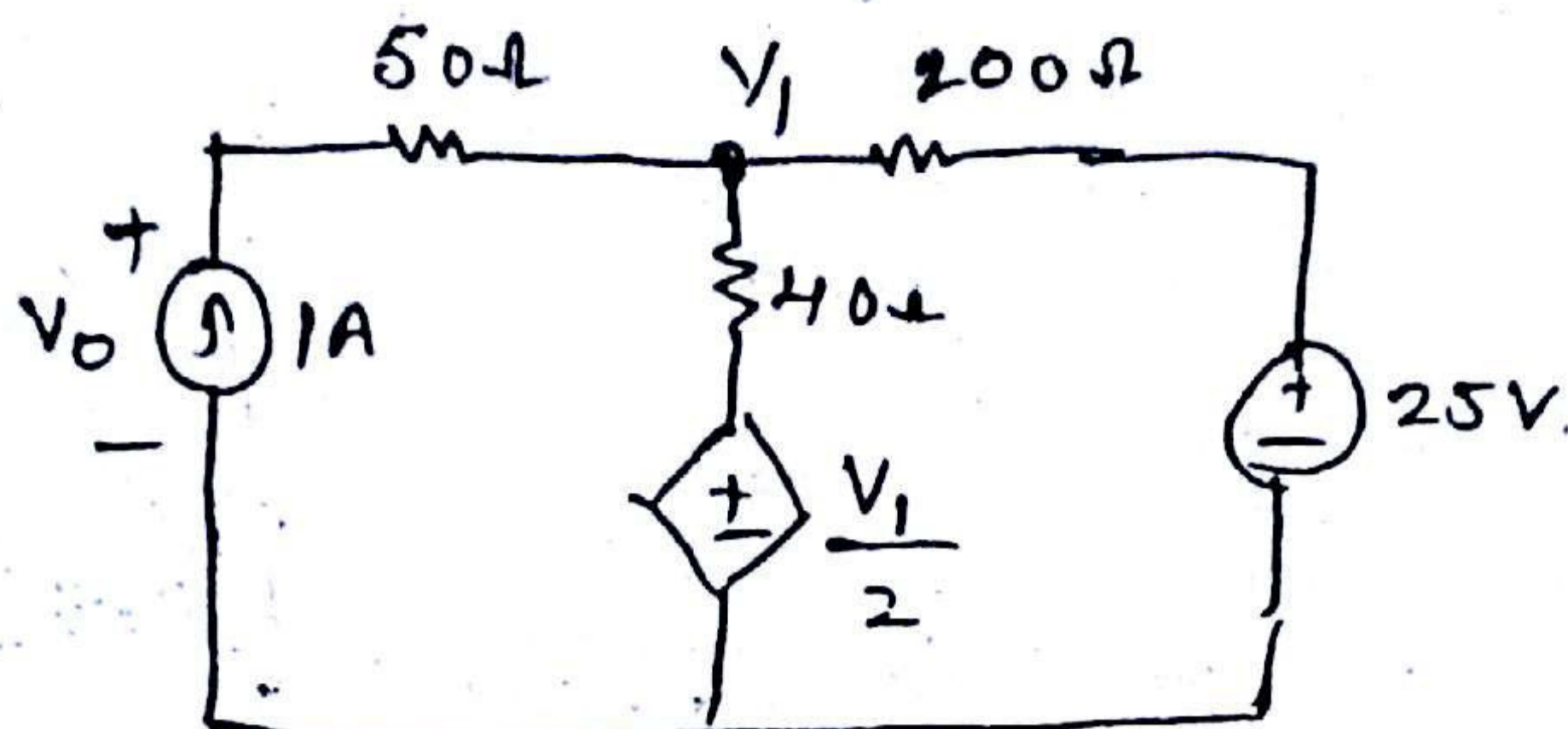


3. (a) The switch is closed at  $t=0$  find  $i_L(t)$  for  $t>0$  Also  $v_L(t)$  for  $t>0$  :-

10

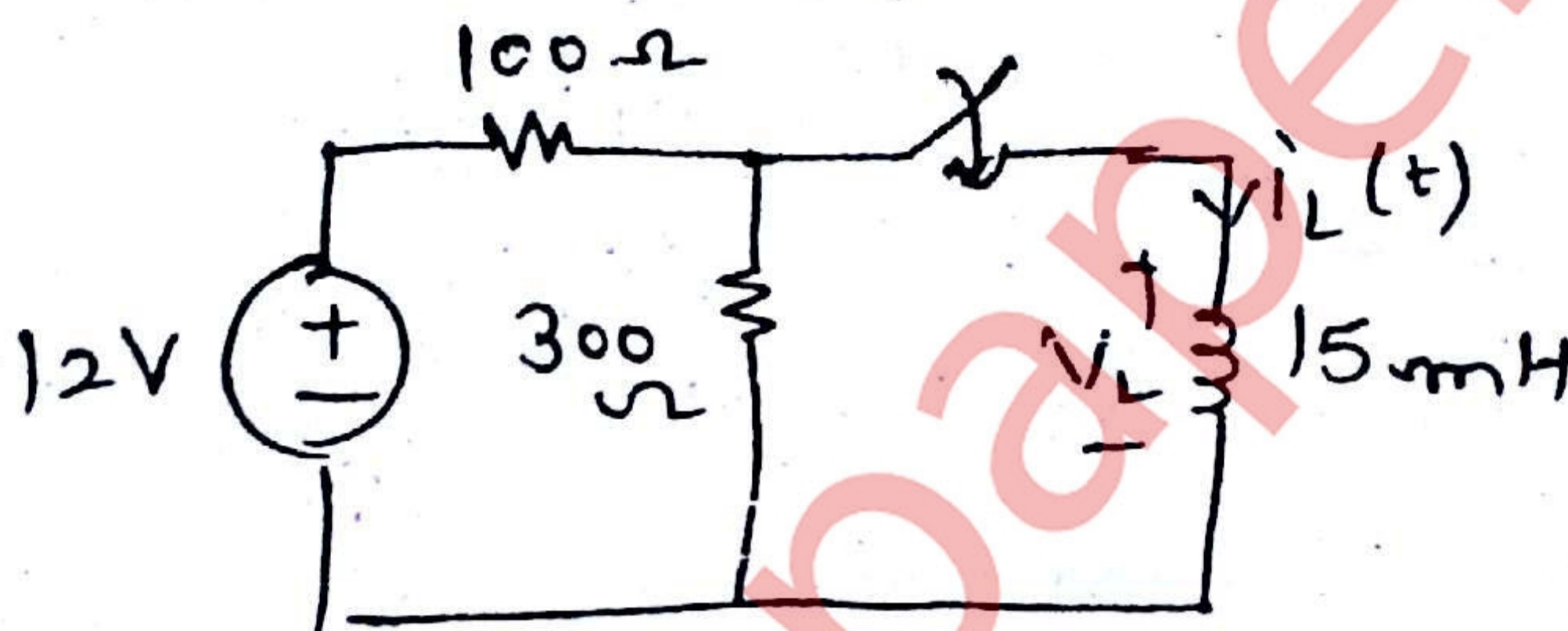

(b) Determine Y parameter and hence calculate Z parameter for the following network :-


10

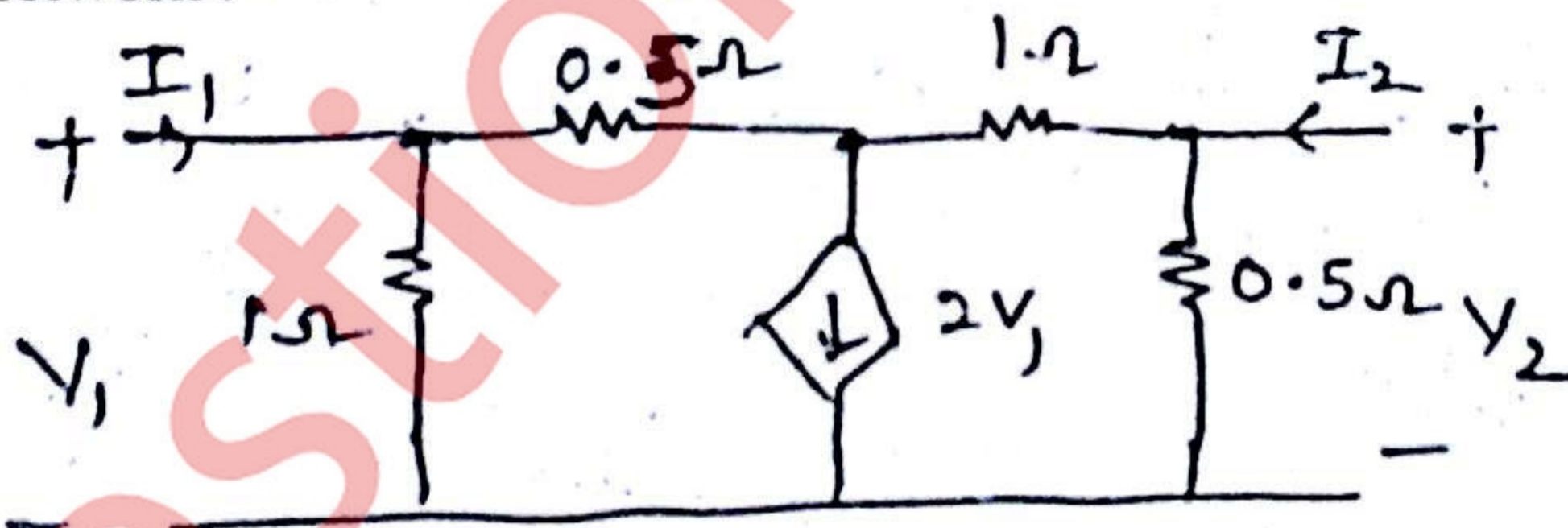

4. (a) For the tree shown below obtain :-

10

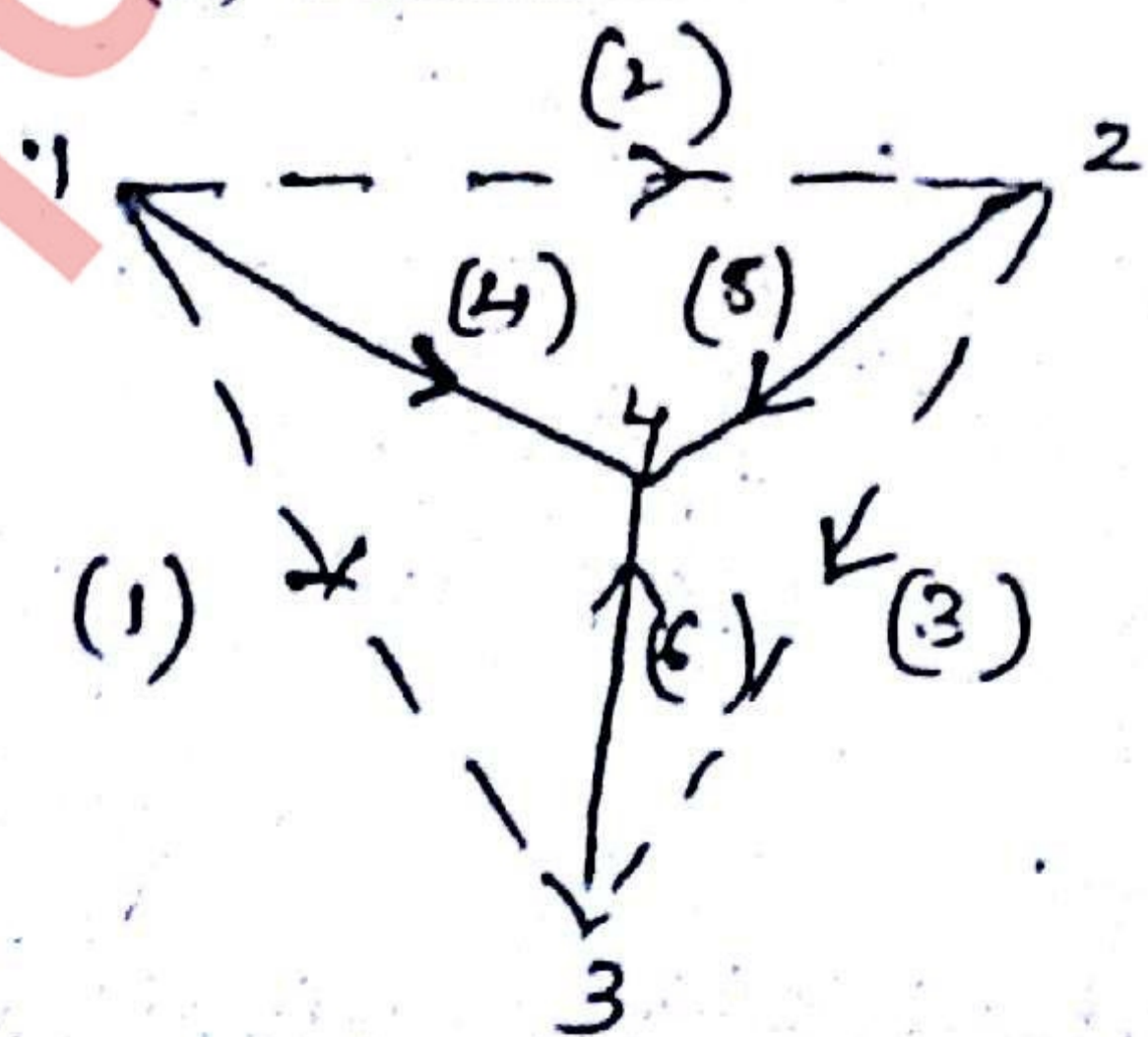- (i) Tieset matrix.
- (ii) Fundamental cutset matrix.




TURN OVER






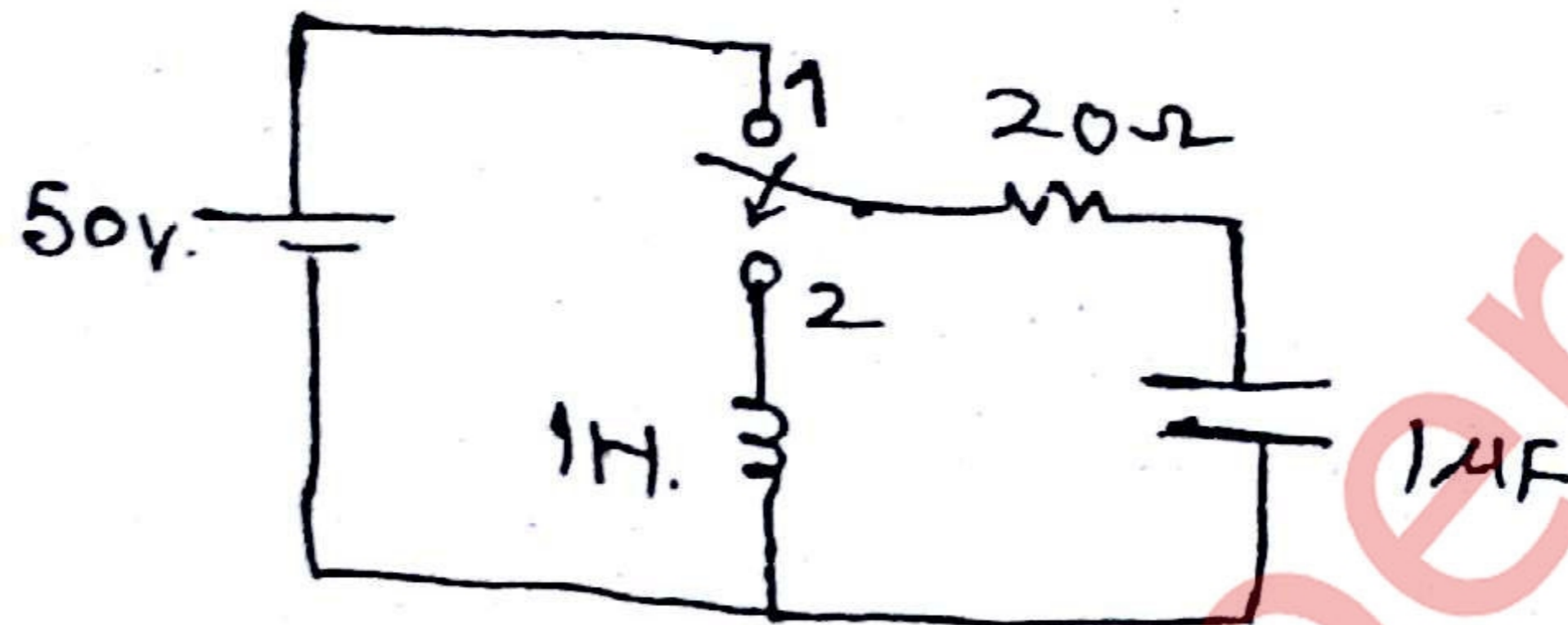- (b) Derive the condition of symmetry and reciprocity for h-parameters. 10
5. (a) For a given network the switch is in position 1 initially and steady state is achieved. At time  $t=0$ , the switch is changed to position 2. 10

Find  $i$ ,  $\frac{di}{dt}$ ,  $\frac{d^2i}{dt^2}$  for  $t=0^+$  :-



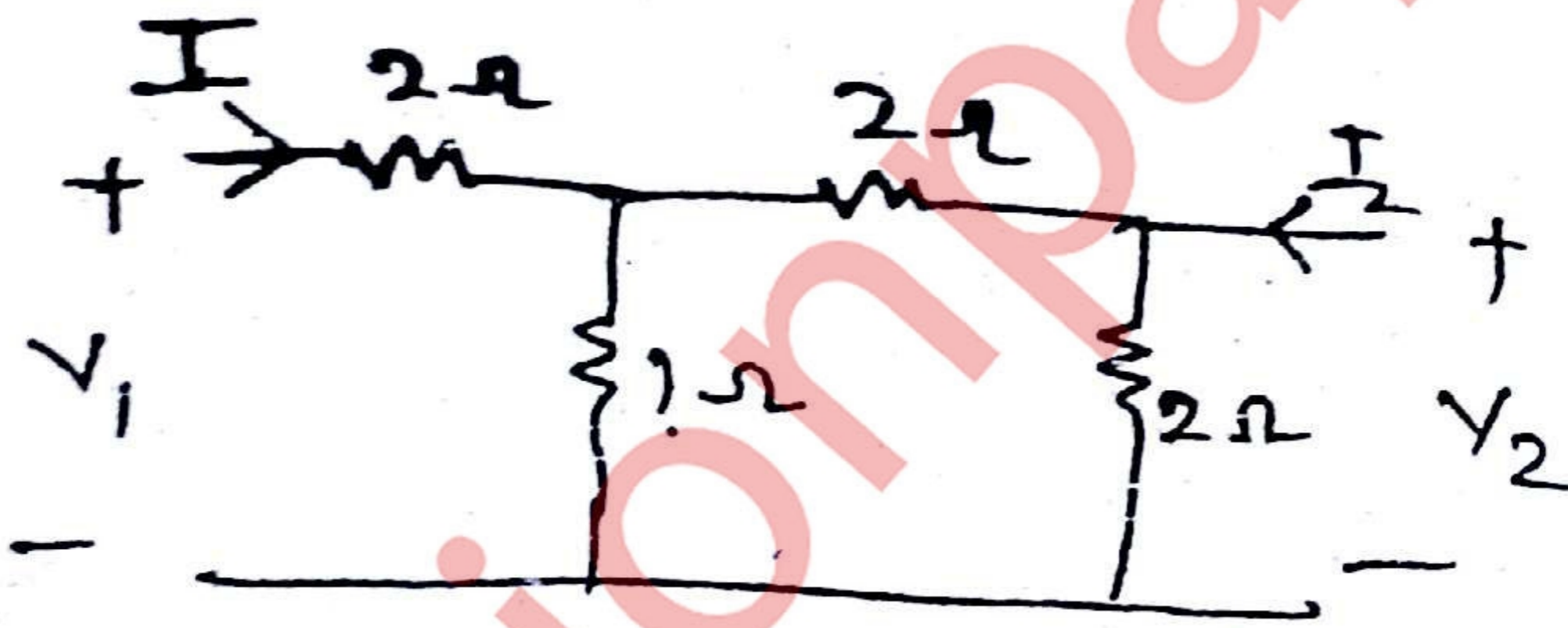- (b) Two identical section are connected in cascade, find transmission parameter for overall Cascaded network. 10



6. (a) Synthesis the given function in cauer I and cauer II forms :- 10

$$Z(s) = \frac{s^2 + 7s + 10}{s^3 + 10s^2 + 24s}$$

- (b) Synthesis the given function in Foster I and Foster II forms :- 10

$$Z(s) = \frac{(s^2 + 1)(s^2 + 3)}{s(s^2 + 2)}$$