

Q.P. Code : 534402

(3 Hours)

[Total Marks : 80

- N.B. :** (1) Question No.1 is **Compulsory**
(2) Attempt any **three** questions out of remaining **five** questions.
(3) Assume suitable data wherever necessary

1. Answer the following questions.

- (a) Explain cross-over distortion. **5**
(b) Explain precision full wave rectifier using op-amp **5**
(c) Compare RC phase shift and wein Bridge oscillator **5**
(d) Compare current series and current shunt negative feedback using op-amp **5**

2. (a) Derive frequency of oscillations and condition for sustained oscillations for RC phase shift oscillator along with circuit diagram **12**

- (b) Design op-amp based circuits for **8**
(i) $V_o = -2V_1 - 4V_2 + 3V_3$
(ii) $V_o = +\frac{dv_{in}}{dt}$

3. (a) For the following given specifications for DIBO. Differential amplifier Calculate I_C , V_{CEQ} , A_d , AC , $CMRR$, R_p , R_o **10**
Given : $R_C = 3.8k\Omega$, $V_{BE} = 0.5V$, $R_{in1} = R_{in2} = 150\Omega$, $\beta_{ac} = \beta_{dc} = 90$
 $R_E = 1.2K$

(b) Draw and explain Block diagram of op-amp **5**


(c) Design a schmitt trigger for $V_{UT} = 4V$, $V_{LT} = 3V$, $V_{CC} = V_{EE} = \pm 15V$ **5**

4. (a) Design 3 op-amp Instrumentation amplifier for gain $A_{VT} = 600$. **5**

(b) Design a class B push pull power amplifier deliver a peak power of 3 watts into a resistive load of 12Ω with low distortion. Assume supply voltage = 24V. **15**

[TURN OVER

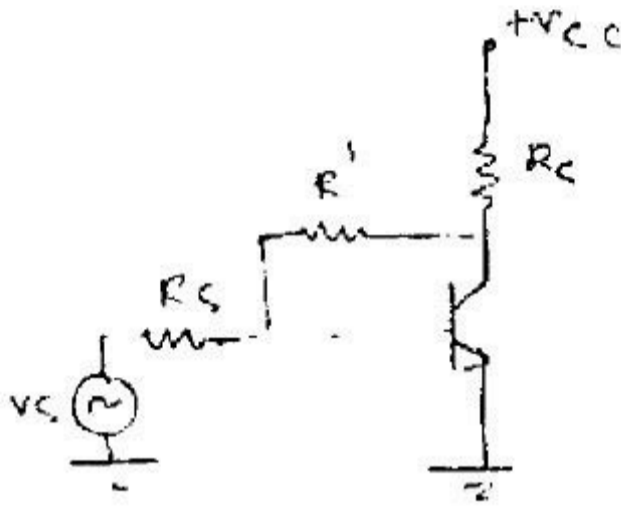5. (a) Identify the type of negative feedback used in below circuit and find A_{vf} , R_{if} and R_{of} 10



$$R_C = 4k\Omega$$

$$R_1 = 40k\Omega$$

$$R_2 = 10k\Omega$$

$$R_E = 1k\Omega$$

$$h_{fe} = 50$$

$$h_{re} = h_{oe} = \infty$$

- (b) Explain concept of virtual ground in op-amp 5
- (c) Draw and explain a circuit to convert sine wave into square wave. 5
6. Write short notes on (Any **Four**) 20
- Peak detector using op-amp
 - Practical Integrator
 - Heat sink and its design steps
 - Antilog Amplifier
 - Constant current source circuit used in differential amplifier

Transistor type	P _{dm} max @ 25°C Watts	I _{cm} max @ 25°C Amps	V _{GS} max volts d.c.	V _{GS} min volts d.c.	V _{DS} (500 Hz)	V _{GS} (500 Hz) d.c.	V _{GS} (500 Hz) d.c.	V _{GS} (500 Hz) d.c.	V _{GS} (500 Hz) d.c.	V _{GS} (500 Hz) d.c.	T _j max °C	D.C. current		Signal typ.	h _{FE} min.	V _{GS} max max.	θ _{JA} °C/W	Derate above 25°C W/°C
												min	typ.					
2N 3055	115.5	15.0	1-1	0.00	40	70	90	7	200	20	50	70	15	50	120	1.8	1.5	0.7
ECN 055	50.0	5.0	1.0	0.0	50	55	60	5	200	25	50	100	25	75	125	1.5	3.5	0.4
ECN 149	30.0	4.0	1.0	0.0	40	—	—	8	150	30	50	110	33	60	115	1.2	4.0	0.3
ECN 100	5.0	0.7	0.6	0.0	60	65	—	6	200	50	90	280	50	90	280	0.9	3.5	0.03
BC147A	0.25	0.1	0.25	0.0	4.5	50	—	6	125	115	180	220	125	720	260	0.9	—	—
2N 525(PNP)	0.25	0.1	0.25	0.0	30	—	—	—	100	35	—	65	—	45	—	—	—	—
BC147B	0.25	0.1	0.25	0.0	45	50	—	6	125	200	250	450	240	330	500	0.9	—	—

BFW 11—JFET MUTUAL CHARACTERISTICS

Transistor type	h _{ie}	h _{oc}	h _{re}	θ _{JA}
BC 147A	2.7 K Ω	18μ Ω	1.5 × 10 ⁻⁴	0.4°C/mW
2N 525 (PNP)	1.4 K Ω	25μ Ω	3.2 × 10 ⁻⁴	—
BC 147B	4.5 K Ω	30μ Ω	2 × 10 ⁻⁴	0.4°C/mW
ECN 100	500 Ω	—	—	—
ECN 149	250 Ω	—	—	—
ECN 055	100 Ω	—	—	—
2N 3055	25 Ω	—	—	—

—V _{GS} volts	I _D	g _m	g _{fs}	g _{os}	τ _d	Derate above 25°C	θ _{JA}
I _D max. mA	0.2	0.4	0.6	0.8	1.0	2.4	3.5
I _D typ. mA	1.0	1.2	1.6	2.0	2.5	3.0	4.0
I _D min. mA	7.6	5.4	4.6	4.0	3.3	2.7	2.0
	4.0	2.2	1.6	1.0	0.5	0.0	0.0

N-Channel JFET

Type	V _{GS} max Volts	V _{DS} max Volts	V _{GS} max Volts	P _D max @ 25°C	I _D max	I _{DS}	g _{os} (typical)	τ _d	Derate above 25°C	θ _{JA}
2N5822	50	50	30	300 mW	2 mA	3000 μs	6	50 KΩ	2 mW/°C	0.59°C/mW
BFW 11 (typical)	30	30	30	300 mW	7 mA	5600 μs	2.5	50 KΩ	—	0.59°C/mW