

15/15

19


Electronic Circuits Analysis & Design-II

(3 Hours)

[Total Marks : 80

- N.B. : (1) Question No. 1 is compulsory.
 (2) Attempt any three questions out of remaining five questions.
 (3) Assume suitable data wherever necessary.

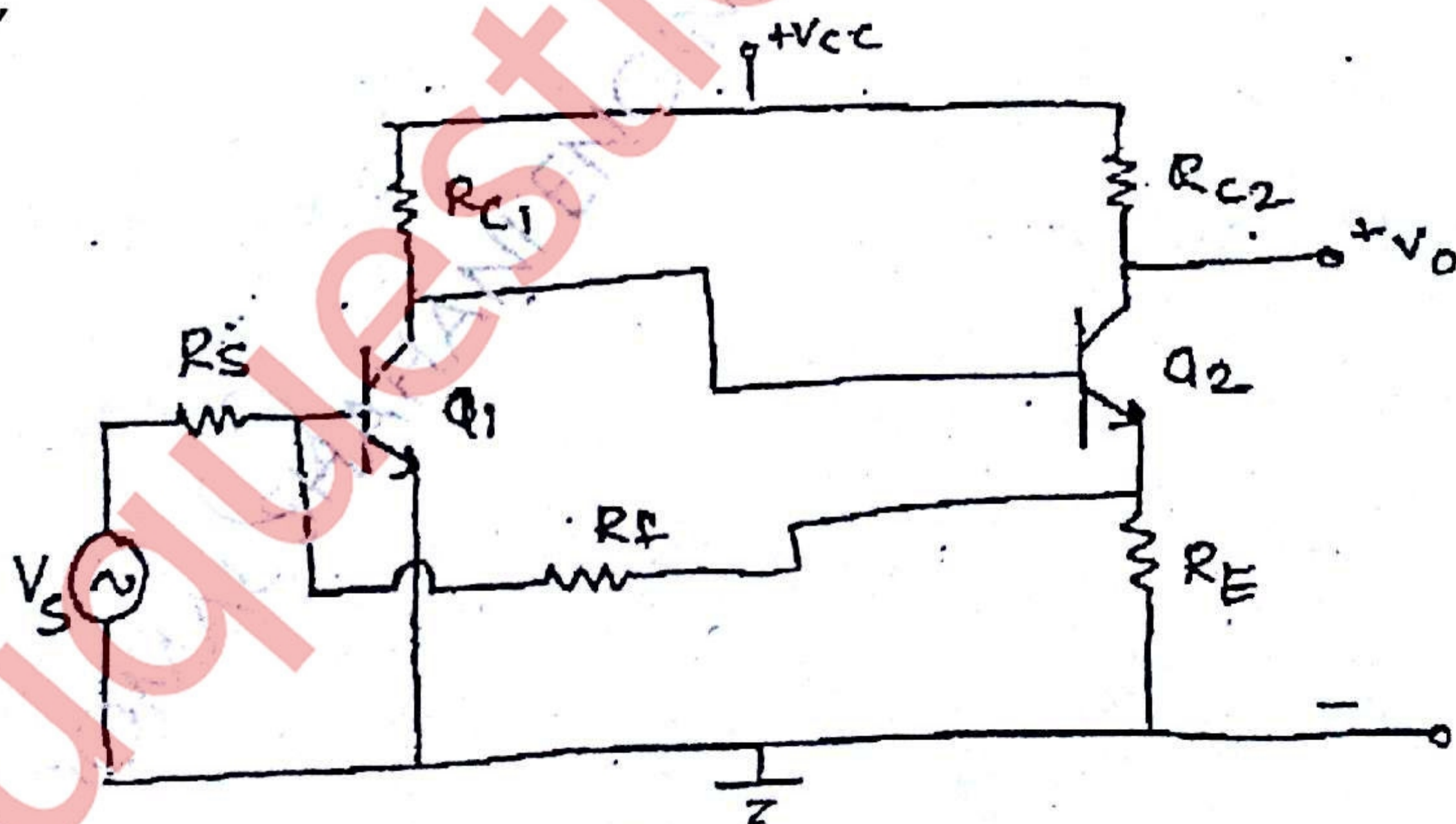1. (a) Derive Barkhausen's criteria for oscillations. 5
 (b) Explain zero crossing detector. 5
 (c) Give design steps for Heat sink used in power amplifiers. 5
 (d) Explain precision rectifier using Op-amp. 5
2. (a) Compare LC and RC oscillators. Draw Hartley oscillator and derive expression for frequency of oscillation and condition for oscillations. 10
 (b) Design class A transformer coupled power amplifier for output power of 15W to the speaker of 12 Ω. 10
3. (a) Write characteristics of instrumentation Amplifier. Derive gain formula of 3 op-Amp instrumentation amplifier. 10
 (b) Design Wein bridge oscillator for output frequency, $f = 8\text{kHz}$. 5
 (c) Design a schmitt trigger for $V_{UT} = 4\text{V}$, $V_{LT} = -4\text{V}$, $V_{CC} = V_{EE} = \pm 15\text{V}$ 5
4. (a) Calculate A_{vf} , R_{if} and R_{of} . 10



$h_{ef} = 50$, $R_f = 1.2\text{k}\Omega$, $R_{c1} = 3\text{k}\Omega$, $R_E = 50\Omega$, $h_{ie} = 1.1\text{k}\Omega$, $R_s = 1.2\text{k}\Omega$,
 $R_{c2} = 500\Omega$.

- (b) Draw monostable multivibrator and explain its operation with waveforms. 10

TURN OVER

27/5/15

2

BM/IV/CBGS/ECA

Q.P. Code : 3579

2

5. (a) Derive relations for DC and AC analysis of single input unbalanced output differential Amplifier. 10
(b) For the following given specifications for Dual input balanced output differential amplifier. 10

$R_c = 3.3k \Omega$, $R_{in1} = R_{in2} = 100 \Omega$.
 $R_E = 1 k \Omega$
 $V_{CC} = V_{EE} = |20V|$
 $\beta_{dc} = \beta_{ac} = 100$
 $V_{BE} = 0.7V$

Calculate :

- (i) I_C & V_{CEQ}
(ii) A_d
(iii) A_c
(iv) CMRR
(v) R_i & R_o

6. (a) Explain Block diagram of Op-amp. 5
(b) Design following circuit using Op-amp to obtain following outputs. 10
(i) $V_o = -3V_a + 2V_b - 5V_c + V_d$
(ii) $V_o = \frac{-dvin}{dt}$
(c) Compare current shunt and current series negative feedback using op-Amp. 5

TURN OVER

3

BM/IV/CBGS/ECAL

QP Code : 3579

3

DATA SHEET

Transistor type	P_{max} @ 25°C Watts	$V_{ce(sat)}$ volts	$V_{ce(sat)}$ volts	$V_{ce(sat)}$ volts	$V_{ce(sat)}$ volts	$V_{ce(sat)}$ volts	T_j max. °C	D.C. current mA	Signal V _{rms}	$R_{\theta jc}$ °C/W	V_{ce} max.	D_{stg} above 25°C W/C
2N 3055	115.5	1.1	70	90	7	200	20	50	50	120	1.4	0.7
ECN 055	50.0	1.0	55	60	5	200	25	50	75	125	1.5	0.4
ECN 149	30.0	1.0	—	—	8	150	30	50	60	115	1.2	0.3
ECN 100	5.0	0.6	65	—	6	200	50	90	90	280	0.9	0.05
BC147A	0.25	0.1	30	—	6	125	115	180	220	65	—	—
2N 525(PNP)	0.225	0.25	30	—	—	100	35	—	45	—	—	—
BC147B	0.25	0.1	45	—	6	125	200	190	320	450	0.9	—

RFW 115-VOLT MUTUAL CHARACTERISTICS

Transistor type	$R_{\theta jc}$ °C/W	V_{ce} max.	I_{ce} max.	V_{ce} min.	I_{ce} min.	V_{ce} max.	I_{ce} min.	V_{ce} min.	I_{ce} max.	V_{ce} min.	I_{ce} max.	V_{ce} min.	I_{ce} max.
BC 147A	2.7 K Ω	18V Ω	1.5 x 10 ⁻⁴	0.4	0.4	1.0	1.0	1.2	1.6	2.0	2.4	2.5	3.0
2N 525 (PNP)	1.4 K Ω	15V Ω	3.2 x 10 ⁻⁴	1.3	1.3	6.1	6.1	5.4	4.2	3.1	2.2	2.0	1.1
BC 147B	4.5 K Ω	30V Ω	2 x 10 ⁻⁴	5.4	5.4	3.3	3.3	3.7	1.7	0.8	0.2	0.0	0.0
ECN 100	50 Ω	—	—	—	—	—	—	—	—	—	—	—	—
ECN 149	15 Ω	—	—	—	—	—	—	—	—	—	—	—	—
ECN 055	12 Ω	—	—	—	—	—	—	—	—	—	—	—	—
2N 3055	6 Ω	—	—	—	—	—	—	—	—	—	—	—	—

N-Channel JFET

Type	V_{gs} max. Volts	V_{gs} (max.) Volts	V_{gs} max. Volts	I_{ds} max. mA	V_{gs} max. Volts	I_{ds} max. mA	V_{gs} max. Volts	I_{ds} max. mA	V_{gs} max. Volts	I_{ds} max. mA	V_{gs} max. Volts	I_{ds} max. mA	V_{gs} max. Volts	I_{ds} max. mA
2N3822	50	50	50	1 mA	175°C	2 mA	300 mV	3000 μ s	6	30 K Ω	2 mW/C	0.59°C/mW	—	—
2N3822 (typical)	30	30	30	7 mA	200°C	7 mA	300 mV	5000 μ s	2.5	50 K Ω	—	0.59°C/mW	—	—