

(3 Hours)

[Total Marks : 80]

- N.B.**
1. Question No. 1 is compulsory.
 2. Attempt any three out of remaining five questions.
 3. Figures to right indicate full marks.
1. Solve any **Four** : 20
 - a. Explain weighted codes.
 - b. Design a half subtractor using only NAND gates.
 - c. Why Excess-3 is called a self complementing code?
 - d. State and prove De-Morgan's theorems.
 - e. Explain with respect to Flip-Flop:-
 - i. Level triggering
 - ii. Edge triggering
 2.
 - a. Design a binary ($B_3 B_2 B_1 B_0$) to gray ($G_3 G_2 G_1 G_0$) code converter. 10
 - b. What is shaft position encoding? 05
 - c. Derive characteristic equation of J-K Flip-Flop. 05
 3.
 - a. Design a 3-bit MOD-5 asynchronous counter using Flip Flops. 10
 - b. What are the different logic families? & explain salient features of the TTL logic family. 10
 4.
 - a. Design the following gates:- 10
 - i. NOR using NAND
 - ii. NAND using NOR
 - b. Explain bidirectional shift register. 05
 - c. Explain 5 & 6 variable K-Maps. 05
 5.
 - a. Explain operation of 1:8 demultiplexer 05
 - b. Show that : 05

$$A\bar{B}C + B + B\bar{D} + AB\bar{D} + \bar{A}C = B + C$$
 - c. Draw BCD subtractor using 7483 05
 - d. What are the hazards in combinational circuits? 05
 6. Write short notes on any **Four** : 20
 - a. Hamming code
 - b. 3 bit odd parity generator
 - c. Standard and nonstandard SOP & POS forms.
 - d. Counter ICs
 - e. Quine McClusky's technique.
