

8/06/15

S.E. Biomed IV

8/6/15

Logic ~~at~~ Circuit.

(B) (21)

BM/IV/CBGS/LC

Q.P. Code : 3585

(3 Hours)

[Total Marks : 80

- N.B. : (1) Question No. 1 is compulsory.
 (2) Attempt any three questions out of remaining five.
 (3) Assume suitable data if necessary, stating your assumption.

1. Solve any four.

- (a) Explain reflective codes with example.
 (b) Explain using boolean laws & implement using logic gates

$$y = \overline{AB} (B + C) + AB (\overline{B + C})$$

 (c) Design half subtracter using NAND gates.
 (d) Convert JK FlipFlop to T FlipFlop.
 (e) Explain with respect to FlipFlop.
 (i) Level triggering
 (ii) Edge triggering

20

2. Reduce the following function using Quine Mcclusky method implement using NAND gates. 20

$$Y = f(A, B, C, D) = \sum m (0, 1, 4, 5, 6, 7, 9, 10, 15) + d (11, 14)$$

3. (a) Design a 2 bit magnitude comparator compare (A_1, A_0) with (B_1, B_0) 10
 (b) Explain bidirectional shift register. 5
 (c) What is Shaft position encoding. 5

- 4 (a) Convert JK FlipFlop to
 (i) T FlipFlop 3
 (ii) D FlipFlop 3
 (iii) Mn FlipFlop with following truth table 4

M	N	Q_{N+1}
0	0	0
0	1	Q_n
1	0	$\overline{Q_n}$
1	1	1

[TURN OVER

Q.P. Code : 3585

2

- (b) Implement following Function using 8 : 1 multiplexer
 $f = \Sigma m (2, 3, 6, 9, 10, 11, 14, 15)$ 10
5. (a) Draw & Explain 2 input TTL NAND gate. 5
(b) Design a 3 bit MOD 5 asynchronous counter using Flipflop 10
(c) Explain 5 & 6 variable k maps. 5
6. (a) Write a short note on decoder. 5
(b) What is Hamming code. Explain with example. 5
(c) What is ASCII code ? 5
(d) Reduce the following & implement using NAND gates 5
 $f(A, B, C) = \Pi M (1, 2, 4, 7)$
-