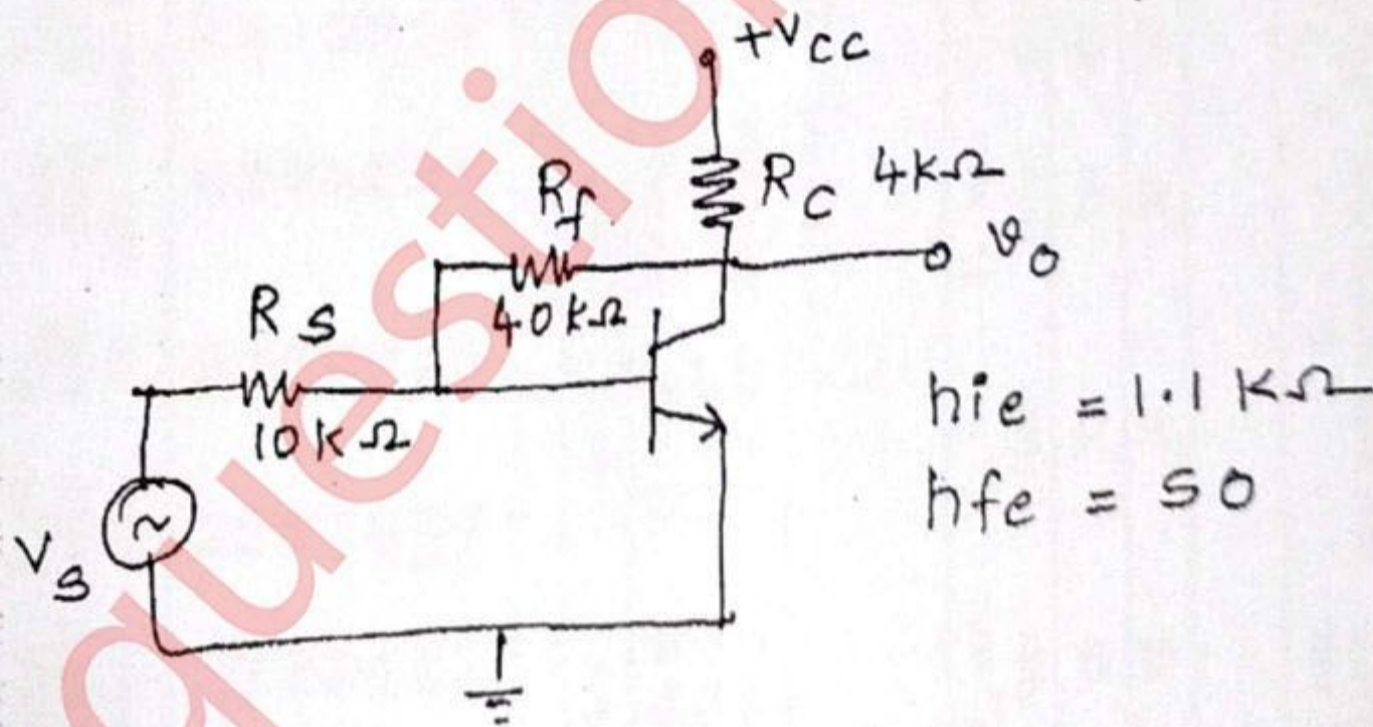


Please check whether you have got the right question paper.

- N.B:
1. Question no one is compulsory.
 2. Attempt any three questions from the following.
 3. Assume suitable data wherever necessary.

- Q.1
- a) Give characteristics of negative feedback. (05)
 - b) Design RC-phase shift oscillator for 10 kHz frequency. (05)
 - c) Compare class-A, class-B and class-C of power amplifier. (05)
 - d) Draw and explain block diagram of op-amp. (05)
- Q.2
- a) Derive expression of gain for instrumentation amplifier and design it for variable gain from 2 to 300. (10)
 - b) Describe working of precision full wave rectifier using op-amp. Draw input-output waveforms (10)
- Q.3
- a) Calculate A_{v_f} , R_{in_f} and R'_{of} . (12)



- b) Give Barkhausen's criteria for oscillations. Derive expression for resonant frequency for Hartley osc. (08)
- Q.4
- a) Draw class-B push pull power amplifier and discuss its working. Derive expression for power dissipation in transistor, efficiency and figure of merit. Also, give its demerits. (10)
 - b) Design circuit using op-amp to satisfy following equation. (10)
- $$V_0 = -100 \int (v_a + 2v_b - 4v_c - 3v_d) dt.$$

21

- Q.5 a) Derive equations for A_d , A_c , CMRR, R_{in} and R_o for Dual Input Unbalanced Output Differential Amplifier. Calculate their values if supply = $\pm 13V$, $R_s = 1K\Omega$, $R_c = 2.7K\Omega$, $R_E = 7.6 K\Omega$, $h_{fe} = 120$, $V_{BE} = 0.6V$.
- b) Discuss working of clamper using op-amp.

- Q.6 a) Design class – A transformer coupled power amplifier for $P_L = 3W$, $R_L = 3\Omega$, $V_{CC} = 18V$, $S \leq 10$.
- b) Design differentiator that will differentiate an input signal with $f_{max} = 100Hz$. Draw the output waveform if the input is sinewave of 1V peak at 100Hz

S. B. (BioMed) / Sem IV / Choice based

3

DBEC DATA SHEET

Transistor type	P _{dm} max @ 25°C Watts	I _{cm} max @ 25°C Amps	V _{ce} min volts	V _{ce} min d.c.	V _{ce0} volts	V _{ce0} (SWS) volts d.c.	V _{ce0} (SWS) volts d.c.	V _{ce0} volts d.c.	V _{ago} volts	T _j max °C	D.C. current		Small signal	h _{fe}	V _{as} max.	
											min	typ.				min.
2N3055	115-5	15-0	1-1	100	60	70	90	7	200	20	50	70	15	50	120	1-8
ECN055	50-0	5-0	1-0	60	50	55	60	5	200	25	50	100	25	75	125	1-5
ECN149	30-0	4-0	1-0	50	40	—	—	8	150	30	50	110	33	60	115	1-2
ECN100	5-0	0-7	0-6	70	60	65	—	6	200	50	90	280	50	90	280	0-9
BC147A	0-25	0-1	0-25	50	45	50	—	6	125	115	180	220	125	220	260	0-9
2N525(PNP)	0-225	0-5	0-25	85	30	—	—	—	100	35	—	65	—	45	—	—
BC147B	0-25	0-1	0-25	50	45	50	—	6	125	200	290	450	240	330	500	0-9

BFW 11—JFET MUTUAL CHARACTERISTICS

-V _{as} volts	I _{os} max. mA	I _{os} typ. mA	I _{os} min. mA	Derate above 25°C													
				0-0	0-2	0-4	0-6	0-8	1-0	1-2	1-6	2-0	2-4	2-5	3-0		
10	9-0	6-8	4-0	7-6	6-1	5-4	4-2	3-1	2-2	2-0	1-1	—	—	—	—	—	—
7-0	6-0	4-0	3-3	4-6	3-3	2-7	1-7	0-8	0-2	0-0	0-0	0-0	0-0	0-0	0-0	0-0	0-0
4-0	3-0	2-2	1-6	1-6	1-0	0-5	0-0	0-0	0-0	0-0	0-0	0-0	0-0	0-0	0-0	0-0	0-0

N-Channel JFET

Type	V _{as} max. Volts	V _{oo} max. Volts	V _{as} max. Volts	P _d max. @25°C	I _{os}	g _m	-V _p Volts	r _d	Derate above 25°C
2N3822	50	50	50	300 mW	2 mA	3000 μΩ	6	50 KΩ	2 mW/°C
BFW 11 (typical)	30	30	30	300 mW	7 mA	5000 μΩ	2-5	50 KΩ	—

UJT type	P _d max. @25°C	I _g max. @25°C	I _p peak pulse current	V _{as} Volts max.	T _j max	η	r _{th(j-c)}	I _p max. μA			
2N2646	300mW	50mA	2Amp.	30	125°C	0-56	0-75	4-7	7-0	9-1	5-0