

SE/SemTV / Biomed. / Choice Based / LIC
 23/5/18
 Linear Integrated Circuits

(1)

(18)

Q.P. Code : 37585


[Time: Three Hours]

[Marks: 20]

Please check whether you have got the right question paper.

- N.B: 1) Q.1 is compulsory.
 2) Attempt any three questions from remaining five questions.
 3) Assume suitable data if necessary.

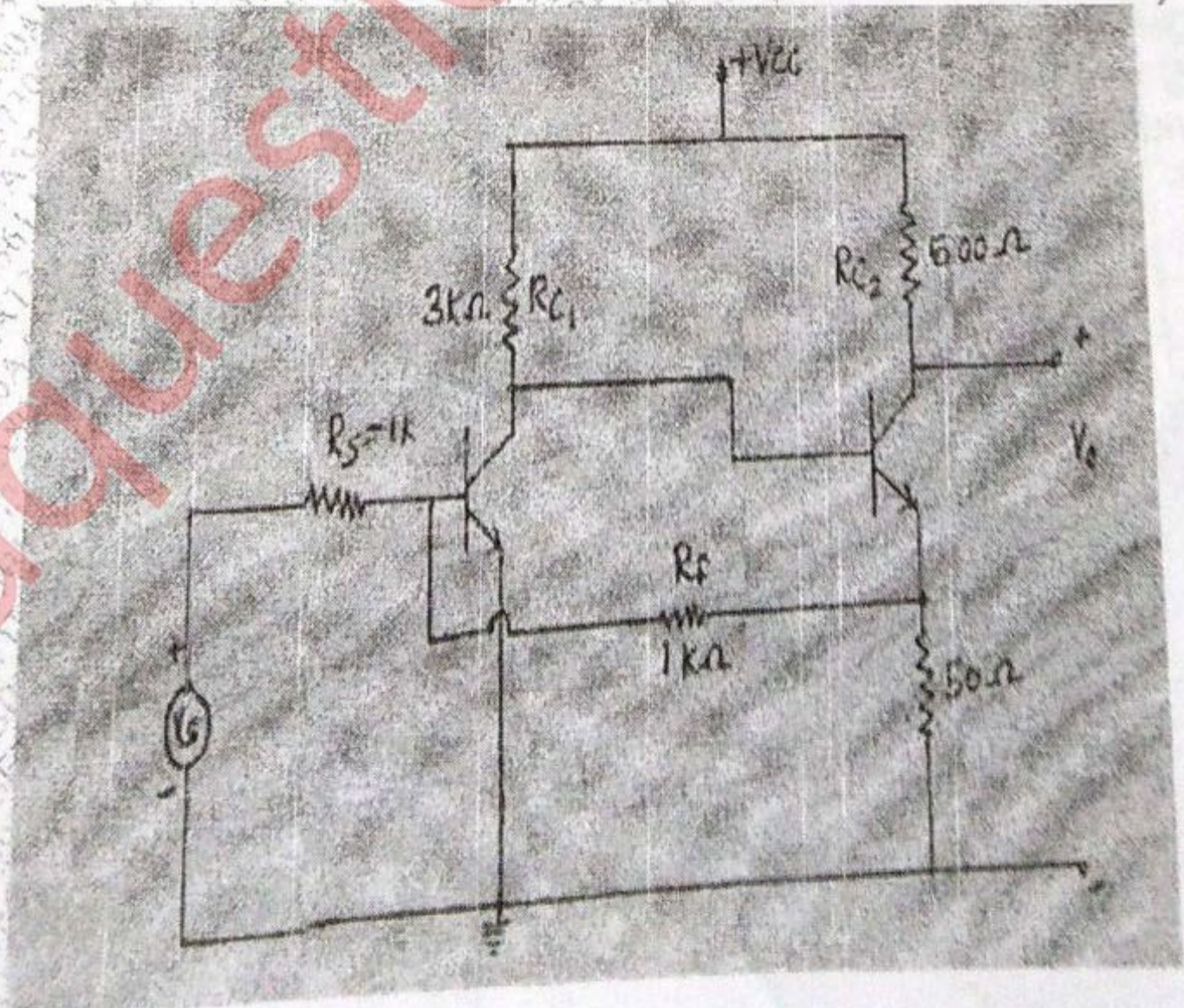- Q.1
- a. Explain working of class C amplifier 05
 - b. Explain current mirror circuit used in differential amplifier. 05
 - c. Compare voltage series and voltage shunt feedback configurations. 05
 - d. A 50 KHz square wave is to be amplified by an op-amp to have an output voltage swing of ± 10 V. 05
 Two op-amps are available.
 i) μA 741 which has slew rate of $0.5V/\mu s$
 ii) TL081 with S.R. of $13V/\mu s$.
 Determine the suitability of the op-amp.
- Q.2
- a. Design a class A transformer coupled power amplifier for the following requirements. 10
 Output ac power = 5W, Dc supply voltage = 12V, Load resistance = 12Ω , $S_{lco} \leq 8$
 Calculate overall efficiency at full load.
 - b. Design a circuit using op-amp for the equation $V_o = -2V_1 - 4V_2 - 6V_3$ 05
 - c. Explain sample and hold circuit using op-amp. 05
- Q.3
- a. For the circuit shown in figure using negative feedback approach. Determine A_{vf} , R_{if} & R_{of} . 10



S.E / sem IV / Biomed. / Choice Based / LIC

23/5/18

Q.P. Code : 37585

- b. In an Integrator circuit $R_1 = 500 \Omega$, $R_f = 5k$, $C = 0.1 \mu F$. If input signal period is $T = 0.5 \text{ ms}$. Then find the frequencies f_a and f_b . Mark those frequencies on Integrator's frequency response. 05
- c. Explain with neat diagram temperature compensated logarithmic amplifier. 05

Q.4 a. Draw and explain working of Wien bridge oscillator. Derive frequency of oscillations and condition for sustained oscillations. 10

b. For a power MOSFET the thermal resistance parameters are as follows:- 05

$$\theta_{dev-case} = 1.5^\circ\text{C/W}, \theta_{case-sink} = 1^\circ\text{C/W}$$

$$\theta_{sink-amb} = 6^\circ\text{C/W}, \theta_{case-amb} = 60^\circ\text{C/W}$$

The ambient temperature is 28°C . The max junction or device temp is 100°C . Determine the max. Power dissipation in the transistor with and without heat sink.

c. Explain advantages of negative feedback used in amplifiers. 05

Q.5 a. Draw neat circuit diagram of 3 op-amp instrumentation amplifier. Derive relation of overall voltage gain. State its specifications and mention its use. 10

b. Explain following terms. 06

1) CMRR 2) Slew rate 3) Input offset voltage.

State its ideal and practical values.

c. Explain peak detector circuit using op-amp. 04

Q.6 a. The following specifications are given for the dual input balanced output differential amplifier of $R_c = 2.2k$, $R_E = 4.7k$, $R_{in1} = R_{in2} = 50 \Omega$, $\pm V_{CC} = 10V$, $\beta_{ac} = \beta_{dc} = 100$, $V_{BE} = 0.715V$. Determine I_{CQ} , V_{CEQ} , A_d and A_c . 10

b. Design a circuit using op-amp for the following equation:- 05

$$V_o = \int V_{in} dt.$$

c. With neat diagram explain Schmitt trigger circuit. 05

S.E / Sem IV / Biomed. / Choice Based / LIC
 23/5/18

85

Q.P. Code : 37585

DBEC DATA SHEET

Transistor type	P _{max} Watts @ 25°C	I _{cm} Amps	V _{ce} volts d.c.	V _{ce} volts d.c.	V _{ce} volts d.c.	V _{ce} volts d.c.	V _{ce} volts d.c.	T _j °C	D.C. current gain		Signal		V _{ce} max	θ _{JA} °C/W	Derate above 25°C W/°C
									min	typ.	max.	min.			
2N 3055	115.5	15.0	1.1	100	60	70	90	200	20	50	15	50	1.8	1.5	0.7
ECN 055	50.0	5.0	1.0	60	50	55	60	200	25	50	25	75	1.5	3.5	0.4
ECN 145	30.0	4.0	1.0	50	40	—	—	150	30	50	33	60	1.2	4.0	0.3
ECN 100	5.0	0.7	0.6	70	60	65	50	200	50	250	125	200	0.9	35	0.05
BC147A	0.25	0.1	0.25	50	45	50	—	125	115	180	—	45	—	—	—
2N 525 (PNP)	0.25	0.1	0.25	85	30	—	—	100	35	—	—	500	—	—	—
BC147B	0.25	0.1	0.25	50	45	50	—	125	200	450	240	330	0.9	—	—

BFW 11—JFET MUTUAL CHARACTERISTICS

Transistor type	R _{gs}	R _{gs}	I _{cm}	P _{max}	T _j max.	f _{max}	f _{max}	V _{gs}	V _{gs}	V _{gs}	Derate	
											above 25°C	θ _{JA}
BC 147A	27 K Ω	15 μ U	15 × 10 ⁻⁴	0.4 C/mW	—	—	—	—	—	—	3.0	3.5
2N 525 (PNP)	14 K Ω	25 μ U	32 × 10 ⁻⁴	0.4 C/mW	—	—	—	—	—	—	1.1	0.5
BC 147B	45 K Ω	30 μ U	2 × 10 ⁻⁴	—	—	—	—	—	—	—	0.0	0.0
ECN 100	50 Ω	—	—	—	—	—	—	—	—	—	0.0	0.0
ECN 140	15 Ω	—	—	—	—	—	—	—	—	—	0.0	0.0
ECN 045	12 Ω	—	—	—	—	—	—	—	—	—	0.0	0.0
2N 2055	6 Ω	—	—	—	—	—	—	—	—	—	0.0	0.0

N-Channel JFET	Type	V _{gs} max.	V _{gs} max.	V _{gs} max.	P _{max}	T _j max.	f _{max}	f _{max}	-V _{gs} Volts	T _j	Derate
2N5222	—	50	50	50	500 mW	175°C	2 mA	3000 p U	6	50 K Ω	2 mW/°C
BFW 11 (typical)	—	30	30	30	300 mW	200°C	7 mA	5000 p U	2.5	50 K Ω	0.59° C/mW