

Duration:3 hours

Total marks:80



- N.S.: (1) Question No.1 is compulsory.  
(2) Solve any three from remaining five questions.  
(3) Figures to the right indicate full marks

- Q. 1 Answer the following questions: (20)
- (a) Write the entity declaration in VHDL for NOR gate.
  - (b) Add  $(22)_{10}$  to  $(56)_{10}$  in BCD.
  - (c) Convert decimal 57 into binary, base 7 and Hexadecimal.
  - (d) Construct Hamming code for 1010.
  - (e) Perform subtraction using 2's complement for  $(10)_{10} - (7)_{10}$
  - (f) State and prove De Morgan's law.
  - (g) Convert  $(77)_{10}$  into Excess-3 code.
  - (h) Perform addition of  $(34)_8$  and  $(62)_8$
  - (i) Find 8's complement of the numbers  $(37)_8$  and  $(301)_8$
  - (j) Explain ASCII code in brief.

- Q. 2(a) Simplify the following equation using K map to obtain SOP equation and realize the minimum equation using only NAND gates. (10)  
 $F(A,B,C,D) = \sum m(1,2,4,6,9,10,12,14) + d(3,7,13)$
- (b) Implement full adder using 8:1 mux. (10)

- Q. 3(a) Obtain the minimal expression using QuineMc-Cluskey method (10)  
 $F(A,B,C,D) = \sum m(1,2,3,5,6,10,11,13,14) + d(4,7)$
- (b) What is race around condition? How to overcome it? (10)

- Q. 4(a) Design 3 bit asynchronous counter and draw the timing diagram. (10)
- (b) Convert JK flipflop to SR flipflop and D flipflop. (10)

- Q. 5(a) Compare TTL and CMOS with respect to different parameters. (10)
- (b) Explain the features of VHDL and its modeling styles. (10)

- Q. 6 Write short notes on (any four) (20)
- a) Moore and Mealy machine
  - b) Sequence generator
  - c) Universal shift register
  - d) Priority encoder
  - e) Carry look ahead adder

\*\*\*\*\*