

(Time: 3 Hours)

(Marks:80)

- N.B. (1) Question No. 1 is compulsory  
 (2) Assume suitable data if necessary  
 (3) Attempt any three questions from remaining questions

1 Attempt ant 5

- (a) Convert  $(451.43)_{10}$  into octal, binary and hexadecimal and base 7. (4)  
 (b) Subtract using 1's and 2's complement method  $(73)_{10} - (49)_{10}$  (4)  
 (c) Perform  $(52)_{10} - (68)_{10}$  in BCD using 9's complement. (4)  
 (d) State De Morgan's theorem. Prove OR-AND configuration is equivalent to NOR-NOR configuration. (4)  
 (e) Encode the data bits 111010001 using Hamming code. (4)  
 (f) Explain SOP and POS and solve the following using K-Map  
 $F(A,B,C,D) = \pi M(1,3,5,6,7,10,11) + d(2,4)$  (4)  
 (g) Explain lockout condition. How can it be avoided (4)

2 (a) Reduce equation using Quine McCluskey method and realize circuit using basic gates. (10)

$$F(A,B,C,D) = \sum m(1,5,6,12,13,14) + d(2,4)$$

(b) Design 4-bit BCD subtractor using IC 7483. (10)

3 (a) Implement the following using only one 8:1 Mux. (5)

$$F(A,B,C,D) = \sum m(0,2,4,6,8,10,12,14)$$

(b) Design a Full Subtractor using only NAND gates. (5)

(c) Design a logic circuit to convert 4-bit gray code to its corresponding BCD code. (10)

4(a) Compare different logic families with respect to fan in, fan out, speed, Propagation delay and power dissipation. (5)

(b) Implement 3 bit binary to gray code converter using Decoder. (5)

(c) Explain 4 bit bidirectional shift register. (10)

5 (a) Design mod 13 synchronous counter using T flipflop (10)

(b) Convert SR flipflop to JK flipflop and D flipflop. (10)

6 Write short note on (any four):- (20)

- (a) ALU  
 (b) 3 bit Up/Down Asynchronous Counter  
 (c) Octal to Binary Encoder  
 (d) 4-bit Universal shift register  
 (e) VHDL