

QP Code : 30702

(3 Hours)

[Total Marks : 80

- N.B. (1) Question No. 1 is compulsory
(2) Assume suitable data if necessary
(3) Attempt any three questions from remaining questions

- 1
- (a) Convert $(532.125)_8$ into decimal, binary and hexadecimal. (3)
 - (b) Convert $(47.3)_7$ BCD, Excess-3 and Gray code. (3)
 - (c) Subtract using 1's and 2's complement method $(56)_{10} - (76)_{10}$. (4)
 - (d) Obtain odd parity Hamming code for 1011. (2)
 - (e) Implement Ex-OR gate using NOR gate only. (2)
 - (f) Perform the following operations without changing the base. (4)
 - i) $(314)_8 + (737)_8$
 - ii) $(312.40)_5 + (214.33)_5$
 - (g) State and prove Demorgans theorem. (2)
- 2 (a) Reduce equation using Quine McCluskey method and realize circuit using basic gates. (10)
 $F(A,B,C,D) = \sum m (1, 3, 7, 9, 10, 11, 13, 15)$.
- (b) Design 8 bit BCD adder. (10)
- 3 (a) Design a logic circuit to convert Gray to BCD code. (10)
- (b) Implement the following using only one 8:1 Mux and few gates. (5)
 $F(A,B,C,D) = \sum m (0, 3, 5, 7, 9, 13, 15)$
- (c) Design a full adder circuit using half adders and some gates. (5)
- 4 (a) Compare TTL and CMOS logic. (5)
- (b) Implement Full subtractor using Demultiplexer. (5)
- (c) Explain 4 bit Universal shift register. (10)
- 5 (a) Design mod 5 asynchronous UP counter. (10)
- (b) Convert SR flipflop to JK flipflop and D flipflop. (10)
- 6 Write short note on (any four):- (20)
- (a) VHDL
 - (b) Decade Counter
 - (c) State table
 - (d) 4-bit Magnitude comparator
 - (e) Multivibrators