

(3 Hours)**[Total Marks : 80]**

- N.B.** 1) Question number 1 is compulsory.
 2) Attempt any 3 questions from the remaining 5 questions.
 3) Each question carries 20 marks.
 4) Within a question, each sub-question carries equal marks.
- 1.**
- | | |
|--|----|
| a) Convert $(-124)_{10}$ to its equivalent sign magnitude form. | 02 |
| b) Convert decimal 214.32 into base 7. | 02 |
| c) Add $(7)_{10}$ and $(6)_{10}$ in BCD | 02 |
| d) Simplify $(B+A)(B+D)(A+C)(C+D)$. | 02 |
| e) Construct Hamming code for BCD 0110. Use even parity. | 02 |
| f) Prove that "A positive logic AND operation is equivalent to a negative logic OR operation". | 02 |
| g) List the applications of shift registers. | 02 |
| h) Minimize the following standard POS expression using K-map
$Y = \Pi M(0,2,3,5,7)$ | 03 |
| i) Write the entity declaration construct in VHDL for NOR gate. | 03 |
- 2.**
- | | |
|---|----|
| a) Obtain the minimal expression using Quine-Mc Cluskey method.
$F(A,B,C,D) = \Sigma m(1,5,6,12,13,14) + d(2,4)$ | 10 |
| b) Compare TIL, CMOS and ECL families with respect to gate, voltage level, fan-in, fan-out, propagation delay, power dissipation, speed and noise margin. | 10 |
- 3.**
- | | |
|--|----|
| a) Design a logic circuit to convert BCD to Gray code. | 10 |
| b) Implement the following using 8:1 MUX.
$F(A,B,C,D) = \Sigma m(0,1,3,5,7,10,11,13,14,15)$ | 05 |
| c) Explain Astable multivibrator. | 05 |
- 4**
- | | |
|---|----|
| a) Explain Master-Slave J-K flipflop. | 05 |
| b) Design 1:16 Demultiplexer using 1:4 demultiplexer. | 05 |
| c) Explain Data flow modelling and Behavioural modelling in VHDL. | 10 |

(TURN OVER)

5. a) Convert JK flipflop to SR flipflop and D flipflop. **10**
b) Design mod 12 asynchronous UP counter. **10**
6. Write short note on (any four):-
- a) Ring Counter
 - b) State table
 - c) 2-bit Magnitude comparator
 - d) 3 to 8 line decoder
 - e) Universal shift register
