

28

31.5.14

Electrical / III CBSEES / EDC

QP Code : NP-18613

(3 Hours)

[Total Marks : 80

- N.B.:**
- Q.1 is compulsory.
 - Attempt any 03 questions from remaining questions.
 - Assumed suitable data when necessary.

- Q.1.
- A) What is Zener diode? 05
 - B) What is Thermal Stabilization? 05
 - C) Explain need of biasing in BJT 05
 - D) What is coupling? Name different types. 05
- Q.2
- A) What is feedback amplifier? Name different types and explain any one of them. 10
 - B) Draw and explain N-channel Enhancement MOSFET with the help of suitable diagram and equation. 10
- Q.3.
- A) Draw and explain double ended and balanced output differential amplifier with the help of suitable equations. 10
 - B) Explain the effects of coupling on performance of BJT. 10
- Q.4
- A) Explain RC phase shift oscillator with the help of suitable diagram and equations. 10
 - B) Explain UJT relaxation oscillator with the help of suitable diagram and equations. 10
- Q.5.
- A) Draw and explain N-channel FET with the help of suitable diagram and equations 10
 - B) Derive the expression for voltage gain, current gain, input impedance and output impedance of CE amplifier. 10
- Q.6. A) Write a short note on any TWO. 20
- i) Full wave bridge rectifier with CLC filter.
 - ii) FET differential amplifier
 - iii) h-parameter model.