

N. B.

- (1) Question No. 1 is compulsory.
- (2) Attempt any three questions out of remaining questions.
- (3) Figures to the right indicate full marks.
- (4) Assume suitable data wherever necessary.

1.
 - a) Draw the circuit diagram and phasor diagram of Maxwell's bridge. 05
 - b) Derive the equation for voltage developed 'V' in a piezoelectric crystal in terms of applied pressure 'P'. 05
 - c) Explain with formulas the concepts of 'limiting error', 'relative error' and 'percentage error'. What is the relation between accuracy and error? 05
 - d) Draw the circuit diagram of dual slope integrator type DVM. Also draw all the appropriate waveforms. 05
2.
 - a) Derive the equation for deflecting torque in PMMC type instrument. A PMMC instrument has a 0.2 Tesla magnetic flux density in its air gaps. The coil dimensions are diameter = 2.5 cm and length = 2.5 cm. Determine the minimum number of coil turns required to give a torque of 5 μNm when the coil current is 100 μA . 10
 - b) Write down the advantages and disadvantages of thermistor. Find the material constant β (in Kelvin) of a NTC thermistor if its resistance at 108°C is 1.87 K Ω and it increases to 1.37 M Ω as the temperature changes to -37°C. 10
3.
 - a) Explain construction and working of Power-factor meter. Draw the necessary diagrams. 10
 - b) Explain the construction and working of dual slope type DVM with proper diagram and waveforms. 10
4.
 - a) Compare Electro-dynamometer type instruments, MI instruments and PMMC instruments. List down the advantages and disadvantages of each. 10
 - b) Explain the construction and working of digital phase meter. Draw the necessary diagrams and waveform. 10
5.
 - a) Derive the expression for deflection ' θ ' in terms of current 'I' for attraction type MI instrument. 10
 - b) Draw the circuit diagram and phasor diagram of Anderson's bridge. Derive the equation for unknown inductance in terms of bridge parameters. 10
6.
 - a) Explain measurement of unknown potential using standard DC potentiometer. 10
 - b) Explain with suitable diagrams measurement of very low, medium and very high impedance measurement using Q meter. Also derive the expression for unknown impedance for each case. 10