

(3 Hours)

[Total Marks : 80

N. B.

- (1) Question No. 1 is compulsory.
- (2) Attempt any three questions out of remaining questions.
- (3) Figures to the right indicate full marks.
- (4) Assume suitable data if necessary.

1. Solve any five :-
  - a) Explain how dc potentiometer measures unknown potential. What enhancement is made in dc potentiometer to convert it in Crompton's potentiometer? 20
  - b) Explain measurement of resistance using Wheatstone's bridge
  - c) What is an instrument transformer? State the types
  - d) Compare RTD, thermistor and thermocouple
  - e) How digital meters are advantageous over analogue meters?
  - f) Short note on - basic Q meter.
2.
  - a) A PMMC instrument with full scale deflection of  $100 \mu\text{A}$  and coil resistance of  $50 \Omega$  is to be converted into a multimeter to measure voltage (0-500V) and current (0-10A). Find the suitable values of shunt and multiplier resistance required. 10
  - b) Justify Hay's bridge is suitable for measuring inductance of high Q coils. Draw its circuit diagram and phasor diagram 10
3.
  - a) Explain systematic, random error and limiting error. Define expression for relative limiting error. 10
  - b) Write a short note on - photo electric transducers 10
4.
  - a) How cold junction and lead compensation is provided for Thermocouple? Also state need for compensation. 10
  - b) Explain with neat diagram 'electrodynamometer type power factor meter'? Show that power factor is proportional to its deflection. 10
5.
  - a) Why synchroscope is required? Explain with neat diagram 'Weston type Synchroscope'? 10
  - b) Explain with neat diagram 'digital energy meter' 10
6. Write a short note on-
  - a) Digital multimeter 07
  - b) Megger 07
  - c) Calibration of voltmeter 06