

(3 Hours)

[ Total Marks : 80

- N. B. :** (1) Question 1 is compulsory.  
 (2) Solve any **three** questions from remaining five questions.  
 (3) **Figures** to the right indicate **full** marks.  
 (4) Assume suitable data if necessary.


1. Attempt the following

- (a) Find the condition of symmetry for Z parameters. 20  
 (b) Define pole and zero of network function and draw p-z plot for

$$V(s) = \frac{4(s+2)}{(s+3)(s^2+4s+5)}$$

- (c) Derive the s-domain equivalent for inductor with initial current  $I_0$  and capacitor with initial voltage  $V_0$ .  
 (d) Define and differentiate with suitable example  
 (i) tree and cotree  
 (ii) graph and oriented graph.

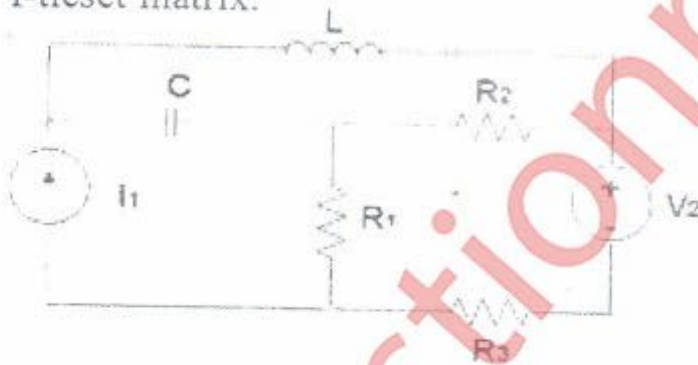2. (a) For the given network draw an oriented graph and write f-cutset and f-tieset matrix. 10




- (b) What will be the value of  $R_L$  to get maximum power delivered to it. What is value of this power. 10



[ TURN OVER

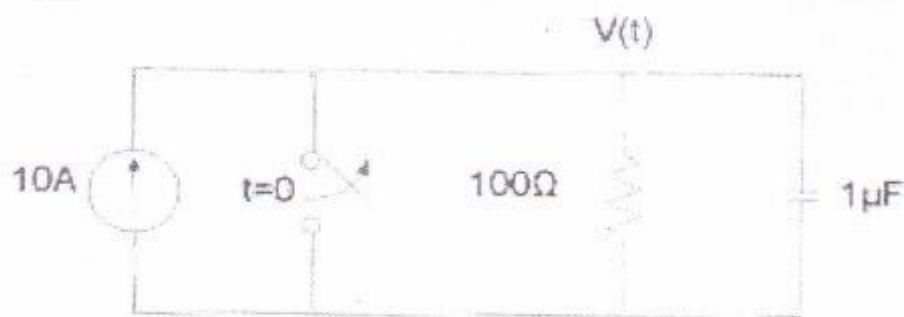3. (a) In the given circuit switch is opened at  $t = 0$ . Find the value of 10

$v, \frac{dv}{dt}, \frac{d^2v}{dt^2}$  at  $t = 0^+$ .




(b) Find  $i(t)$  and  $V_c(t)$  for  $t > 0$  using Laplace transform. 10



4. (a) Find A, B, C, D parameters for the network. 10




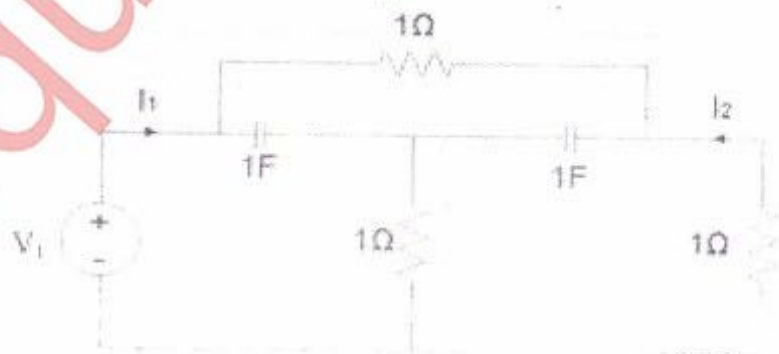(b) Find the driving point admittance  $Y_{11}$  and transfer admittance  $Y_{12}$ . 10



[ TURN OVER

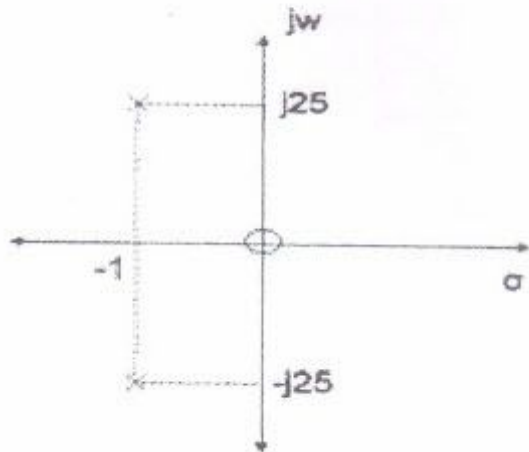5. (a) A series RLC circuit has a scale factor 5 for its driving point admittance and the p-z plot of the same as shown below. Find the values of R, L, C



- (b) Determine Cauer I and Cauer II form of realization of the function

$$Z(s) = \frac{s(s^2 + 2)(s^2 + 5)}{(s^2 + 1)(s^2 + 3)}$$

6. (a) Write the mesh equation for the circuit. Find Y and Z parameters.




- (b) Find the Norton's equivalent across A-B in the figure shown.



[ TURN OVER

(c) Write the mesh equations for circuit

5

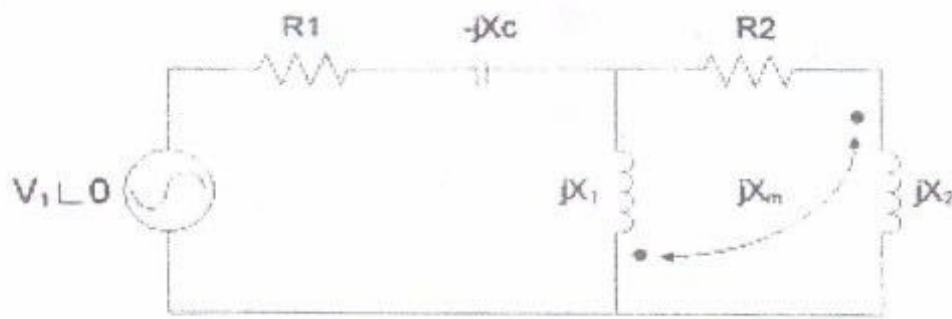

muquestionpapers.com