

Q. P. Code: 24370

(3 Hours)

[Total marks: 80]

N.B:- (1) **Question 1 is compulsory**


- (2) Solve any **three** questions from remaining **five** questions.  
 (3) Figures to the right indicate **full** marks.  
 (4) Assume suitable data if necessary.

Q1 Attempt the following


20

- a) Write short note on duality of network  
 b) Find the condition of reciprocity for Z parameters.  
 c) Write properties of positive real function  
 d) Test whether the polynomial  $s^5 + 3s^3 + 2s$  is Hurwitz.

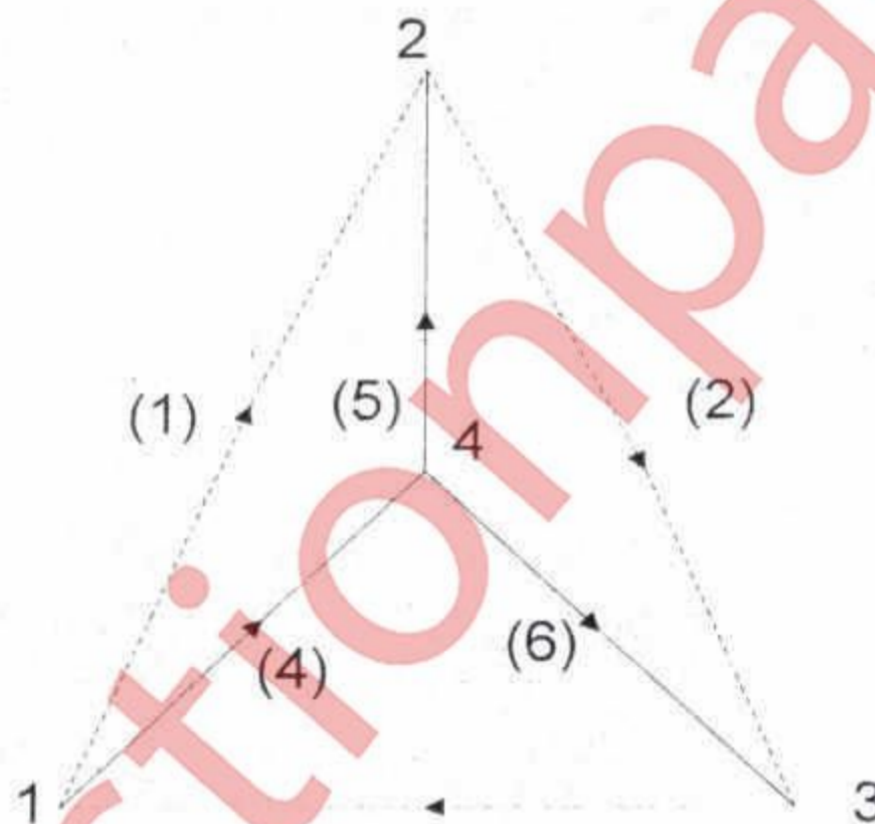
Q2 a) Linear graph of a network is given below. Write f-cutset, f-tieset and incidence matrix. 10



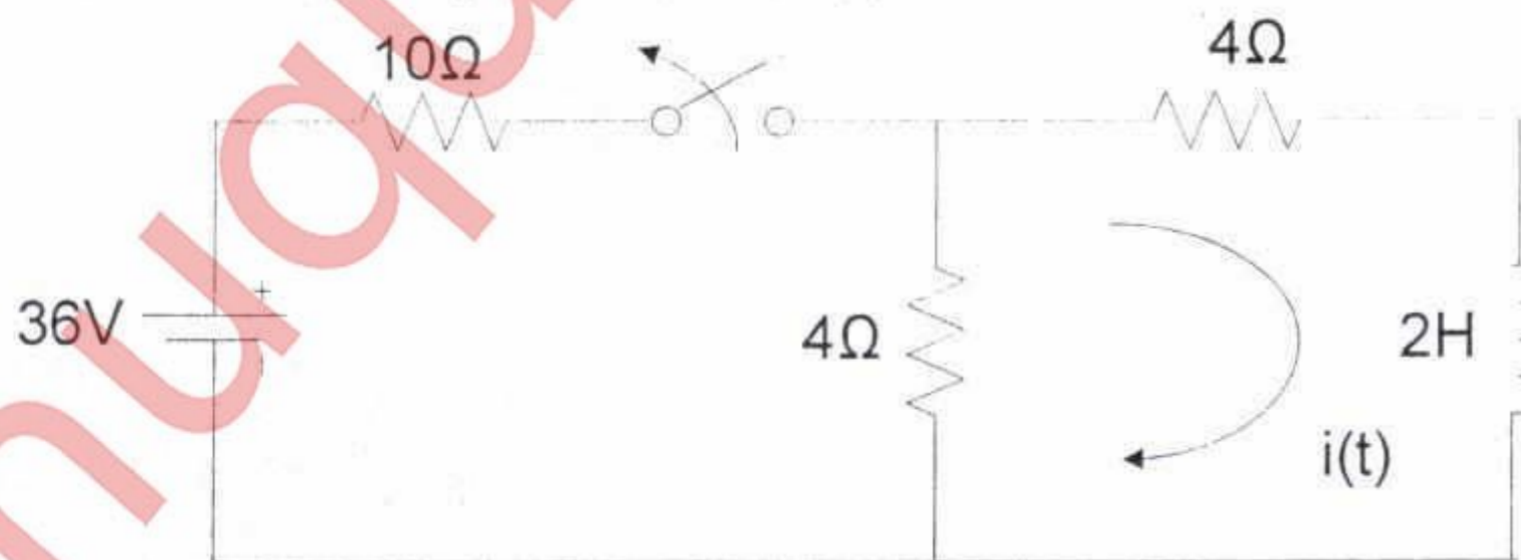
Q2 b) The network shown has acquired steady state with the switch closed for  $t < 0$ . At  $t = 0$ , the switch is opened. Obtain  $i(t)$  for  $t > 0$ . 10



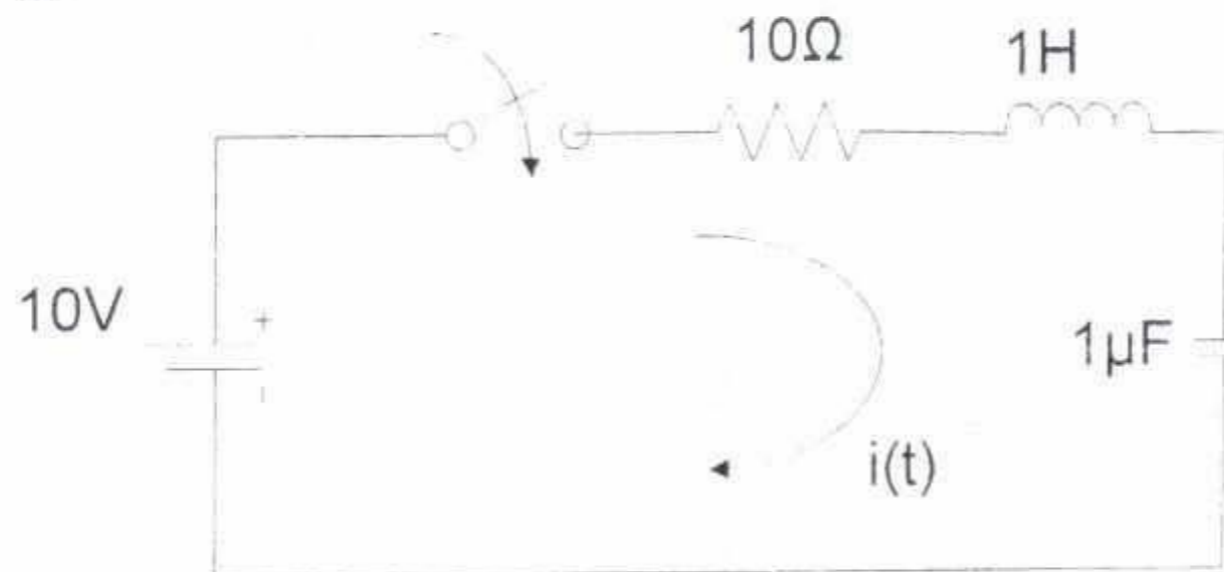
- Q3 a) In the network shown, the switch is closed. Assuming all initial conditions as zero, find  $i$ ,  $\frac{di}{dt}$ ,  $\frac{d^2i}{dt^2}$  at  $t=0^+$ . 10



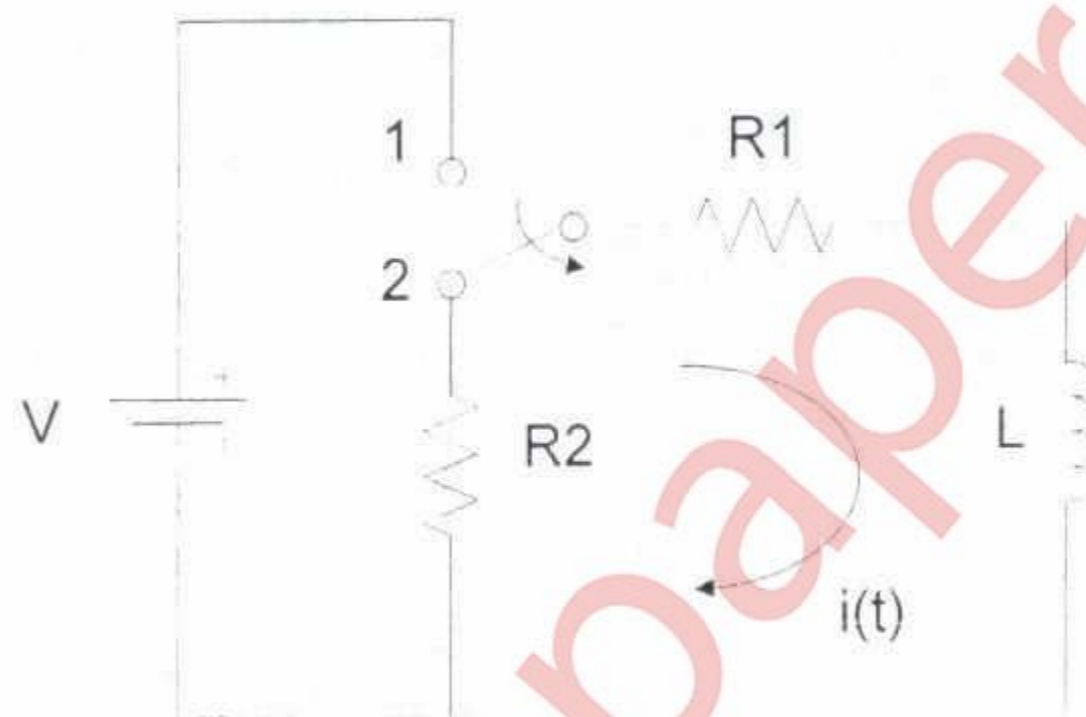- Q3 b) In the network shown, the switch is initially at position 1. On the steady state having reached, the switch is changed to the position 2. Find current  $i(t)$ . 10




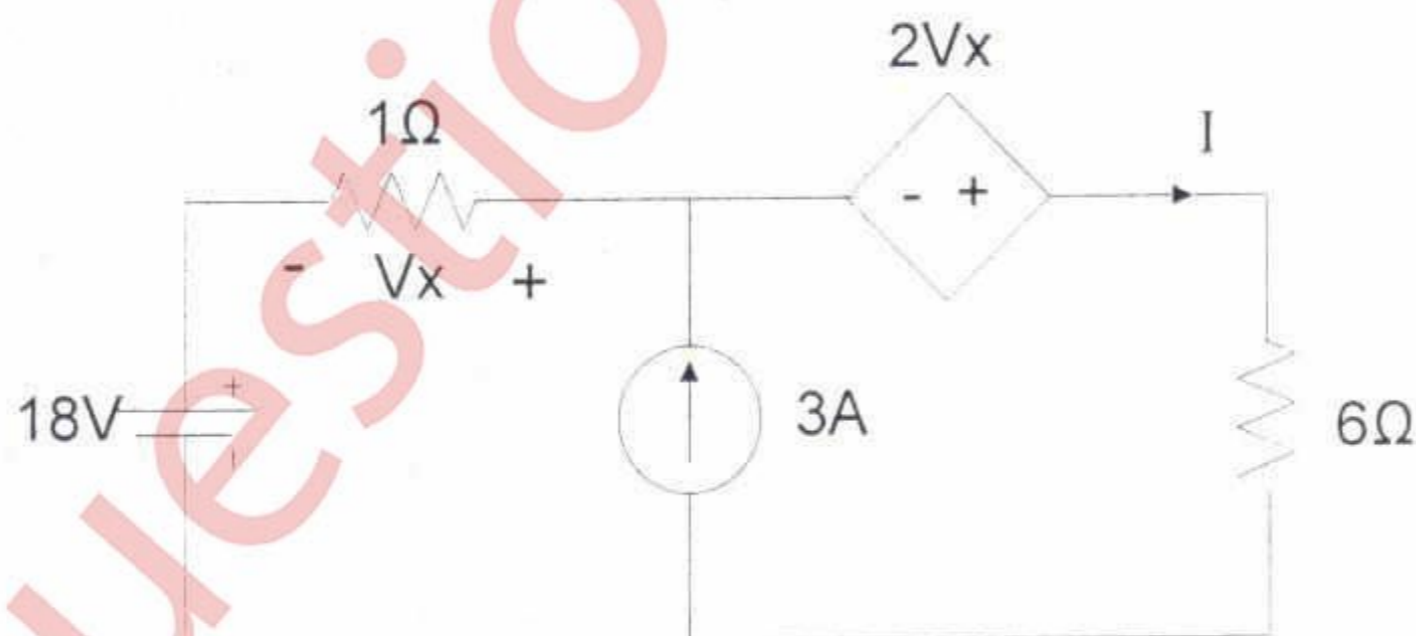- Q4 a) Find the current in the  $6\Omega$  resistor using nodal voltage 10




[TURN OVER]

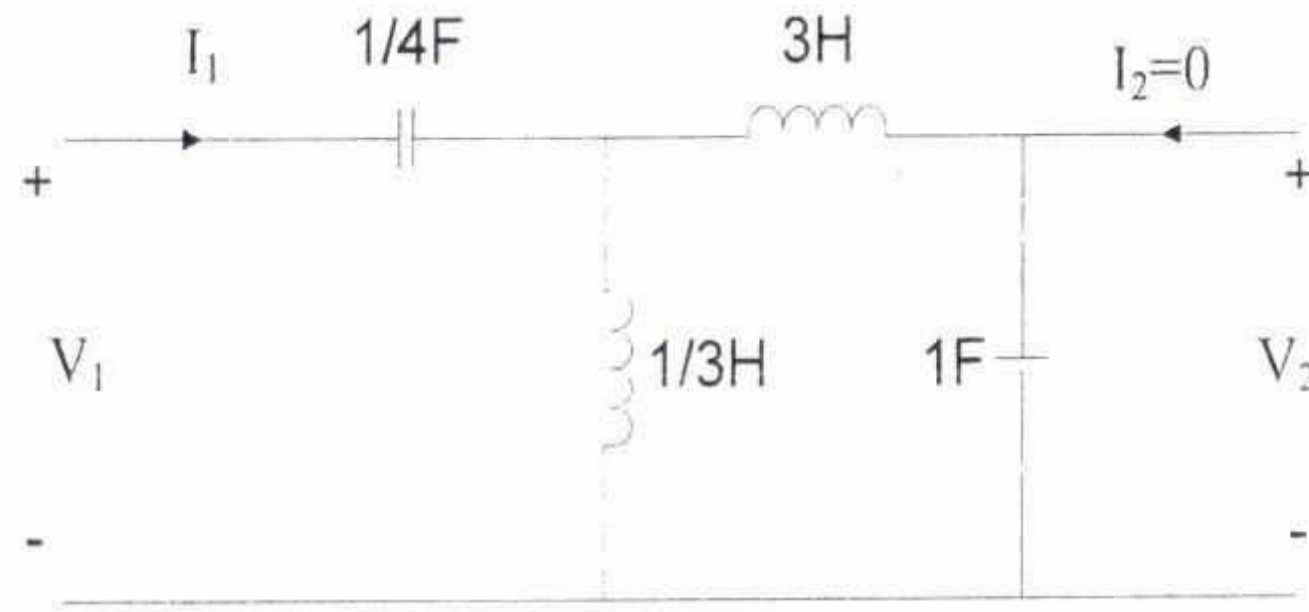Q4 b) Find  $Z_{11}$  and  $G_{12}$  for the following circuit. 10



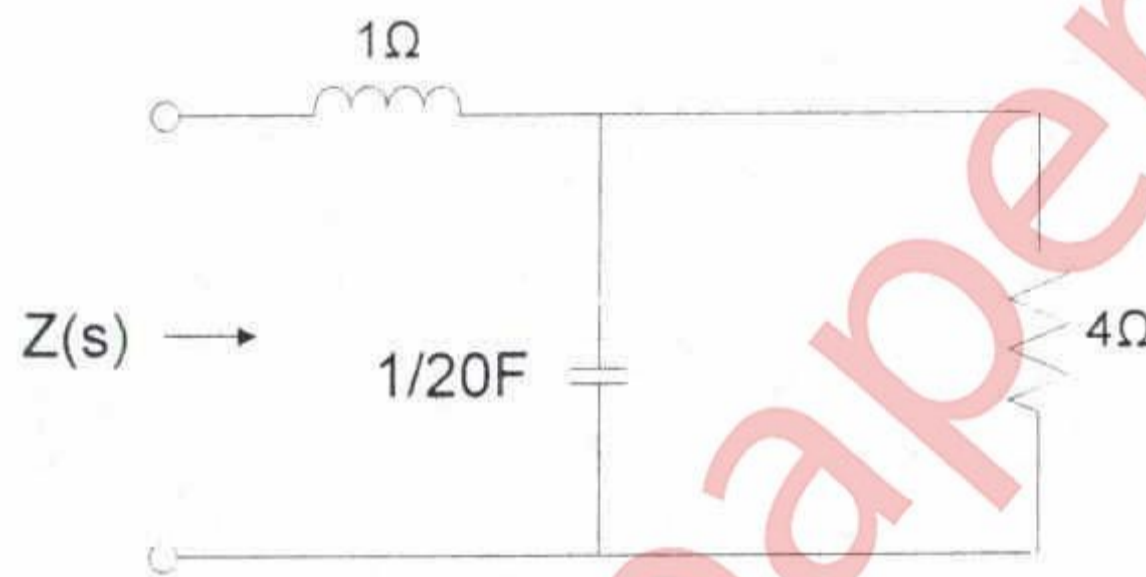
Q5 a) Determine  $Z(s)$  in the network shown. Find out poles and zeros of  $Z(s)$  and plot them on s-plane 10



Q5 b) Realize Cauer I and Cauer II form for following function 10


$$Z(s) = \frac{4(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$$

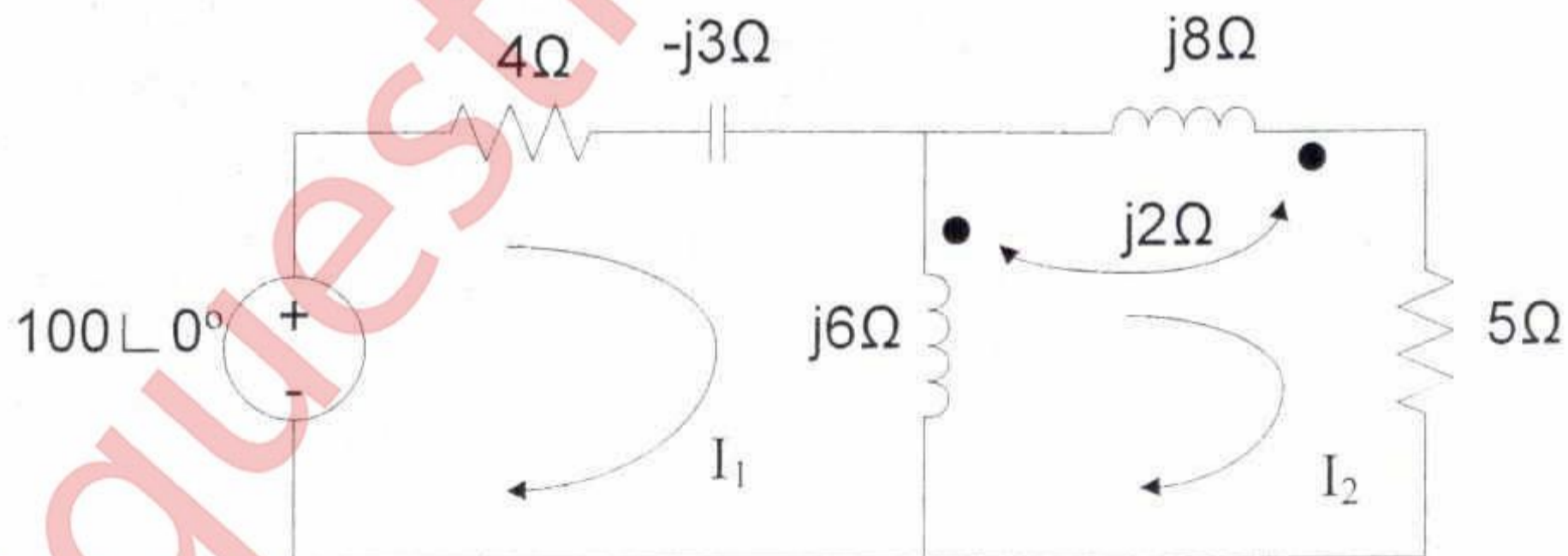Q6 a) Calculate the mesh currents in the circuit shown 10



Q6 b) For the network shown, find Y and Z parameters

10

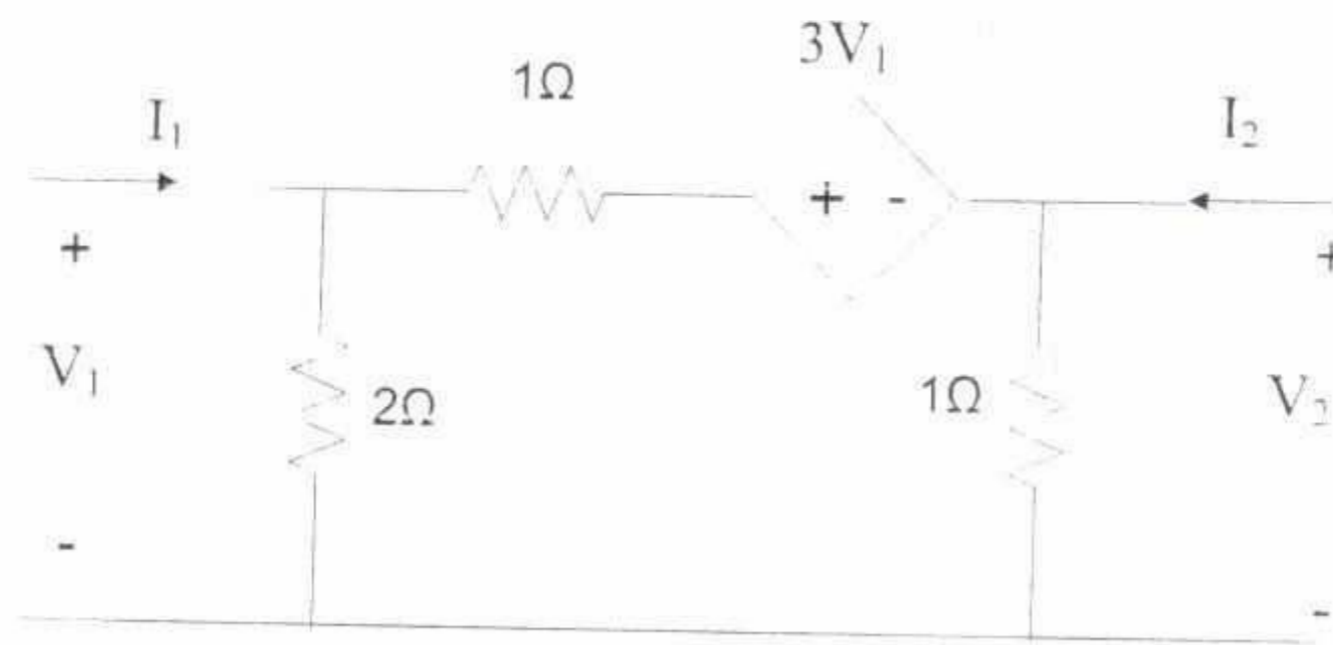

\*\*\*\*\*

muquestionpapers.com

Correction : T1223 / T1485 ELECTRICAL NETWORKS QP Code : 24370



University of Mumbai

---

Correction : T1223 / T1485 ELECTRICAL NETWORKS **QP Code : 24370**  
Question No. 5 a). Inductor value is 1Henry instead of 1ohm in the circuit given

---

University of Mumbai

<https://muapps.in>

[support@muapps.in](mailto:support@muapps.in)

022-26534263 / 022-26534266

Mon-Fri, 10am - 5pm

You have received this email because you are registered with us.

To unsubscribe, please reply to this mail with subject "Unsubscribe"