

(3 Hours)

[Total Marks : 80]


N.B.

- 1) Question No.1 is compulsory.
- 2) Solve any Three questions from question No. 2 To 6.
- 3) Assume suitable data if necessary.


Q1) Solve any Five questions.

[05*04]

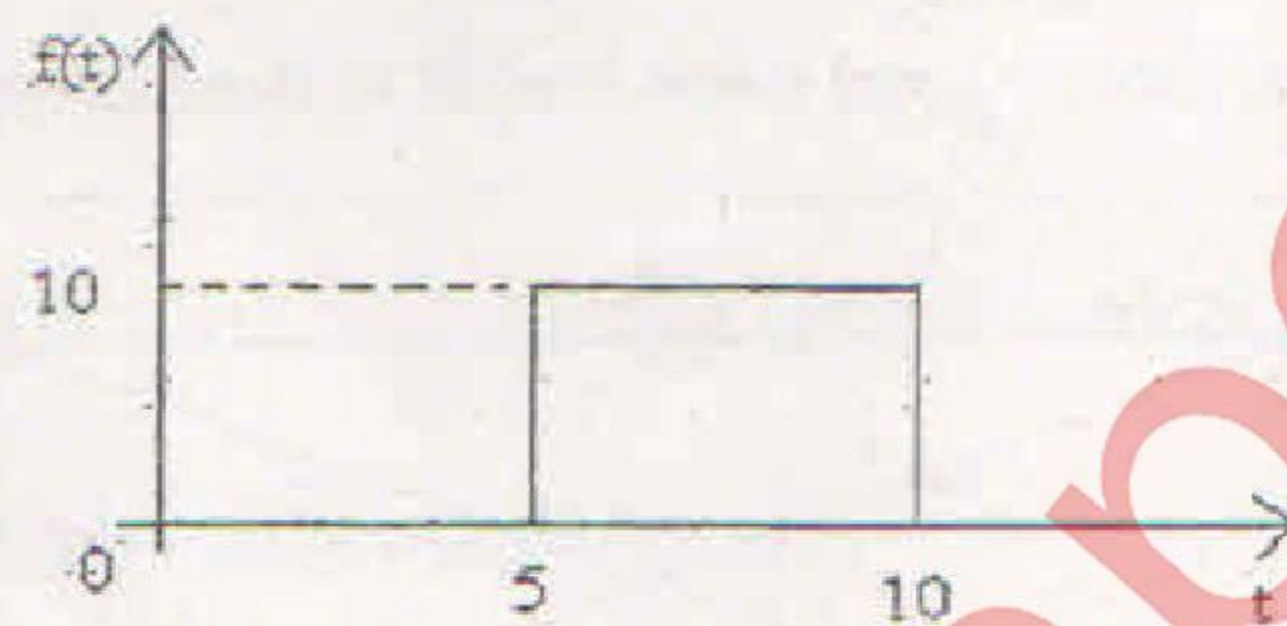- A) Define pole & zero of transfer function & draw P-Z plot for $V(s) = \frac{3(s+3)}{s^2(s+5)}$.
- B) Find the laplace transform of the waveform shown below,



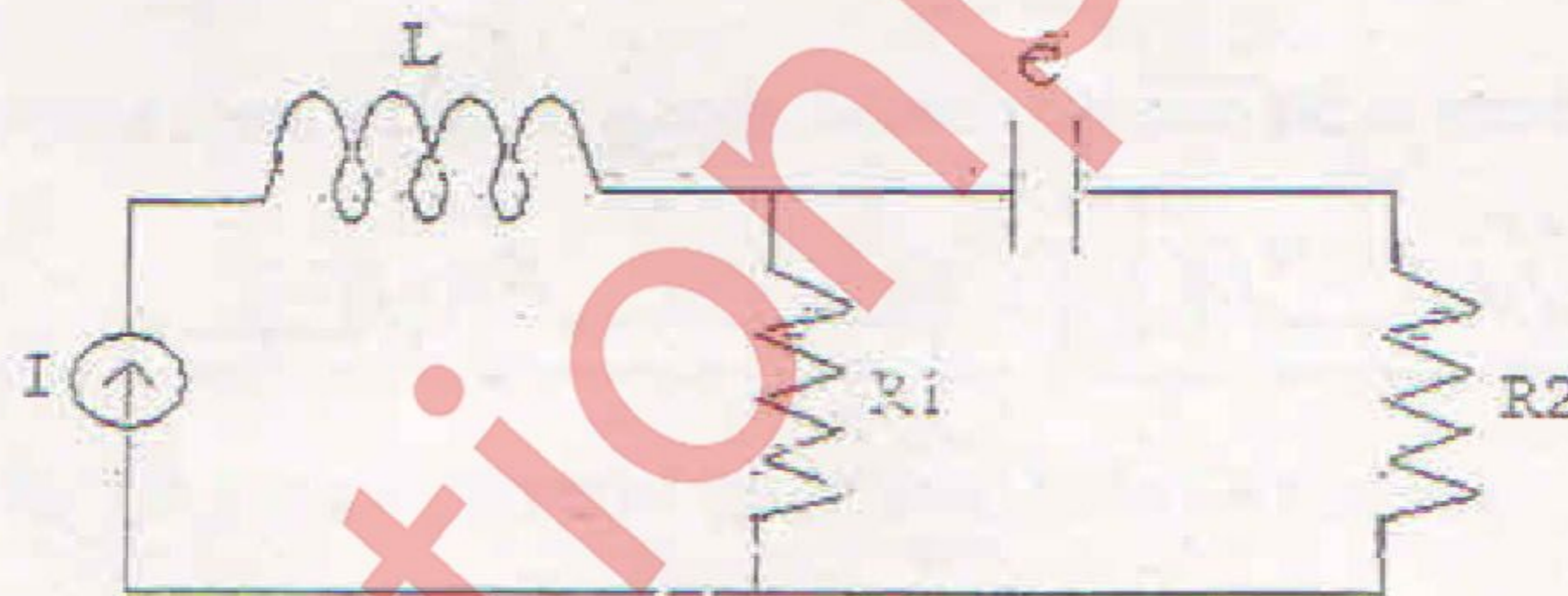
- C) State & explain Millman's theorem.
- D) Find the dual of the given network,



- E) Test whether the following function is Hurwitz polynomial.


$$F(s) = s^4 + 16s^3 + 86s^2 + 176s + 105.$$

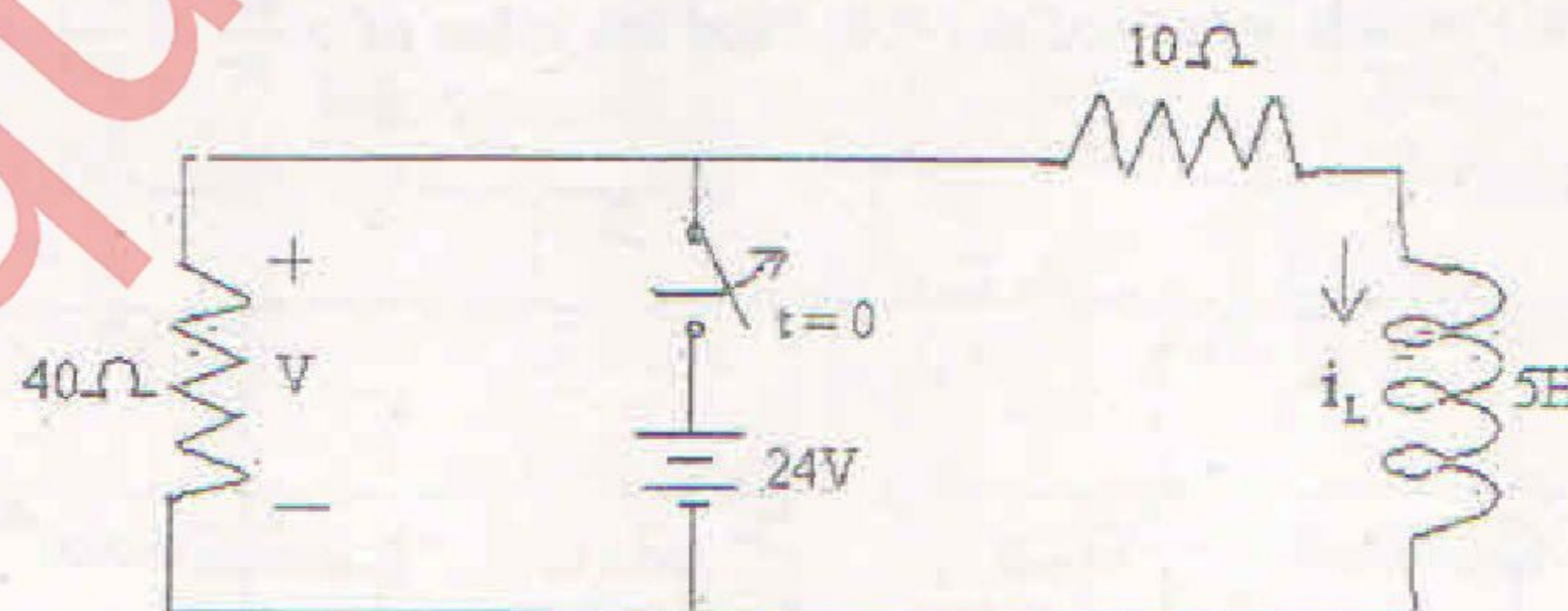- F) Find $i_L(0^+)$ & $V(0^+)$ in the circuit shown below, if switch is opened at $t = 0$.




Q2)

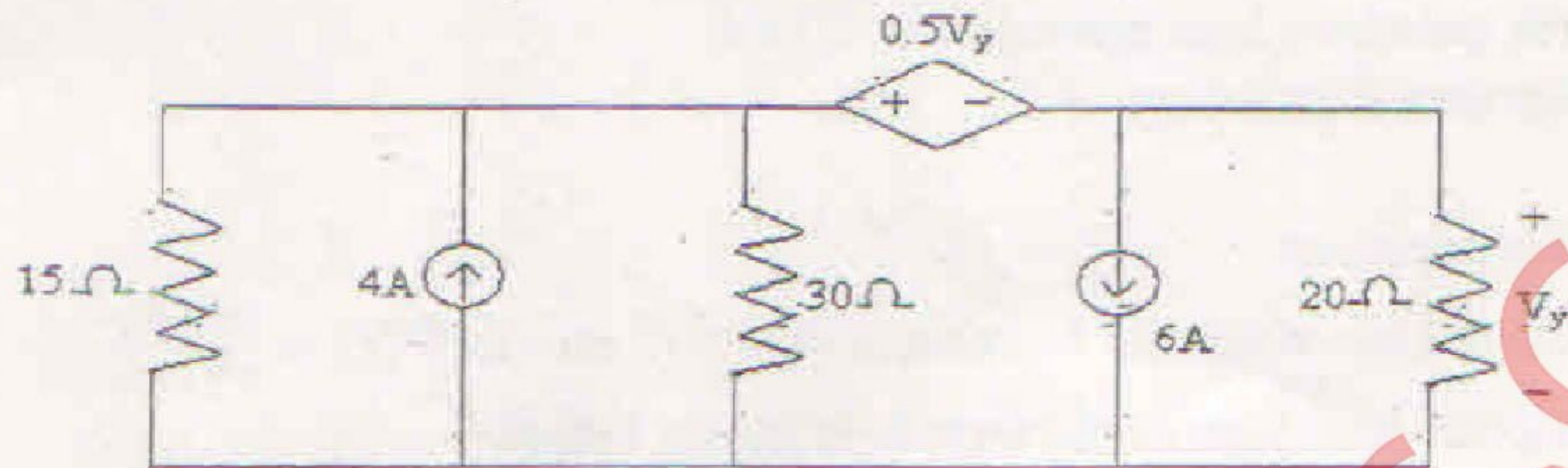A) Use Nodal analysis to find V_y in the circuit shown below, [10]




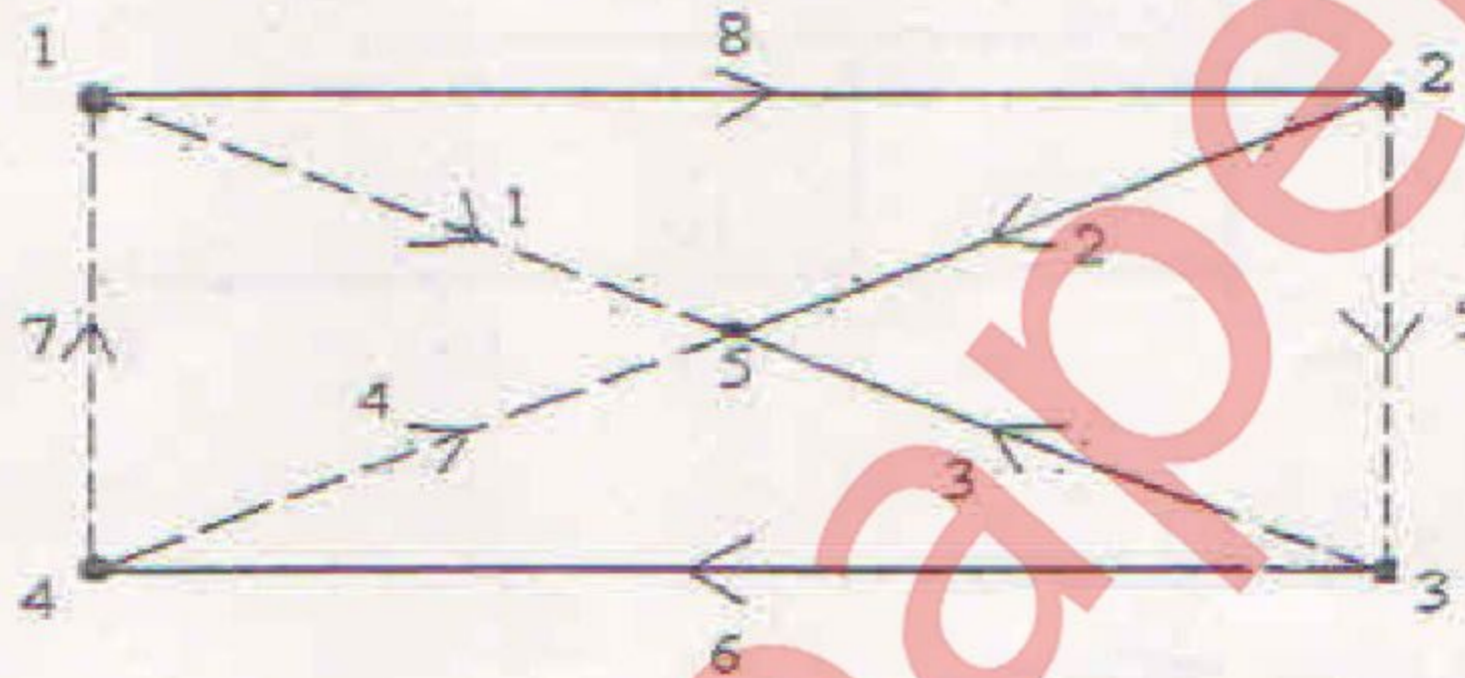B) Write an incidence matrix, fundamental tieset matrix & fundamental cutset matrix for the graph shown below, [10]




Q3)

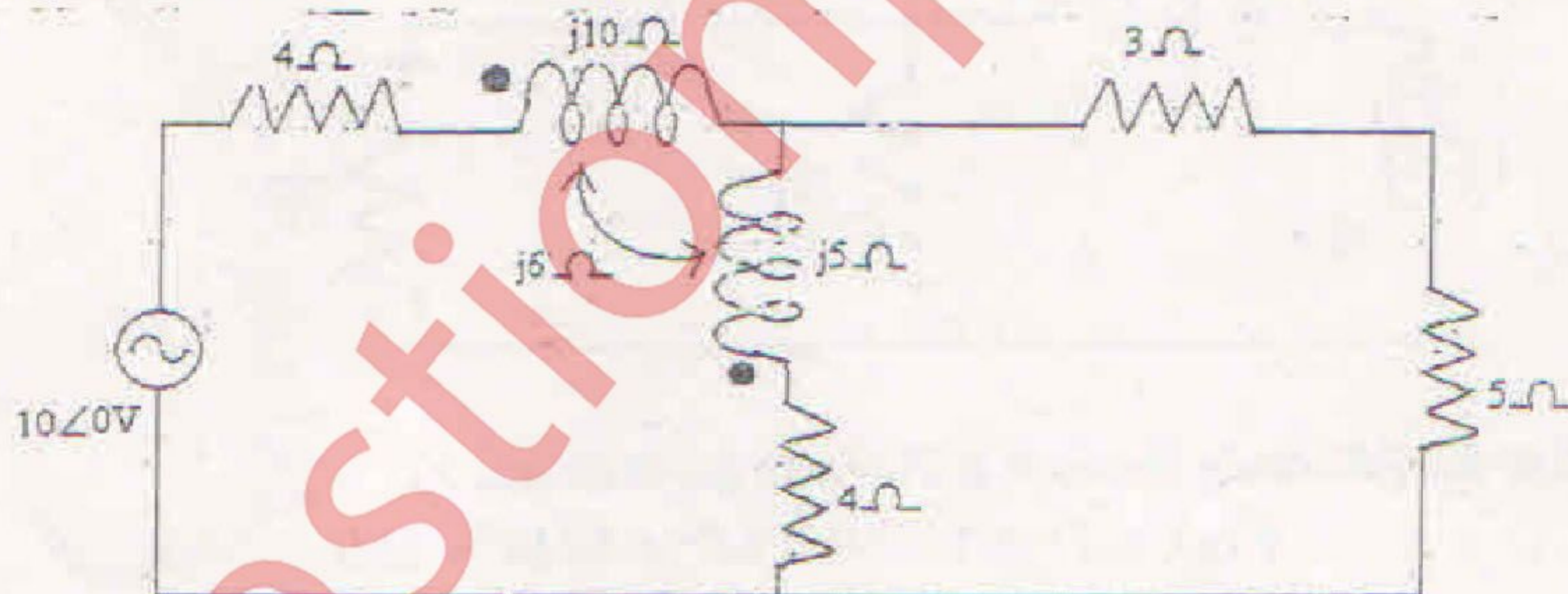
A) Find the loop currents in the coupled network shown below by mesh analysis. [10]



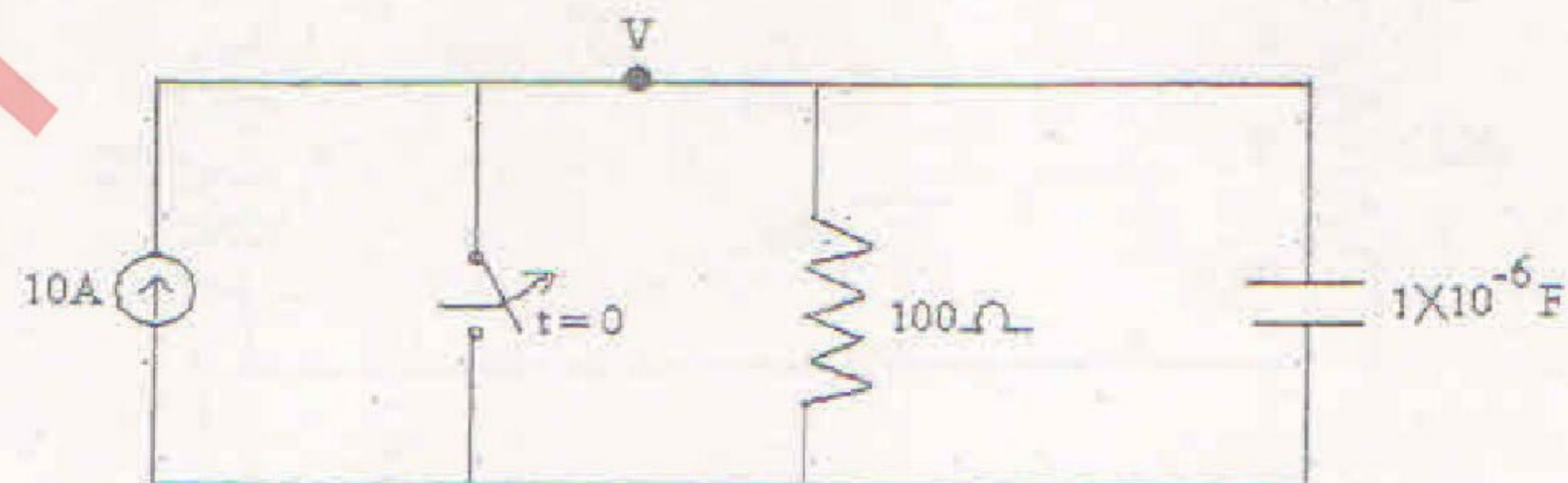B) In the given circuit switch is opened at $t = 0$. Find the value of v , $\frac{dv}{dt}$ & $\frac{d^2v}{dt^2}$ at $t = 0^+$. [10]




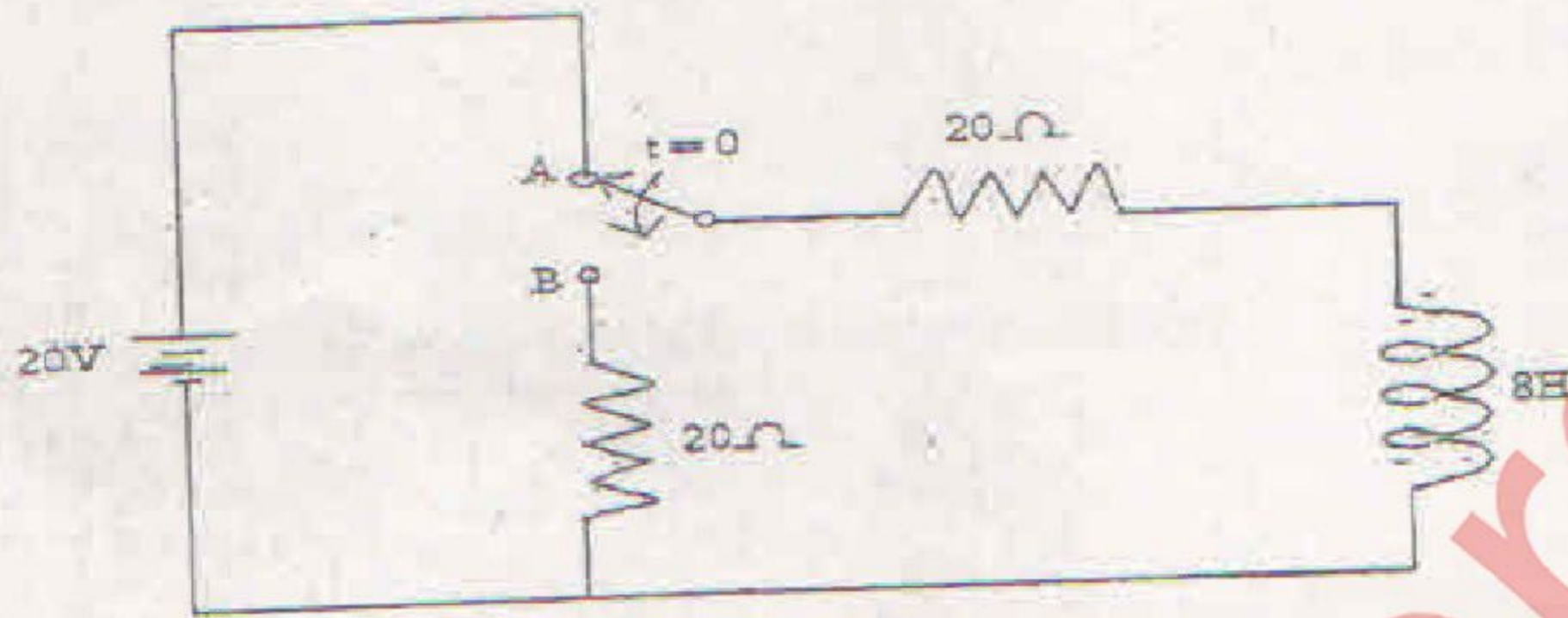- Q4) A) The switch changes its position from "A" to "B" at $t = 0$. Determine current $i(t)$ for $t > 0$ using laplace transform. [10]



- B) Explain Z-parameters & prove the condition for symmetry & reciprocity. [10]

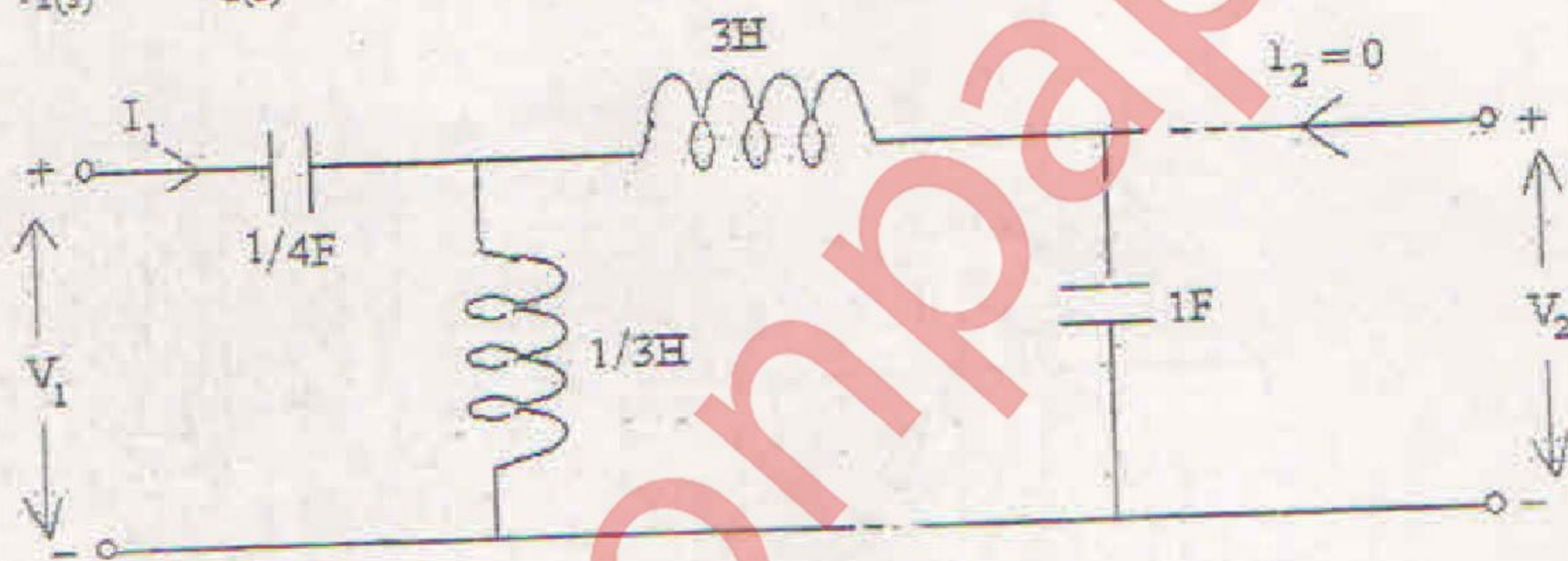
- Q5) A) Find $\frac{V_1(s)}{I_1(s)}$ & $\frac{V_2(s)}{I_2(s)}$ for the circuit shown below, [10]



- B) Find the foster I & foster II forms of the given impedance function. [10]

$$Z(s) = \frac{3(s+2)(s+4)}{s(s+3)}$$

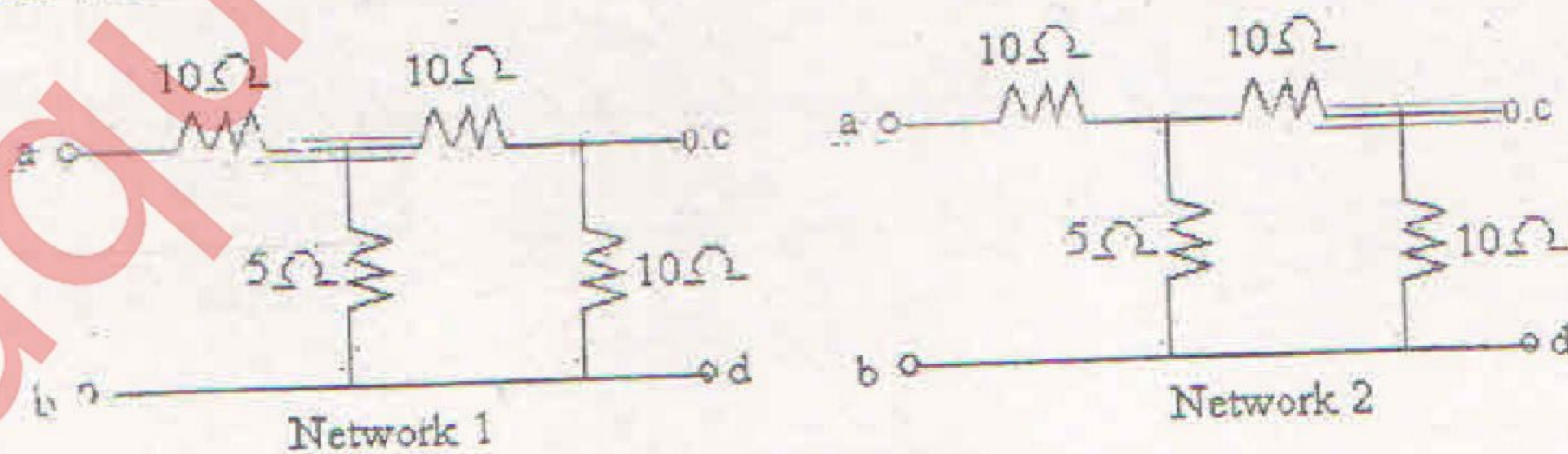- Q6) A) Two networks are shown below; obtain the transmission parameters of the resulting circuit when both circuits are connected in cascade. [12]



- B) Explain the properties of positive real function. [08]