

SE. Electrical IV EBSGS07.6.17  
Q.P. Code : 16094

87

[Time: 3 Hours]

[Marks: 80]

Please check whether you have got the right question paper.

- N.B:
1. Question No.1 is compulsory.
  2. Attempt any Three questions out remaining five questions.
  3. Assume suitable data if necessary and justify the same.

- Q1 Attempt any FOUR:
- a. Discuss the characteristics of ideal op-amp. Compare ideal and practical op-amp.
  - b. Draw and explain the functional block diagram of IC 555.
  - c. Justify "NAND gate is a Universal gate."
  - d. What are shift registers? State its applications.
  - e. State various characteristics of digital ICs.
- Q2. a. Explain the working of practical integrator circuit using op-amp. How it is different from ideal integrator circuit. 10
- b. Draw and explain the working of three op-amp instrumentation amplifier. Derive the expression for its gain. 10
- Q3. a. Derive the expression for the gain of first order low pass filter and draw its frequency response characteristics. 10
- b. Explain operation of monostable multivibrator using IC555. Derive the expression for on time, off time and frequency. 10
- Q4. a. Simplify the following logic expression and realize them using gates 10  
 $F(A,B,C,D) = \pi M (2,8,9,10,11,12,14)$
- b. Design 4-bit Gray to Binary code converter. 10
- Q5. a. Design a synchronous Mod-6 counter using J-K flip-flop. 10
- b. Explain the working of successive approximation A/D converter. 10
- Q.6 Solve any FOUR 20
- a. Convert JK flip top to SR flip flop.
  - b. Implement the following logic function using 8:1 MUX  
 $F(A,B,C,D) = \Sigma m (1,3,4,11,12,13,14,15)$
  - c. Differentiate between combinational and sequential circuits.
  - d. Reduce the expression:  

$$f = A(B + \overline{C})(\overline{AB} + A\overline{C})$$
  - e. i) Convert  $(115)_{10}$  into hexadecimal number.  
 ii) Convert  $(A6F.C9)_{16}$  into Octal number.