

Circuit Theory.

QP Code : 30699


(3 Hours)

[Total Marks : 80

- N. B. : (1) Question No. 1 is compulsory.
 (2) Attempt any **three** questions from remaining questions.
 (3) Use Smith chart wherever required.
 (4) Assume suitable data if required.

1. (a) Test for following polynomial using continued fraction expansion only 20
 $P(s) = s^5 + 12s^4 + 45s^3 + 60s^2 + 44s + 48$
 (b) Obtain transmission parameters (ABCD) in terms of z-parameters.
 (c) List the types of damping in a series R-L-C circuit and mention the condition for each damping.
 (d) Obtain S-domain (Laplace Transform) equivalent circuit diagram of an inductor and capacitor with initial condition.

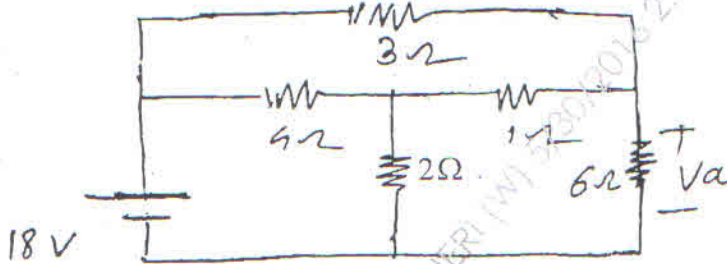
2. (a) Calculate voltage across the resistor 6Ω using source shifting technique. 10



- (b) Compare and obtain Foster-I and Foster-II form using example of RC circuit 10


$$Z(s) = \frac{(s+1)(s+6)}{s(s+4)(s+8)}$$

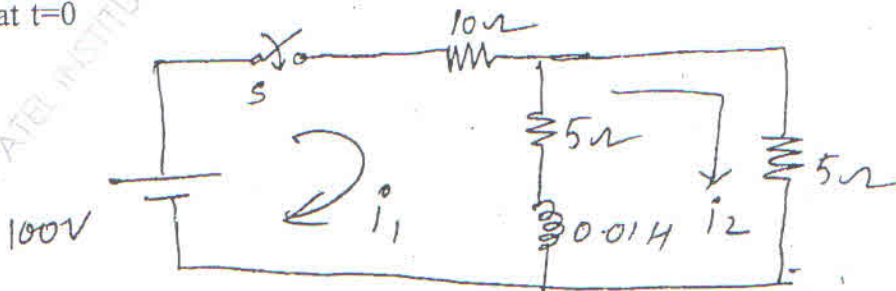3. (a) Design a short circuit shunt stub match for $Z_L = 450 - 600j(\Omega)$. For a line of $Z_0 = 300(\Omega)$ and $f = 20$ MHz. Use Smith chart 10
 (b) In the circuit shown determine current I_1 and I_2 when switch is closed at $t=0$ 10



[TURN OVER

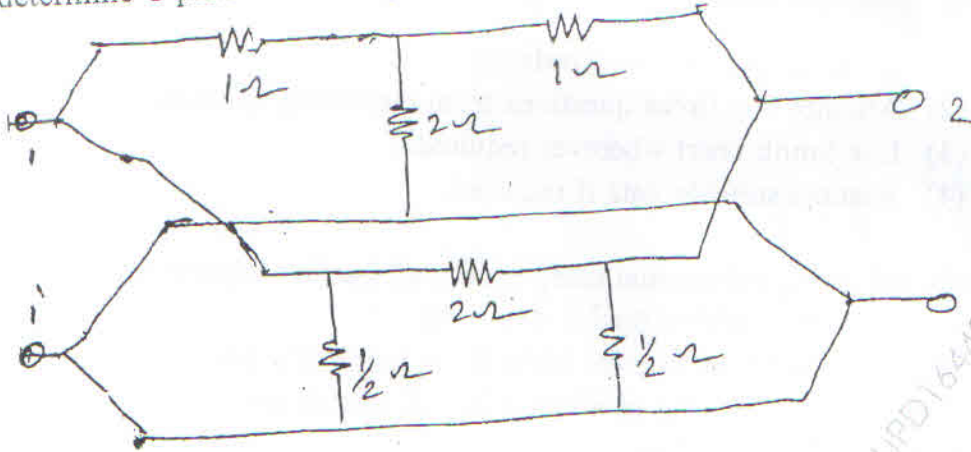4. (a) determine Y-parameter using interconnection of two port networks 10




- (b) Check for positive real function test 5

$$F(s) = \frac{2s^2 + 2s + 1}{s^3 + 2s^2 + s + 2}$$

- (c) Compare Cauer-I and Cauer-II form of LC network 5

$$Z(s) = \frac{2(s^2 + 1)(s^2 + 4)}{s(s^2 + 2)}$$


5. (a) Obtain $i(t)$ for $t > 0$ 10

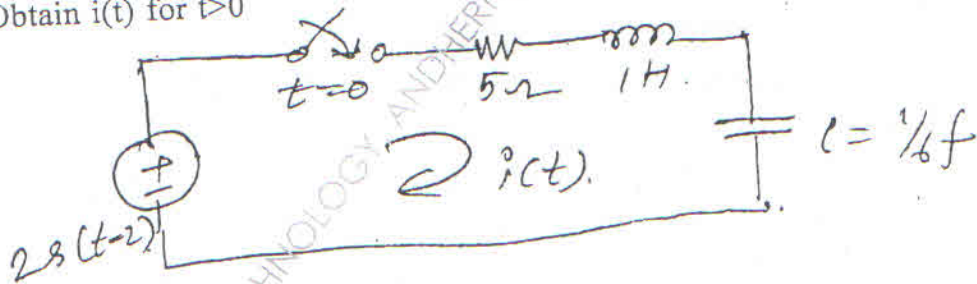

where $r(t)$ is a ramp signal

- (b) Derive an expression for characteristic equation of a transmission line. Also obtain ' α ', ' β ' and ' γ ' of the line. 10

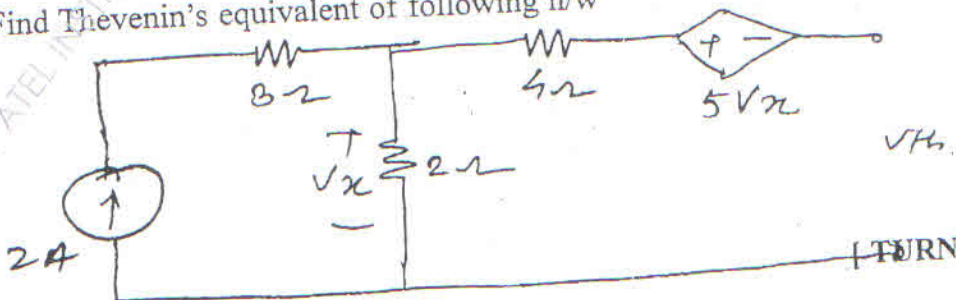
6. (a) Find Thevenin's equivalent of following n/w 8



TURN OVER

- (b) Explain various types of filters.
 (c) Obtain $Z_{11}(s)$, $Z_{21}(s)$, $G_{21}(s)$ for the ladders n/w.

4
8

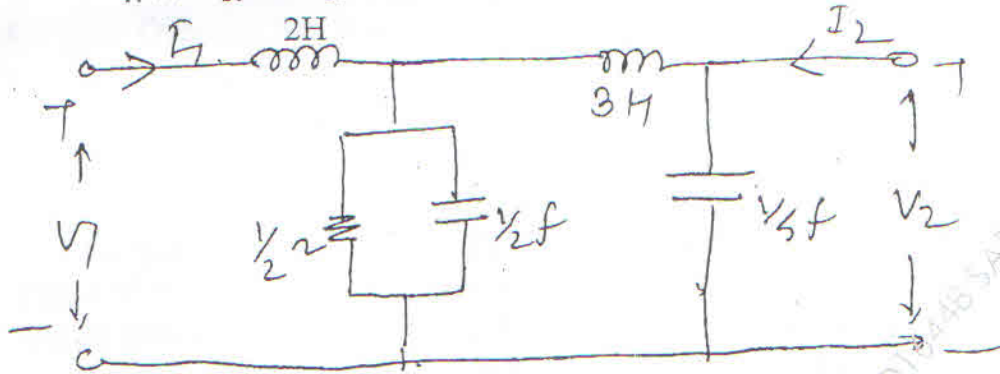

MUPD16448 SARDAR PATEL INSTITUTE OF TECHNOLOGY, ANDHRA (W) 5/30/2016 2:31:01 PM MUPD16448 SARDAR PATEL INSTITUTE OF TECHNOLOGY, ANDHRA (W) 5/30/2016 2:31:01 PM MUPD16448 SARDAR PATEL INSTITUTE OF TECHNOLOGY, ANDHRA (W) 5/30/2016 2:31:01 PM