

Time: 3 Hrs

Marks: 80

- NB:** (1) Question No. 1 is **Compulsory**.
 (2) Attempt any **three** questions out of **remaining five**.
 (3) Each question carries 20 marks and sub-question carry marks.
 (4) Assume suitable data if required.

Q.1 Answer Any Four.

- a) Convert the decimal number $(175.23)_{10}$ to their octal, hexadecimal, BCD and gray code equivalent. **5m**
- b) Prove the following Boolean theorem. **5m**
 $(A+\bar{A}B) = (A+B)$
- c) Implement CMOS inverter and NOR gate. **5m**
- d) Design and implement half subtractor circuit. **5m**
- e) Explain various triggering methods and symbols of flip flops. **5m**

- Q.2** a) Simplify the logic function using Quine-McClusky method. **10m**
 $Y(A, B, C, D) = \sum m(0, 1, 2, 3, 5, 7, 8, 9, 11, 14)$
- b) Design and implement D flip flop using T flip flop and JK flip flop using D flip flop. **10m**

- Q.3** a) Design and implement asynchronous MOD-9 counter using T flip flop. **10m**
- b) Draw and explain 5bit comparator using IC 7485. **10m**

- Q.4** a) Implement and explain 4-bit BCD adder using IC 7483. **10m**
- b) Design and implement the following expression using a single 8:1 multiplexer. **10m**
 $Y(A, B, C, D) = \sum m(0, 2, 3, 6, 8, 9, 12, 14)$

- Q.5** a) Draw and explain master slave JK flip flop with its advantage. Derive characteristics equation and excitation table of JK flip-flop. **10m**
- b) Implement and explain 4-bit twisted ring counter. **10m**

- Q.6** Write a short note on **any three**. **20m**
- a) Hamming code
- b) Characteristics of logic families
- c) Static and dynamic Hazards
- d) Application of flip flop in switch debouncing