 


Please check whether you have got the right question paper.

- N.B:
1. Question No.1 is **Compulsory**
  2. Solve any **three** from the remaining **five** questions.
  3. Draw neat **logic diagram** and assume **suitable data** wherever necessary.

- Q.1**
- a. Two inputs TTL NAND gate **05**
  - b. Explain ring counter **05**
  - c. Draw truth table and logic diagram of Full Subtractor using half Subtractors and gates **05**
  - d. Explain the characteristics parameters of logic families **05**
- Q.2**
- a. Analyze the clocked synchronous machine given below. Write excitation equations, excitation/transition table and state/ output table (Use state names A-D for Q1-Q-2=00-11) **10**



- b. Design 1 digit BCD adder using IC 7483 and perform  $(1010)_{BCD} + (1100)_{BCD}$  **10**
- Q.3**
- a. Design a mealy sequence detector to detect ----0100---- using D flip-Flops and logic gates **10**
  - b. Design a circuit with optimum utilization of PLA to implement the following functions **10**
- $P = \sum m(1,3,8,10,10,15)$   
 $Q = \sum m(0,1,5,7,9,12,14)$   
 $R = \sum m(0,2,5,8,9,11)$
- Q.4**
- a. Implement following function using 4:1 MUX and NAND gates **10**
- $P(A,B,C,D) = \sum m(1,2,6,7,8,10,13,14)$
- b. Explain IC 74194 working in detail with applications **10**
- Q.5**
- a. Use K-map to reduce following function and then implement it by NOR gates. **10**
- $F = \pi M(0,1,4,7,8,11,12,14) + d(2,5,6)$
- b. Eliminate redundant states and draw the reduced state diagram **10**

Present state	Next State		Output Y
	X=0	X=1	
A	B	C	1
B	D	C	0
C	F	E	0
D	E	B	1
E	B	C	1
F	C	E	0
G	F	G	0



- Q.6** Write short notes on any three
1. Master slave JK Flip Flop
  2. Write a VHDL code for full adder
  3. Stuck at '0' and '1' faults
  4. CPLD and FPGA architecture block diagram