

DEC

Q.P. Code : 5313


(3 Hours)

[Total Marks : 80


- N.B. : (1) Question No.1 is compulsory  
 (2) Solve any three questions from remaining questions.  
 (3) Assume suitable data if it is required.

1. Solve any Four questions :

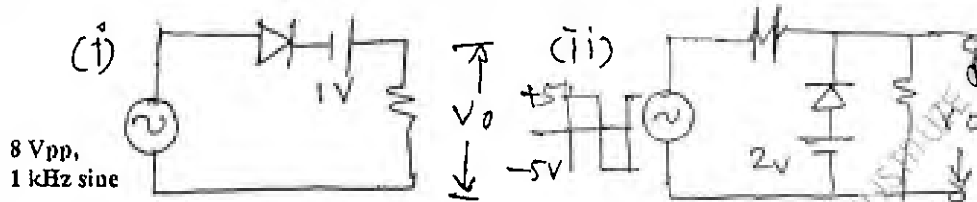
(a) Draw output waveform for following circuits.



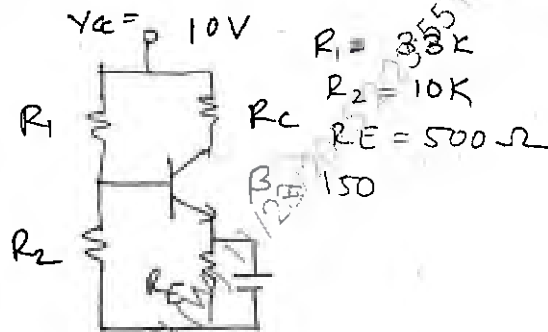- (b) Explain Wilson current source. 5  
 (c) What are different biasing methods used for FET, explain self bias technique. 5  
 (d) State and Explain Barkhausen criteria. 5  
 (e) Derive expression for efficiency for Class A transformer coupled amplifier. 5
2. (a) Find  $I_{CQ}$ ,  $V_{CEQ}$ ,  $R_i$  and  $R_O$  for following circuit with  $R_C = 1.2 \text{ k}\Omega$ . 10



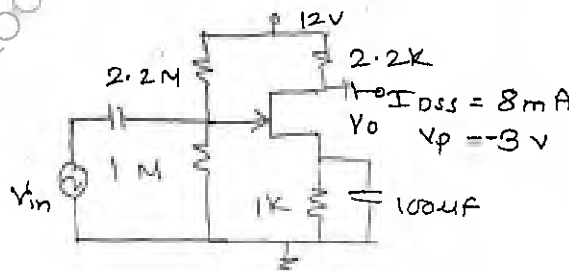
- (b) Explain any one method for biasing for E-MOSFET. 10
3. (a) Find  $A_v$ ,  $R_i$  and  $R_O$  for following circuit. 10



TURN OVER

SARDAR PATEL INSTITUTE OF TECHNOLOGY

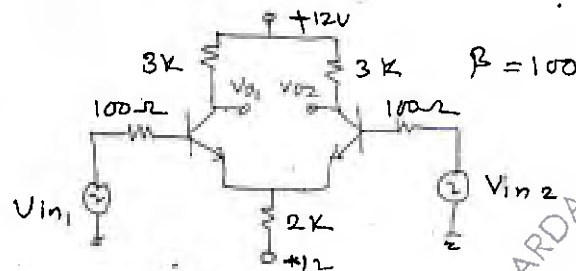- (b) Explain need for cascading of amplifiers. Explain CS-CE combination in detail. 10
4. (a) What is use of negative feedback in amplifier? Draw block diagram for current shunt feedback and find  $A_f$ ,  $R_{if}$  and  $R_{of}$ . 10
- (b) Explain High frequency response of CS-CS amplifier and hence derive equation of output frequency. 10
5. (a) For the following diff-amp find  $A_d$ ,  $A_c$  and CMRR. 10



- (b) Explain working of Class B push-pull power amplifier. What is cross over distortion? 10
6. Write short notes on (any four) 20
- High frequency oscillator,
  - Cascode amplifier,
  - High frequency model for BJT
  - Heat sinks
  - Constant current source used in diff-amp.