

[Time: 3 Hours]


[Marks:80]

Please check whether you have got the right question paper.

- N.B:
1. Question no1 is compulsory and solve any three questions from remaining.
 2. Draw neat and labeled diagrams.
 3. Assume suitable data if it is required.

Q.1 Solve any five:

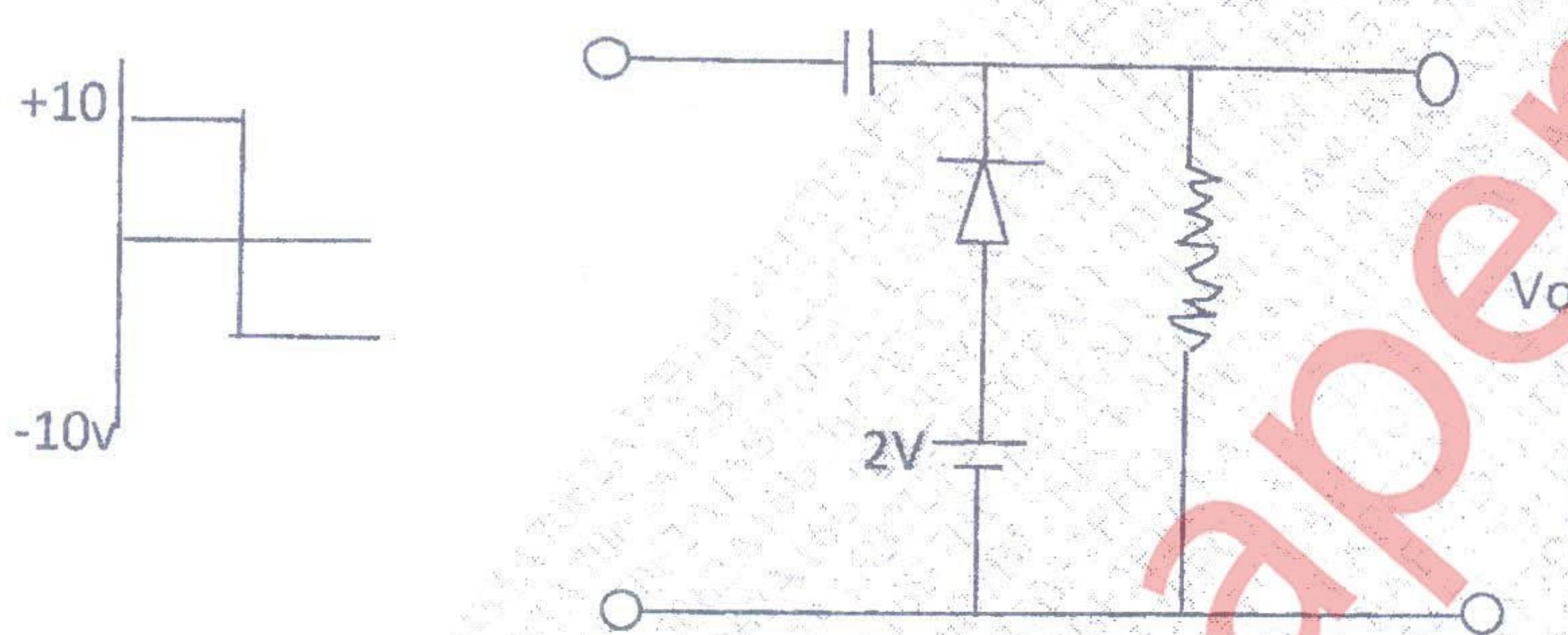- 1) Draw the output waveform for following circuit. Identify the type.




20

- 2) Explain any one biasing circuit used for E-MOSFET.
- 3) Explain effect of coupling and by pass capacitors on frequency response of CS amplifier.
- 4) State advantages of negative feedback.
- 5) Derive expression for efficiency of Class A Transformer coupled amplifier.
- 6) Compare CS amplifier with CE amplifier.

Q.2

- a) For the given circuit find I_B , V_{CE} , I_{CO} .


10

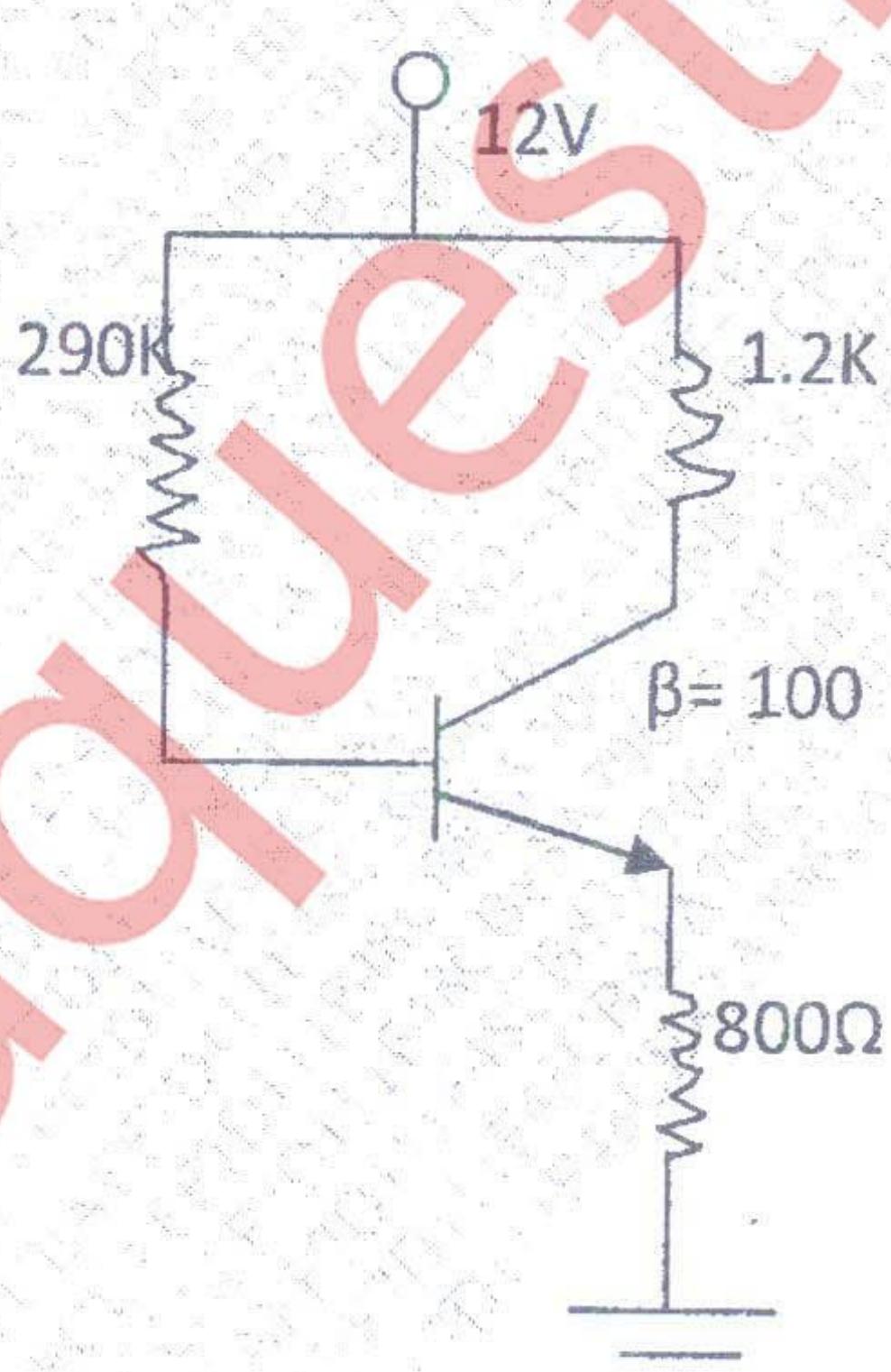

- b) Explain working of CS amplifier using JFET and derive formula for voltage gain, R_i and R_o .
(using self bias)


10

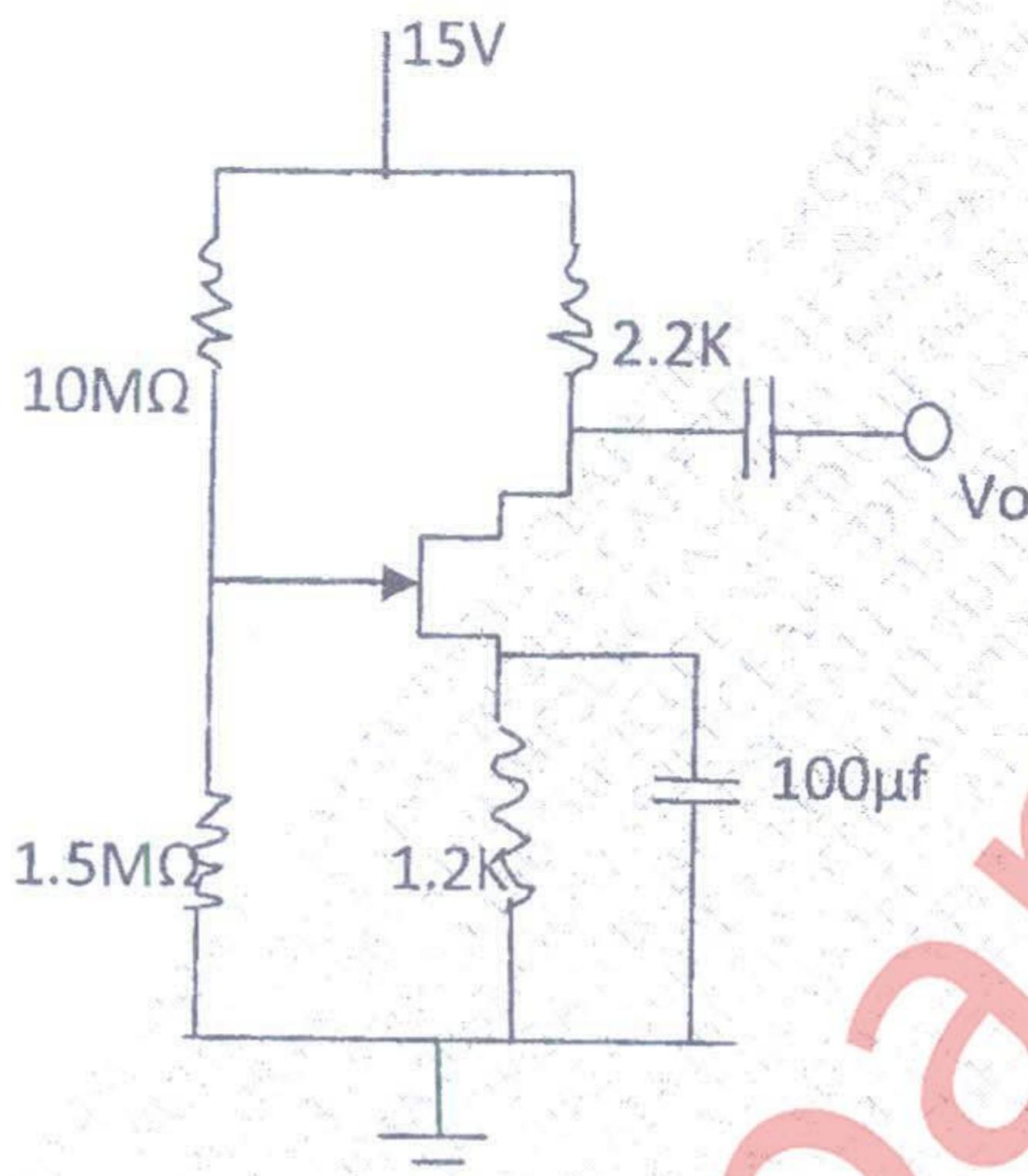- Q.3 a) Explain need for cascading amplifier stages. Explain working of CS-CE multistage amplifier and Derive expressions for A_{VT} , R_i and R_o . 12
 b) Explain working of Wein Bridge oscillator with the help of circuit diagram and give equation of frequency of oscillations. 08
- Q.4 a) For dual i/p balanced output diff amp derive expression for A_d and A_c . Suggest modification to improve CMRR. 10
 b) For the following circuit calculate A_v , R_i and R_o . 10



$$I_{DSS}=8\text{mA}, V_p=3\text{V}, R_d=50\text{k}$$

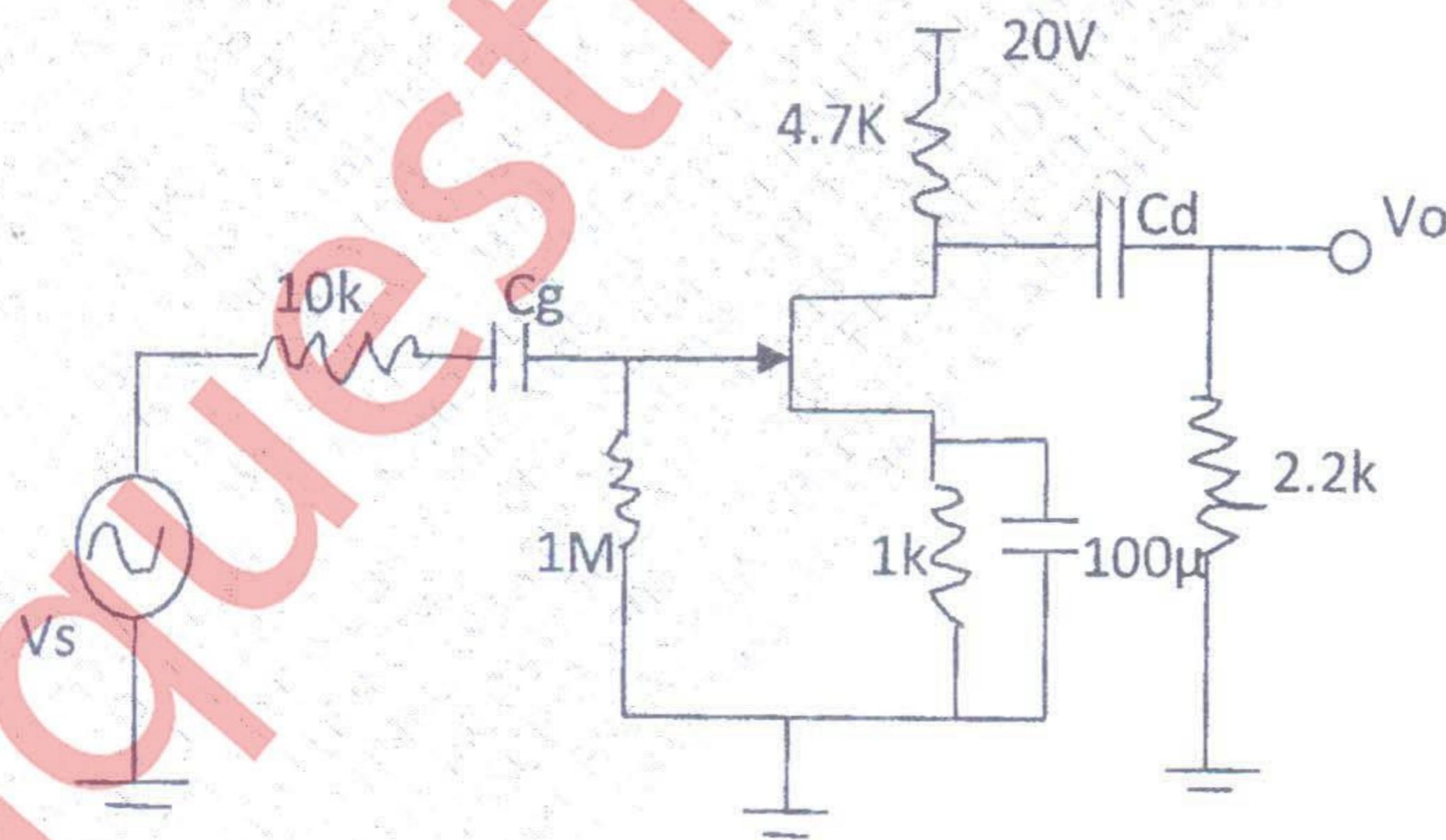- Q.5 a) Prove that efficiency of Class B transformer coupled power amplifier is 78.5%. Suggest schemes For removing cross over distortion. 10
 b) For the given circuit of CS amplifier find higher cut off frequency. 10



$$I_{DSS}=8\text{mA}, V_p=-4\text{V}, r_d=\infty$$

$$C_{gd}=2\text{pF}, C_{gs}=4\text{pF}, C_{ds}=0.5\text{pF}, C_{wi}=5\text{pF}, C_{wo}=6\text{pF}$$

(C_{wi} & C_{wo} are wiring capacitances at i/p and o/p respectively.)

Q.6 Write short notes on any four:

- 1) Comparison of CB, CE and CC amplifier
- 2) Current series negative feedback
- 3) Constant current source (in diff amp)
- 4) Cascode amplifier
- 5) Heat sink used in power amplifiers.

20