


Please check whether you have got the right question paper.

- N.B:**
1. Question no1 is compulsory and solve any three questions from remaining.
 2. Draw neat and labeled diagrams.
 3. Assume suitable data if it is required.

Q.1 Solve all:

20

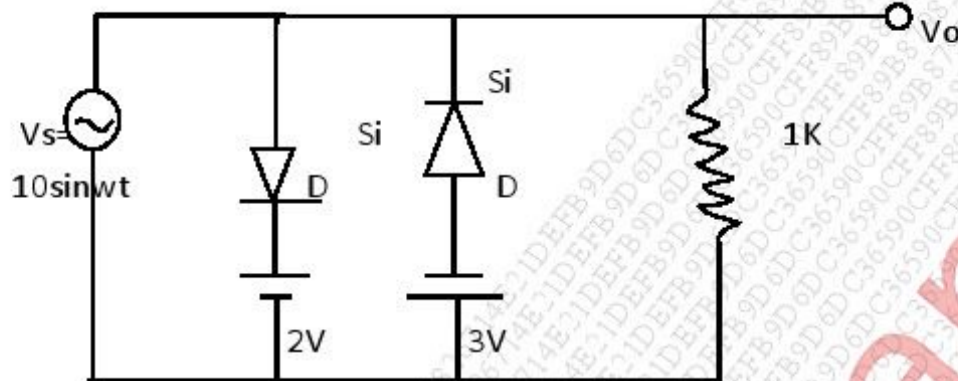- 1) Draw the output voltage waveform for a shown circuit.




- 2) Explain self bias circuit of D-MOSFET.
- 3) Draw high frequency ac equivalent circuit for CS JFET amplifier.
- 4) State the characteristics of negative feedback amplifier.
- 5) Explain any one method to improve CMRR of differential amplifier.

Q.2

- a) Determine operating point, V_B & V_E of given circuit.

10

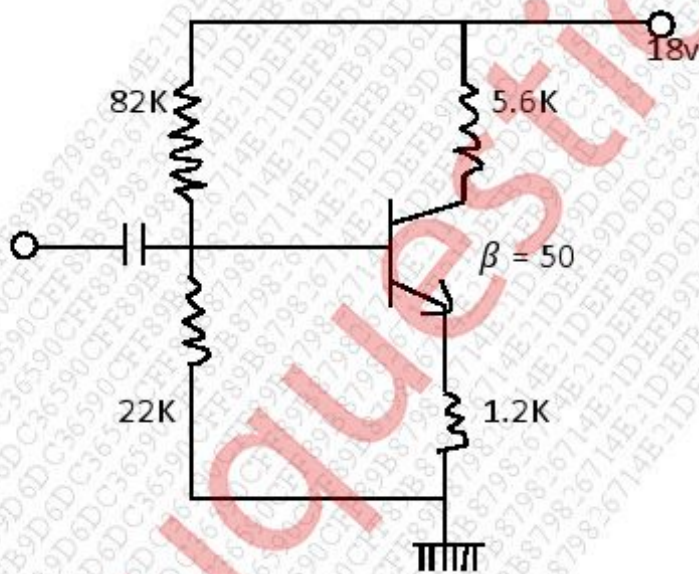

- b) Derive the expression of voltage gain, input impedance & output impedance for CS self biased JFET amplifier.

10

Q.3

- a) What is a need of multistage amplifier, derive the equation of overall voltage gain, Input resistance & output resistance.

12

- b) Explain the Hartley oscillator with proper circuit diagram.

08


Q.4

- a) Derive an expression for A_d , A_c & CMRR for dual input balanced output differential amplifier.

10

b) Determine A_v , Z_i & Z_o for given circuit

10

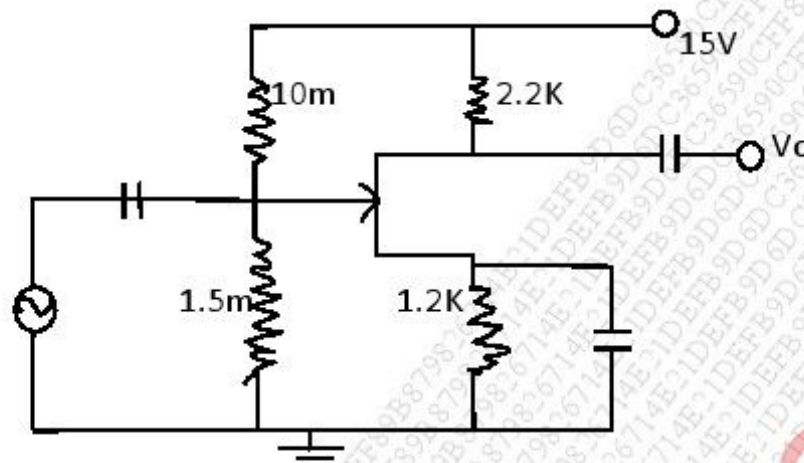

$I_{DSS} = 8\text{mA}$

$V_p = 3\text{V}$

$R_d = 50\text{k}$


Q.5

a) Draw the circuit diagram of Class AB push-pull amplifier & explain the working principle.

10

b) Determine higher cut off frequency for a given circuit

10

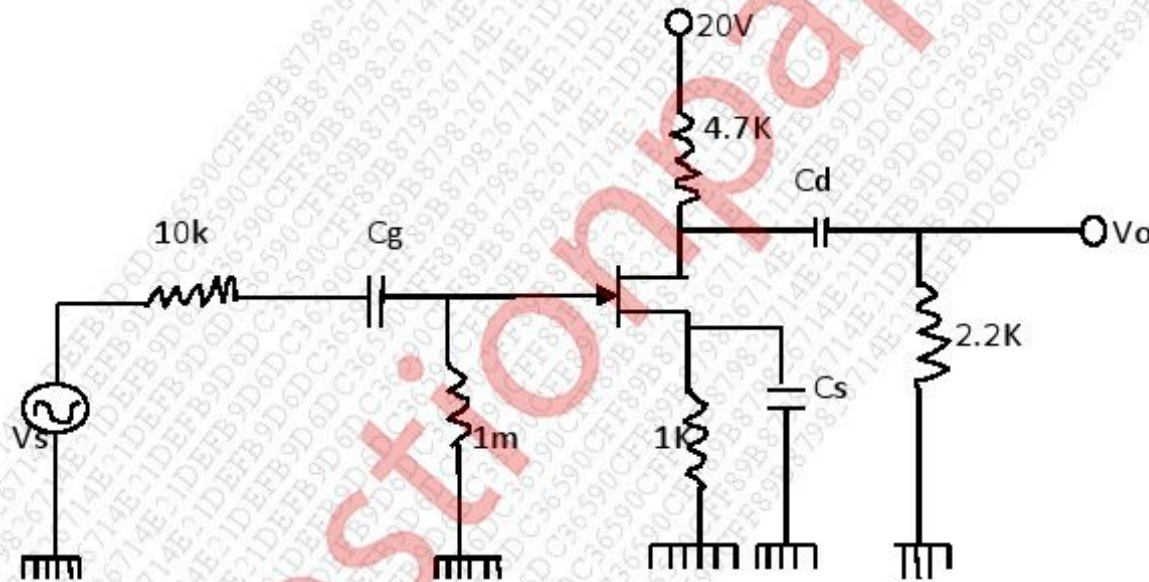

$I_{DSS} = 8\text{mA}$, $V_p = -4\text{V}$, $r_d = \infty\Omega$

$c_{gd} = 2\text{PF}$, $c_{gs} = 4\text{PF}$, $c_{ds} = 0.5\text{PF}$, $c_{wi} = 5\text{PF}$, $c_{wo} = 6\text{PF}$

c_{wi} & c_{wo} are wiring capacitance (Input & Output respectively)

Q.6

Write short notes (any four)

20

- 1) Comparison of CB, CE & CC amplifier
- 2) Voltage shunt negative feedback amplifier
- 3) Wilson current source
- 4) Cascode amplifier
- 5) Cross over distortion in class B power amplifier