

Digital Electronics

QP Code : 5174

(3 Hours)

Total Marks: 80

- N.B.** (1) Question No. 1 is **Compulsory**
 (2) Out of remaining questions, attempt **any three**
 (3) **Assume** suitable data if required
 (4) Figures to the right indicate **full marks**
1. (a) Compare SRAM and DRAM [5]
 (b) Compare Mealy and Moore machine [5]
 (c) Compare TTL and CMOS Logic [5]
 (d) Design a full adder using 3:8 decoder [5]
 2. (a) State and Prove DeMorgan's Laws [10]
 (b) Explain carry look ahead adder. What is its advantage over a simple adder [10]
 3. (a) Design a 4 bit Grey to Binary code converter [10]
 (b) Implement the given function using 8:1 Multiplexer [10]
 $F(A, B, C, D) = \sum m(0,1,4,5,6,8,10,12,13)$
 4. (a) Explain the working of Bidirectional Shift register with proper timing diagram [10]
 (b) Write a VHDL program to design a 1:8 Demux using Data flow modeling [10]
 5. (a) Minimize the following expression using Quine McClusky Technique [10]
 $F(A,B,C,D) = \sum m(1,2,5,7,9,15) + d(0,3,11)$
 (b) Convert D FF to T FF and SR FF to JK FF [10]
 6. (a) Design synchronous counter to count the sequence 0-1-2-3-4-5-0 [10]
 (b) Compare PAL with PLA with suitable examples of logic expressions [10]