

Q.P. Code : 545502**(3 Hours)****[Total Marks : 80**

- N.B. :** (1) Attempt **four** questions, question no **1** is **compulsory**.
 (2) Assume suitable data where ever required.
 (3) Answers to the questions should be grouped together.
 (4) Figure to the **right** of question indicates **full** marks.

1. Attempt any **four** : **20**
 - (a) Why wave analyzer is known as frequency selective voltmeter?
 - (b) Define accuracy, precision and sensitivity with suitable example.
 - (c) General specifications of Digital Multi-meter.
 - (d) List name of bridges for RLC measurement with proper classification.
 - (e) Significance of three and half digit display.

2. (a) What is eddy current sensor? Explain measurement of current using it. **10**
 (b) Draw neat block diagram of CRO and explain its functioning, comment on role of sweep in CRO. **10**

3. (b) Draw and explain Weighted resistor network type DAC for 3 bits input taking suitable example. **10**
 (b) Explain Kelvin's double bridge and its application in very low resistance measurement. **10**

4. (a) Explain dual slope integration type ADC with the help of block diagram and comment on its speed. **10**
 (b) Explain LVDT and define its application in displacement measurement. **10**

5. (a) Explain Hetrodyne type waves analyser and its applications. **10**
 (b) Discuss DSO with the help of block diagram along with various modes of operation also explain its applications. **10**

6. (a) Draw and discuss Maxwell Bridge and its application for measurement of inductance. **10**
 (b) Define Q factor and explain working of a Q meter for Q factor measurement. **10**