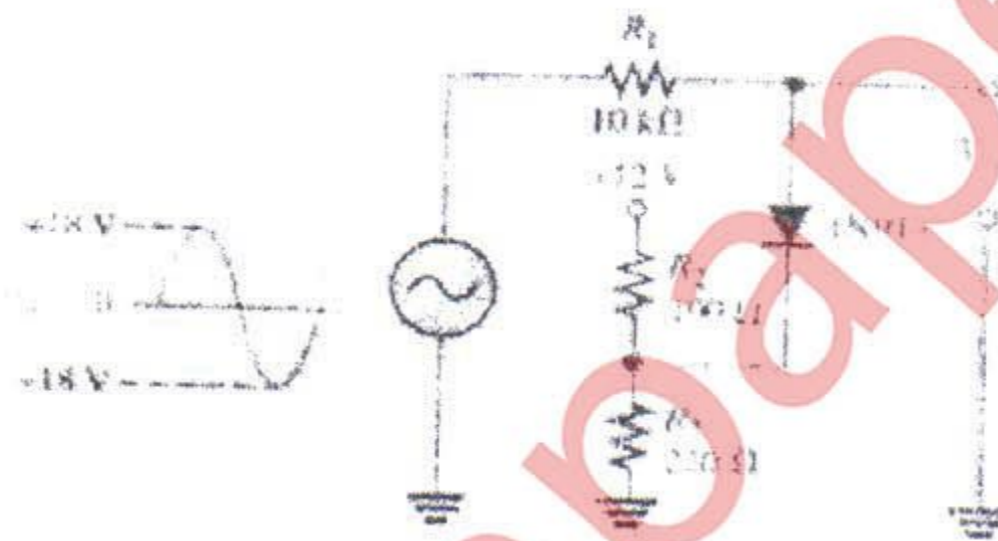


Max. Time: 3 hr


Max. Marks: 80

 Q.1 is compulsory (any Four). Attempt any 3 from Q.2 to Q.6

- 1(a) Describe the output voltage waveform for the diode limiter shown below (5)




- 1(b) Define a filter. How are filters classified? (5)
1(c) Explain Thermistor compensation with circuit diagram (5)
1(d) For the network of Fig. shown below determine I_C and V_{CE} , V_B , V_C (5)




- 1(e) How FET be employed as a voltage controlled resistor. (5)
2(a) Determine the minimum value of R_L to ensure that the Zener diode is in the "on" state (10)


[TURN OVER

 

 - 2(b) Compare class A, class B power amplifiers based on the output waveform for collector current, linearity, distortion and efficiency. (10)
- 3(a) Determine V_C and V_B for the network of fig. shown below. (10)



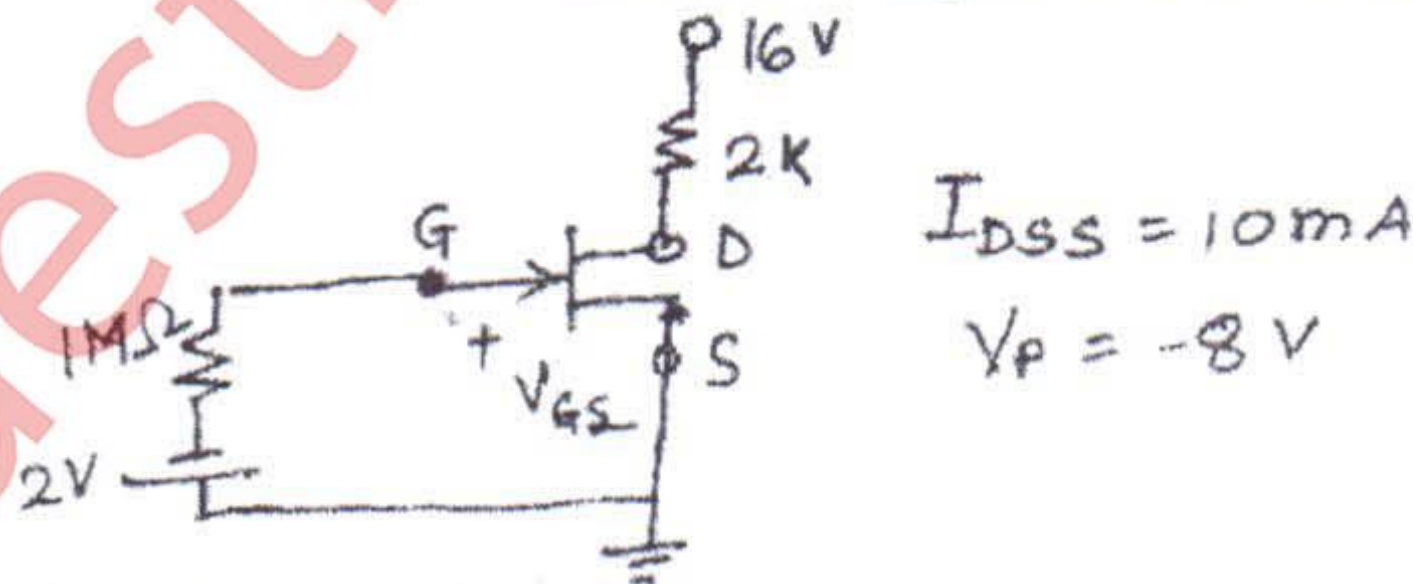- 3(b) Derive the expressions for the I_B , I_C and V_{CE} for emitter bias configuration of BJT. (10)
- 4(a) Explain the structure, operation and current-voltage characteristics of Enhancement type MOSFET. (10)
- 4(b) Determine V_{GS} , I_D , V_{DS} for the fixed Bias configuration as shown in fig below (10)



- 5(a) Using standard 5% resistances, design a circuit such that $V_0 = -2(3v_1 + 2v_2 - 4v_3)$. (10)

TURN OVER