

Analog Electronics (3 Hours)




[Total Marks : 80

- N. B. : (1) Question No. 1 is compulsory.
 (2) Attempt any **three** questions from the remaining **five** questions.
 (3) **Figures to the right** indicate full marks.
 (4) Assume **suitable** data if **necessary**.

1. Attempt any **four** questions from the following:-

20

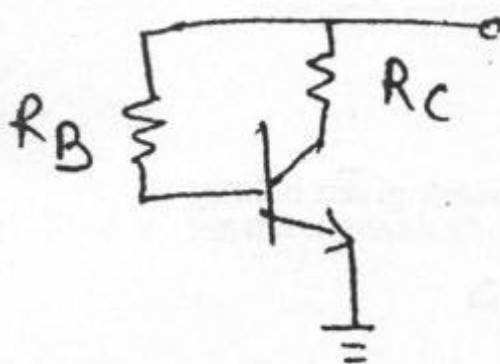- (a) Explain with the help of circuit diagram any one method to obtain full-wave rectification.
 (b) Find R_B and R_C for the network given.



$$I_{BQ} = 40 \mu A$$


$$V_{CC} = 20 V$$

$$I_{C_{sat}} = 8 mA$$

- (c) Can FET be employed as a voltage controlled resistor? If yes, explain how.
 (d) List five characteristics of an ideal op-amp.
 (e) Draw and explain an adder circuit using op-amp.
 (f) Draw and explain the typical block diagram of a regulated power supply.

2. (a) Find I_C , I_B , V_{CE} , V_E and V_B for the following circuit.

10

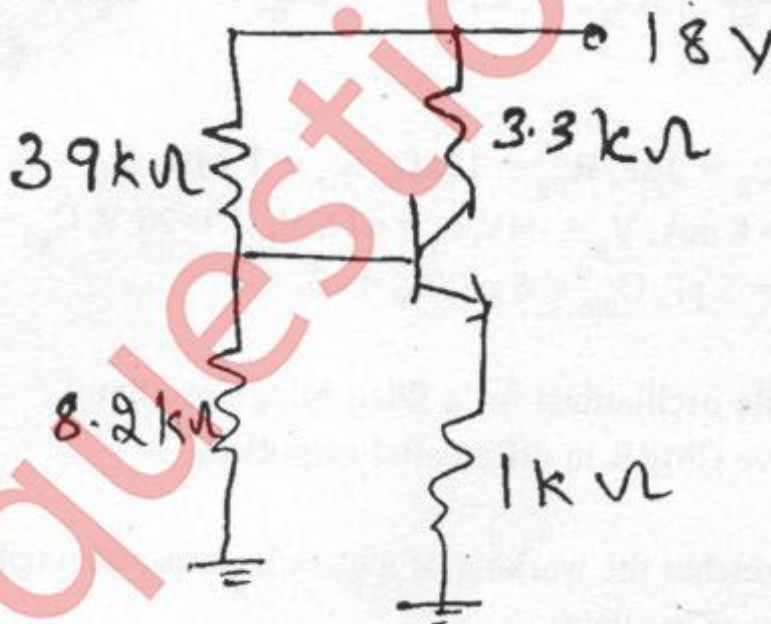


$$\beta = 120$$

- (b) Derive the stability factor $S(I_{CO})$ for emitter-stabilized Bias circuit. Calculate $S(I_{CO})$ for the same circuit if $R_B = 510 k\Omega$, $R_C = 2.4 k\Omega$, $R_E = 1.5 k\Omega$, $V_{CC} = 2.4 k\Omega$, $\beta = 100$.

[TURN OVER


3. (a) Find I_{DQ} , V_{GSQ} , V_{DS} , V_D and V_G for the following network.

10

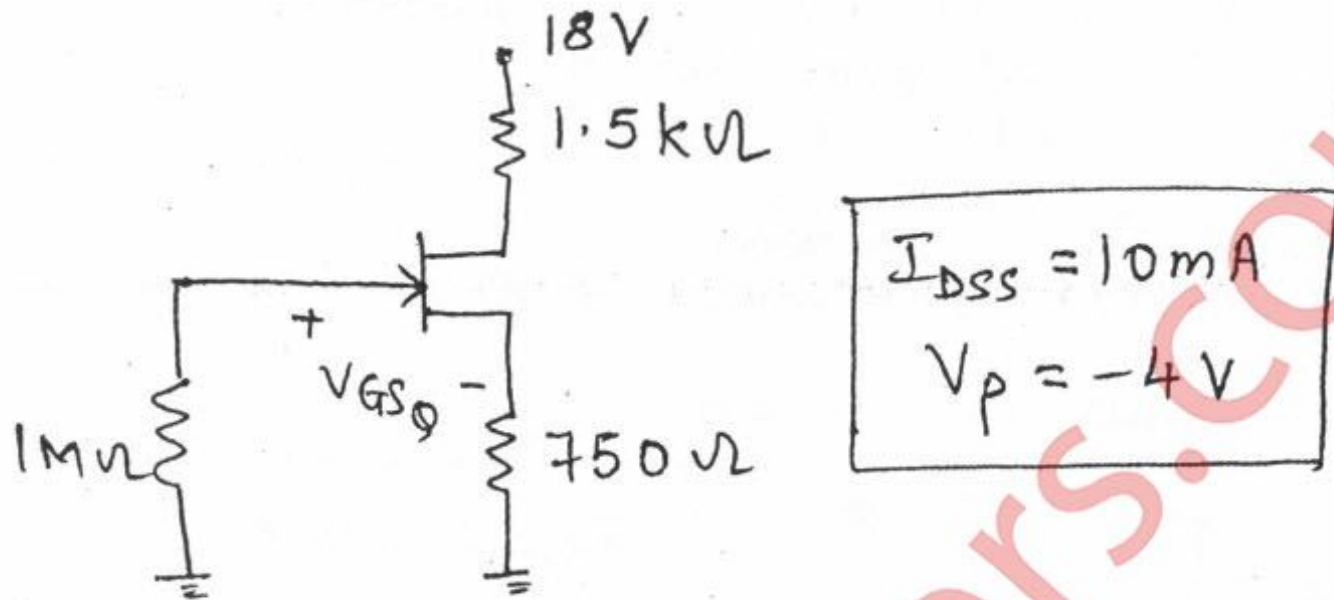

(b) Determine the high frequency cut-off for the network given below:

10

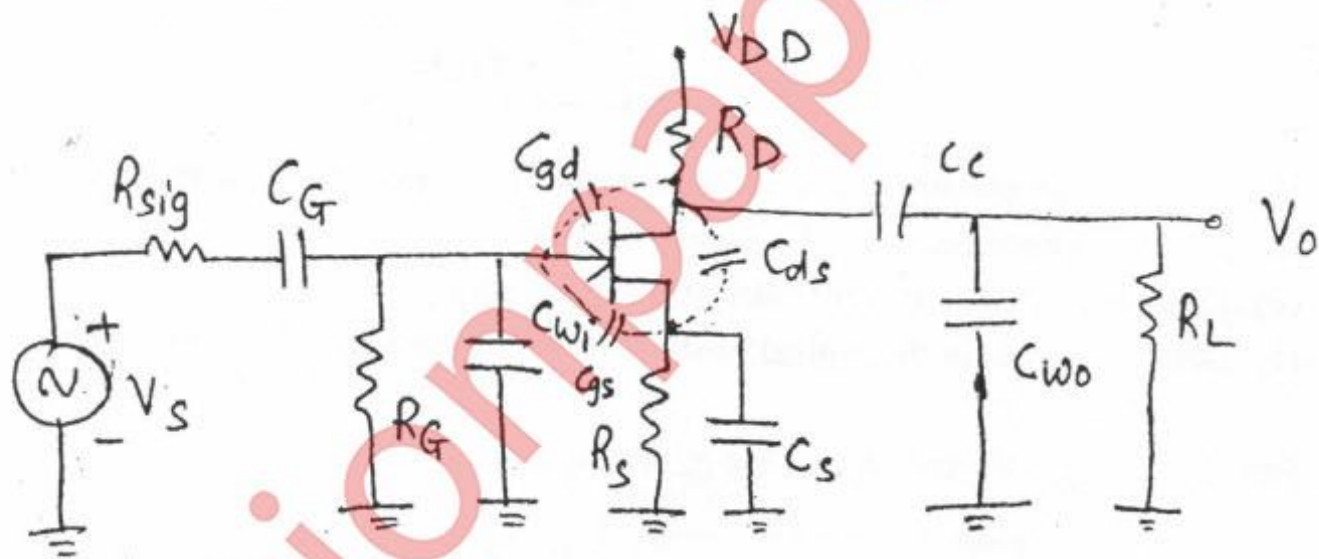

$C_G = 0.01\ \mu\text{F}$, $C_C = 0.5\ \mu\text{F}$, $C_S = 2\ \mu\text{F}$, $R_{sig} = 10\text{k}\Omega$, $R_G = 1\ \text{M}\Omega$, $R_D = 4.7\ \text{k}\Omega$, $R_S = 1\text{k}\Omega$, $R_L = 2.2\ \text{k}\Omega$, $I_{DSS} = 8\ \text{mA}$, $V_p = -4\text{V}$, $r_d = \infty\Omega$, $V_{DD} = 20\ \text{V}$, $C_{gd} = 2\text{pF}$, $C_{gs} = 4\ \text{pF}$, $C_{ds} = 0.5\ \text{pF}$, $C_{wi} = 5\ \text{pF}$, $C_{wo} = 6\ \text{pF}$, $A_v = -3$.

4. (a) Derive the conditions for stable oscillations for a Wien bridge oscillator.

10

(b) Explain the methods to improve CMRR in differential amplifiers.

10

5. (a) Draw and explain with neat sketches the working of a class B push-pull amplifier.


10

(b) Draw and explain a series voltage regulator.

10

6. (a) Draw and explain working of a schmitt trigger (inverting and non-inverting configuration) with input and output waveforms. 10

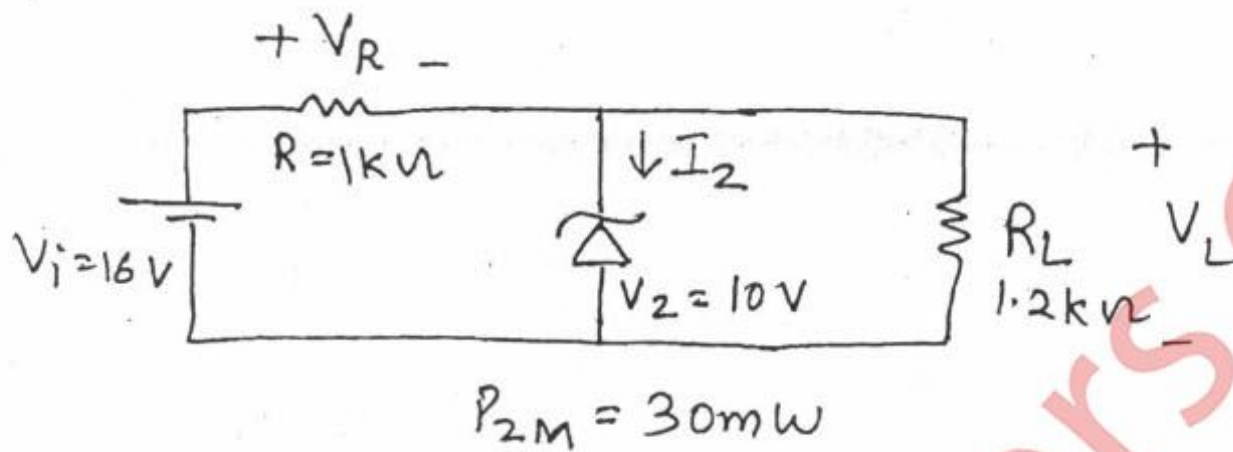(b) For the network shown below find V_L , V_R , I_2 and P_2 . 5



(c) Find V_0 for the network shown below:- 5

