



(3 Hours)


[Total Marks : 80

- N.B. :** (1) Question No. 1 is **compulsory** based on entire syllabus.
 (2) Solve **any THREE** main questions out of remaining.

1. Answer **any four** :

20

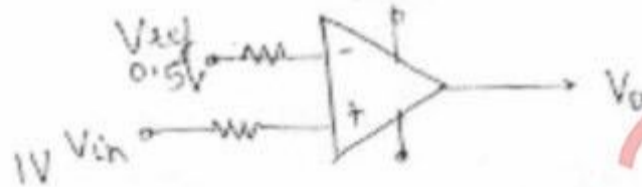
- a) What is the Shockley's equation in FET?
 b) Draw the output of following comparator. Explain its operation.
 Reference voltage is 0.5V. Input is sine wave of 1V peak.



- c) Compare CB CE and CC configurations.
 d) What are the characteristics of an Ideal Op-Amp?
 e) Draw the circuit of Log amplifier and explain.



2. Answer the following :-

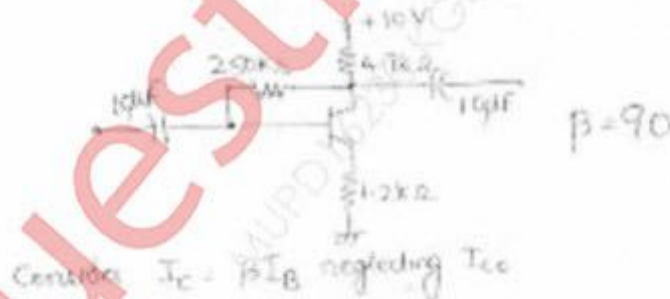- a) Perform DC analysis and determine voltage V_{CEQ} and the current is I_B, I_C . 10
 $R_C = 4.7K, R_E = 1.2K, R_B = 250K, V_{CC} = 10V.$



- b) Determine the output of following :

10

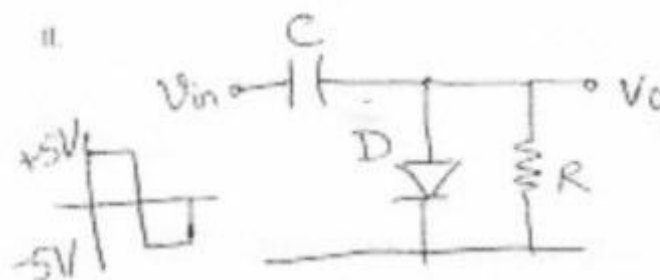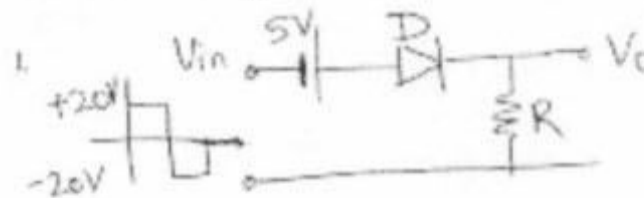

[TURN OVER]


3. Answer the following :

a) Draw the circuit and find frequency of oscillation for Wein Bridge oscillator. 10
Explain its operation.

b) Draw and explain the circuit of integrator and differentiator using op-amp. 10

4. Answer the following :-

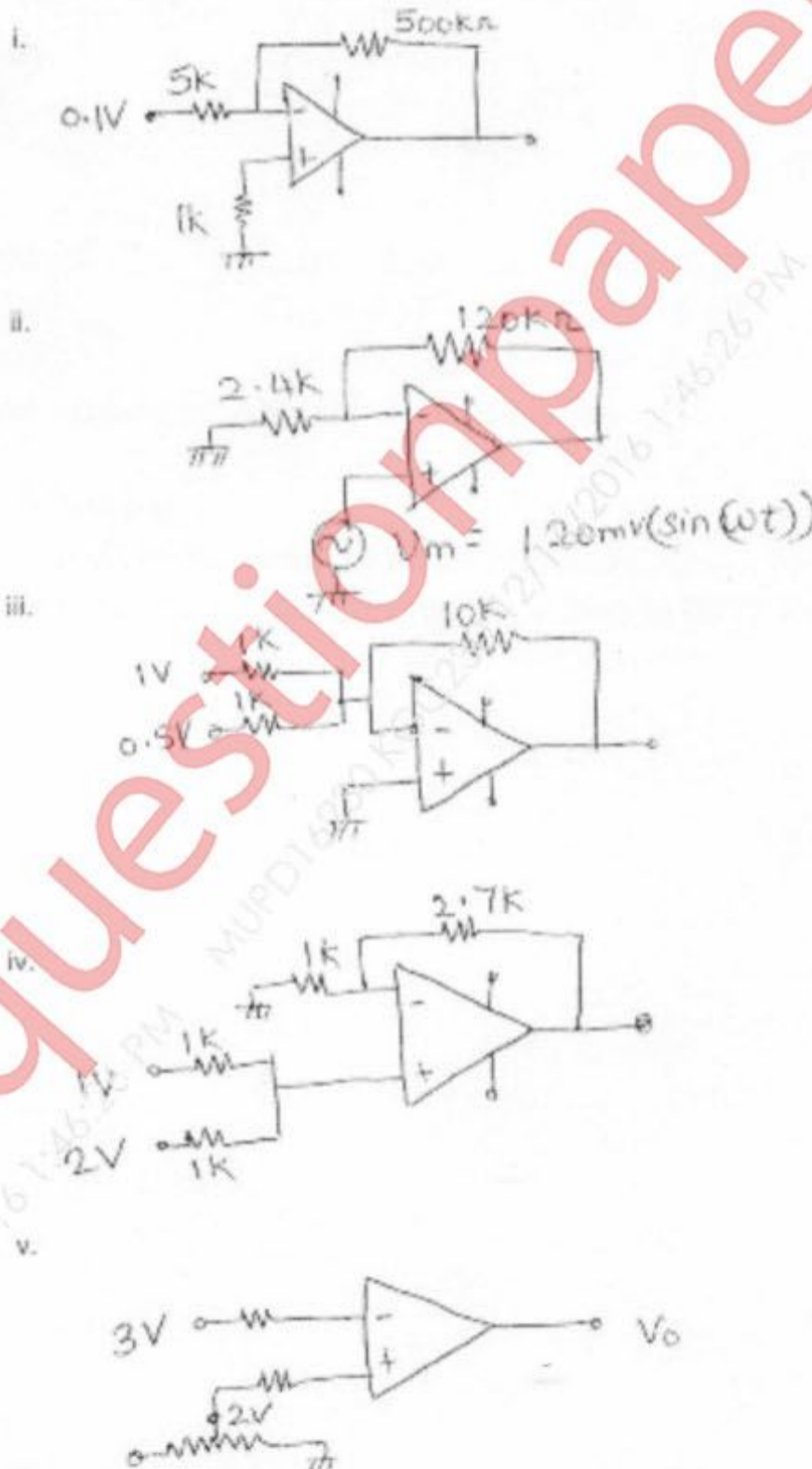a) Draw the output of following op-amp circuits. 10




b) Explain the working of JFET. Draw the characteristics (graphs)

10

[TURN OVER]

5. Answer the following :-

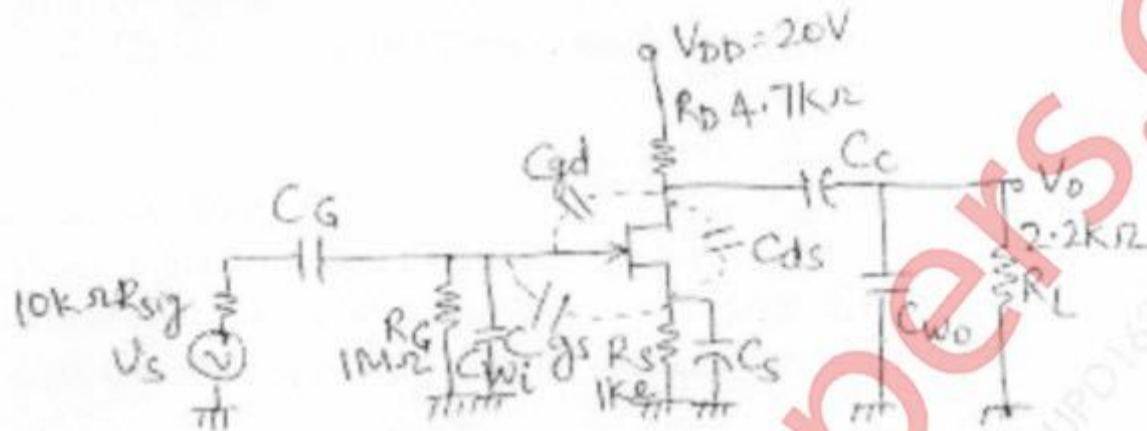a) Determine the lower cutoff and higher cutoff frequency for high frequency 10 circuit as shown.



$C_G = 0.01 \mu F$

$C_{gd} = 2 \text{ pF}$

$C_{wo} = 6 \text{ pF}$

$I_{DSS} = 8 \text{ mA}$

$C_C = 0.5 \mu F$

$C_{gs} = 6 \text{ pF}$

$C_{wi} = 5 \text{ pF}$

$V_p = 6 \text{ V}$

$C_S = 2 \mu F$

$C_{ds} = 0.5 \text{ pF}$

$A_v = -3$

$R_d = \infty$

b) Draw and explain CLASS B Power amplifier.

10

6. Answer the following :

a) Draw and explain the circuit of series regulator.

10

b) Why is the potential divider biasing circuit best in BJT? Explain with an example.

10
