



SE / Sem - III / INST / Digital Electronics / 25-11-13

**N.B. :** (1) Question No. 1 is **compulsory**. Attempt any **three** questions out of remaining **five** questions.

(2) **All** questions carry **equal** marks.

(3) Assume suitable **data** if **necessary**.

1. Solve any **four** out of following :- 20
  - (a) Convert  $(123.091)_{10}$  to HEX, Octal and Binary.
  - (b) State and prove De Morgan's theorems.
  - (c) Implement 4:1 MUX using logic gates.
  - (d) Design T flipflop using NAND gates only.
  - (e) Explain noise margin and fanout of digital ICS.
  
2. (a) Performe following operation :- 5
  - (i)  $(29)_{10} - (33)_{10}$  using 2's complement method.
  - (ii)  $(123)_{16} \times (ABC)_{16}$
  
- (b) Prove that  $(A + \bar{B} + AB)(A + \bar{B})(\bar{A}B) = 0$  5
- (c) Design binary to XS3 code converter using logic gates. 10
  
3. (a) Simplify following using K-map and implement using only any one type of universal gates. 10  
 $y = f(A, B, C, D) = \pi M(0, 1, 6, 7, 8, 9)$
- (b) Design full adder using two half adders.. 5
- (c) Compare demultiplexers and decoders. 5
  
4. (a) Implement full subtractor using two 4:1 MUX. 10
- (b) Design synchronous mod 4 updown counter using JK flip-flops. 10
  
5. (a) Design asynchronous decade counter using T flip-flop. 10
- (b) Design Johnson's counter using D flip-flop. 10
  
6. Write short notes on any **four** :- 20
  - (a) Carry look ahead adder
  - (b) Basic dynamic RAM Cell.
  - (c) ASCII Codes
  - (d) FPGA
  - (e) ALU.