



(3 Hours)

[Total Marks : 80]

- N.B. :** (1) Question No. 1 is **compulsory**. Attempt any 3 questions out of remaining 5 questions.
 (2) **All** questions carry **equal** marks.
 (3) Assume **suitable** data is **necessary**.

1. Attempt any **four** :— 20
- Explain difference between synchronous and asynchronous counter.
 - Explain gray code and its application in brief.
 - Design SR slip slop using only NOR gates.
 - Design Half subtractor using logic gates.
 - Implement 8 : 1 MUX using two 4 : 1 MUX.
2. (a) Perform following operations :— 10
- $(3FD \cdot 1E)_{16} \rightarrow (?)_{10}$
 - $(119 \cdot 27)_{10} \rightarrow (?)_8$
 - $(110101100111 \cdot 1010)_2 \rightarrow (?)_{10}$
 - $21 - 39$ using 2's complement
 - $(168)_H \times (32F)_H$
- (b) Prove that— 10
- $A [B + C (\overline{AB + AC})] = AB$
 - $A + \overline{AB} + \overline{A}BC + \overline{A}BCD = A + B + C + D$
3. (a) Minimize following using k-map and implement using logic gates. 10
- $$f = \sum m (0, 1, 3, 5, 9, 12) + d (2, 4, 6, 7)$$
- (b) Design 2 bit magnitude comparator. 10
4. (a) Implement following using 8 : 1 MUX. 10
- $$f = \sum m (0, 1, 3, 4, 5, 9, 10, 12, 13, 15)$$
- (b) Design full adder using 3 : 8 decoder. 10
5. (a) Convert SR flip flop to JK flip flop. 10
- (b) Design MOD-11 asynchronous counter using JK flip flop. 10
6. Write short note on any **four** :— 20
- | | |
|-----------------------------|-------------------|
| (a) Ring Counter | (d) PLA and PAL |
| (b) Logic family Comparison | (e) Hamming Code. |
| (c) ALU | |