

Digital Electronics

Q. P. Code : 550601

(3 Hours)



(Total Marks : 80)

- N.B.** (1) Question no 1 is compulsory.  
 (2) Attempt any three questions from the remaining questions  
 (3) Figures to the right indicate full marks.  
 (3) Assume suitable data wherever necessary.

1. Answer the following (**any four**) 20  
 (a) Convert: (i)  $(21D.2F)_{16}$  to  $(?)_{10}$ . (ii)  $(67)_{10}$  to  $(?)_{BCD}$ .  
 (b) What is a debounce switch? Why is it used in digital switching circuits? Explain.  
 (c) State and prove DeMorgan's theorems.  
 (d) Design half subtractor using logic gates.  
 (e) Simplify with k-map & implement with logic gates  $f = \sum m(2, 3, 4, 5, 12, 13)$ .
2. Perform. 20  
 (a) Perform the following:-  
 (i) Subtract  $(CB2)_{16}$  &  $(972)_{16}$  use the 16's complements method.  
 (ii) Write the Hamming code for data 1101.  
 (b) Simplify using Boolean laws & implement with logic gates.  
 (i)  $f = \overline{A}BCD + A\overline{B}CD + \overline{A}BC\overline{D} + A\overline{B}C\overline{D}$   
 (ii)  $f = (AB.(C + D)).(\overline{AB})$
3. (a) Convert SR flip flop to D flip flop & TFF. 10  
 (b) Design & implement with gates a parity generator circuit for odd parity. 10
4. (a) Design a MOD-6 ripple counter using JKFF draw o/p waveforms for each flip flop. 10  
 (b) Design & implement a full odder circuit using a 3:8 Decode. 10
5. (a) Explain with a neat diagram working of SISO shift register. Draw necessary timing diagram. 10  
 (b) Simplify following using k-map & implement using logic gates. 10  
 $f = \sum m(0,3,5,7,8,11,12,15)+d(2,13)$
6. Write a short notes on:- (any four) 20  
 (1) ALU  
 (2) Dynamic RAM cell.  
 (3) PAL & PLA.  
 (4) FPGA  
 (5) Schottky clamped TTL.

\*\*\*\*\*