

N.B.

1. Q.1 is compulsory. Attempt any three from the remaining questions.
2. All questions carry equal marks.
3. Figures to the Right indicate full marks.
3. Assume suitable data if necessary

Q.1 Attempt any four

20

- a. What are priority encoders? Explain their usage in detail.
- b. Perform subtraction using 2's complement :
(i) $23 - 48$ (ii) $32 - 64$.
- c. Convert $(110101.10101)_2$ to equivalent decimal and hexadecimal number.
- d. Explain Ring counter in detail.
- e. Encode the following binary words into 7-bit odd parity Hamming code .
(i) 1001 (ii) 1101.
- f. Write the significance of standard SOP and POS forms of Boolean expressions. Convert the Boolean expression $y = (A + B)(B + C)(A + C)$ into standard POS form.

- Q.2 A. Reduce the following function using Karnaugh Map technique and implement it using gates : 10

$$f(A, B, C, D) = \prod M(4, 6, 10, 12, 13, 15)$$

- B. Design full adder circuit using half adder circuits. 10

- Q.3 A. What do you mean by Multiplexer tree? Construct 32:1 multiplexer using 8:1 multiplexer. 10

- B. Design parity generator / checker circuits. 10

- Q.4 A. What are sequential circuits? Explain D flip-flop in detail. 10

- B. Design Modulo-9 ripple counter using T flip-flops. 10

- Q.5 A. Implement the following function using 8:1 Multiplexer : 10

$$f(P, Q, R, S) = \sum m(0, 1, 3, 4, 8, 9, 15)$$

- B. Explain working of Bi-directional universal shift register. 10

- Q.6 Write short notes on the following 20

- a. Random-Access Memory.
- b. FPGA.
- c. Comparison of features of TTL, ECL and CMOS family.
- d. Arithmetic Logic Unit (ALU).