

QP Code : NP-18622

(3 Hours)

[Total Marks :80



- N.B. : (1) Question No.1 is compulsory. Attempt any 3 out of remaining questions.
(2) All questions carry equal marks.
(3) Assume suitable data is necessary.

1. Answer any four out of following.

- (a) What is Race around condition? what are solutions for this condition?
(b) Explain difference between combinational and sequential circuit.
(c) Implement XNOR logic gate using only NAND gates and only NOR gates.
(d) Implement half adder using logic gates.
(e) Explain difference between demultiplexer and decoder.

20

(a) Perform following conversions / arithmetic operations.

10

- (1) $(97AC. 21)_{16}$ $(?)_{10}$
(2) $(895.01)_{10}$ $(?)_8$
(3) $(110111011101.1101)_2$ $(?)_{16}$
(4) $(23)_{10} - (11)_{10}$ using 2's complement.
(5) $(16)_7 + (13)_7$

(b) Minimize following logic function using K-map and implement with logic gates.

$$F = \sum m(5,6,7,13,14,15)$$

3. (a) Implement full adder using logic gates.
(b) Implement following function using one 8:1 mux.
 $F = \sum m(2,3,7,8,10,12,13)$

10

10

4. (a) Design MOD-5 Asynchronous counter using JK flipflop.
(b) Design Ring Counter using D flipflop.

10

10

- (a) Convert 1. SR flipflop to D flipflop
2. SR flipflop to T flipflop

10

(b) Prove following using boolean laws

1. $\overline{AB(B+C)} = \overline{BC}$

2. $\overline{AB(C+D).AB} = \overline{A+B+C+D}$

6. Write short notes on any four.

20

- (a) S.R flipflop
(b) Comparison of TTL and CMOS
(c) PAL and PLA
(d) Serial input and serial output register
(e) Hamming code.