


(3 Hours)

[ Total Marks : 80


- N.B. :** (1) Question No. 1 is compulsory.  
 (2) Attempt any **three** questions from the remaining **five** questions.  
 (3) **Figures** to the **right** indicate **full marks**.  
 (4) Assume **suitable** data, if **required**.

1. Attempt any **four** questions :-

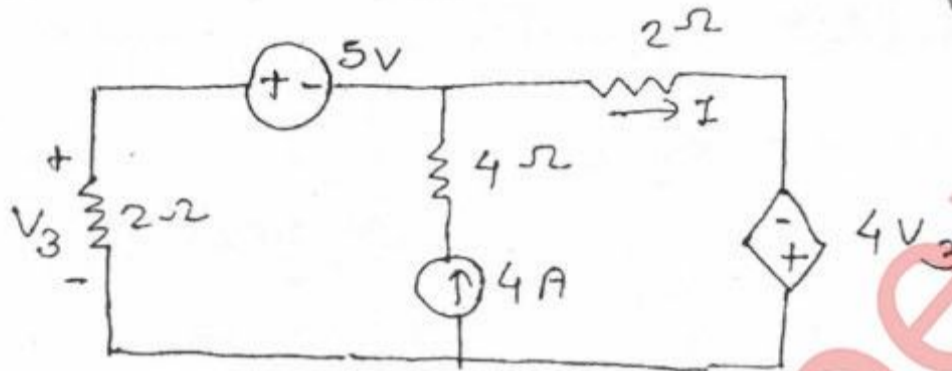
(a) Determine the current  $I$  through  $2\Omega$  resistor :-



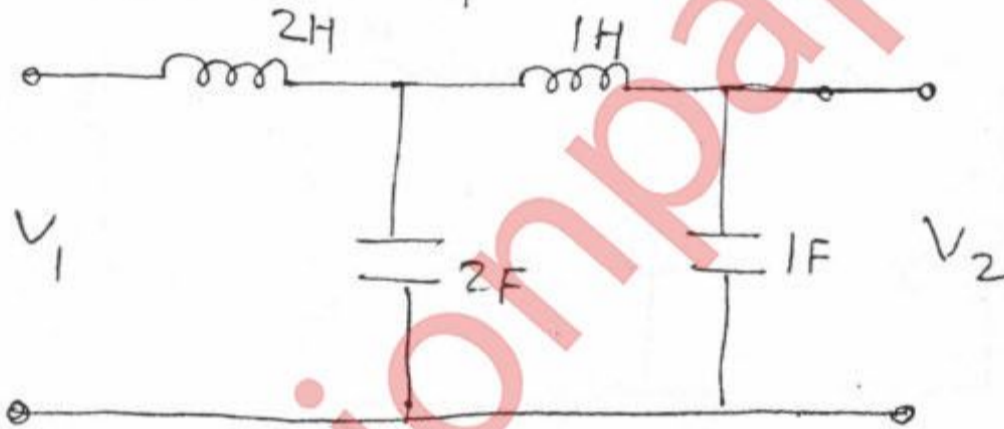(b) For the given circuit find  $\frac{V_2}{V_1}$



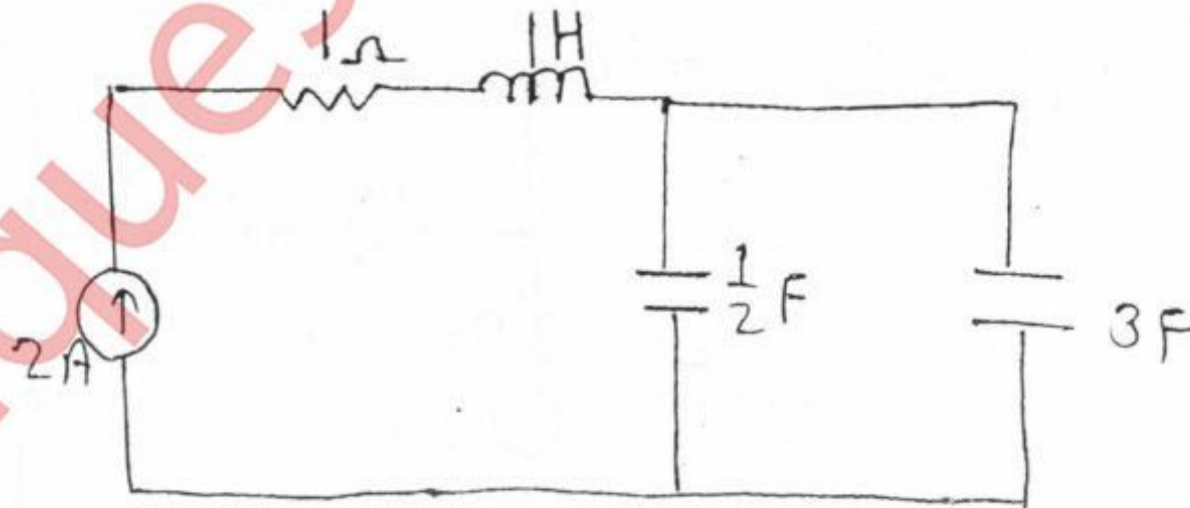- (c) Write all the properties of LC synthesis.  
 (d) Draw the dual network of the circuit shown in figure :-



TURN OVER




20


(e) Discuss the initial and steady state conditions in relationship with voltage and current for the following circuit elements :-

- (i) Resistor.
- (ii) Inductor.
- (iii) Capacitor.

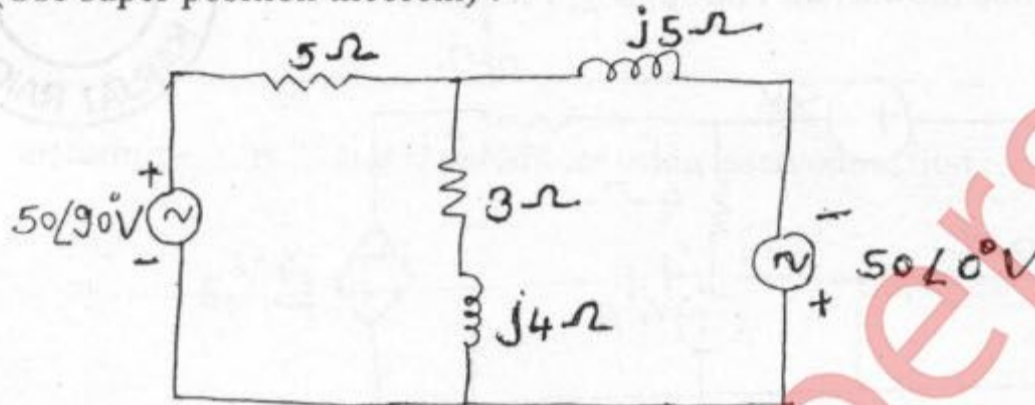2. (a) Find the currents through  $3 + j4\Omega$  impedance of the network given below. 10  
(Use super position theorem) :-




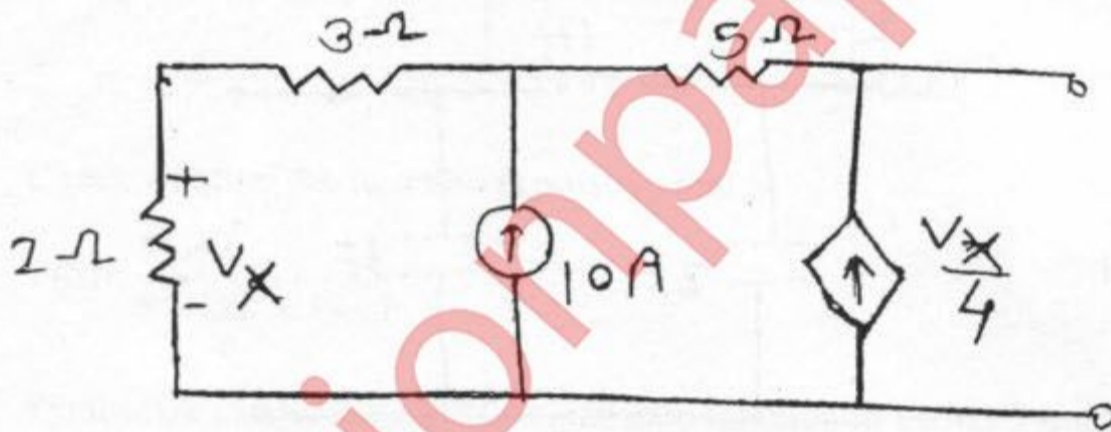(b) Determine the venin's equivalent network for the network given below :- 10



3. (a) For the network shown draw graph and write :- 10

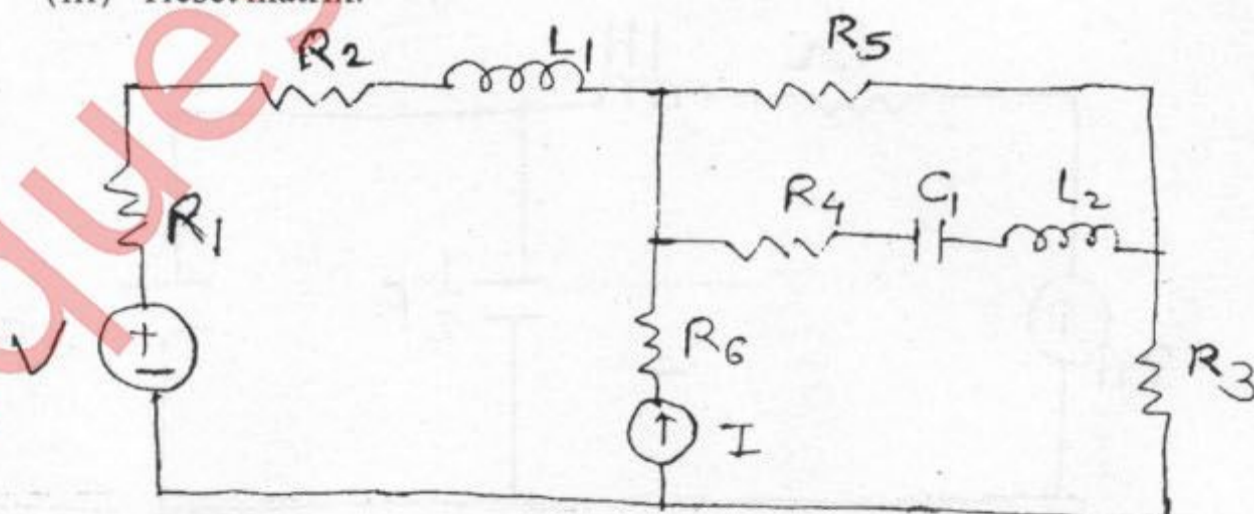- (i) Incidence matrix.
- (ii) Cutset matrix.
- (iii) Tieset matrix.




TURN OVER



(b) Find the currents  $I_1, I_2, I_3$  and  $I_4$ .

10

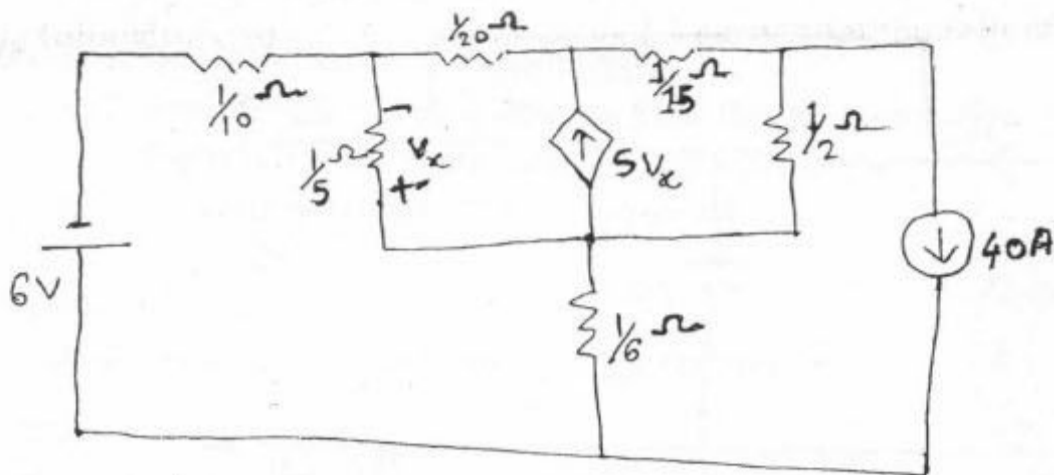


4. (a) The switch in the network is opened at  $t = 0$ . Find  $i(t)$  for  $t > 0$  if

10


(i)  $L = \frac{1}{2}H$  and  $C = 1F$

(ii)  $L = 1H$  and  $C = 1F$

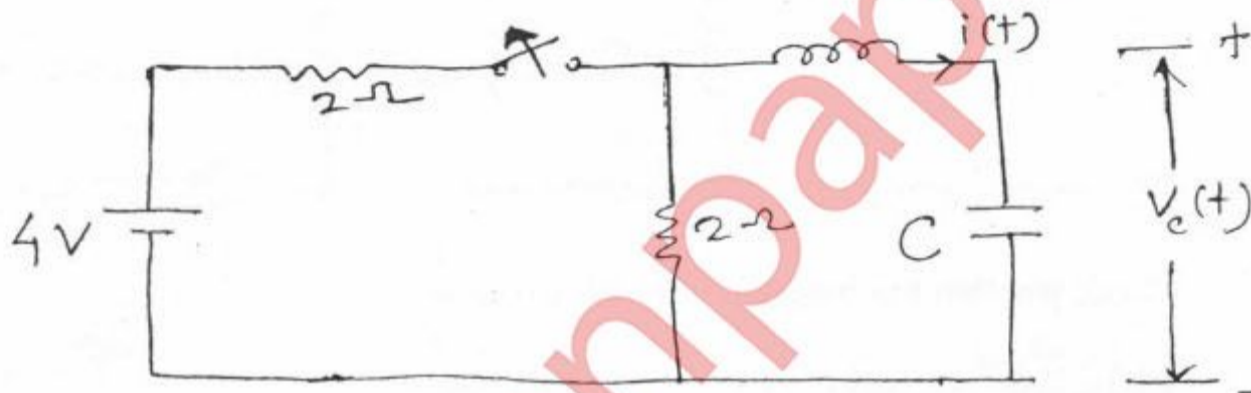

(b) For the given network find  $i(0^+), \frac{di(0^+)}{dt}, \frac{d^2i(0^+)}{dt^2} :-$


10

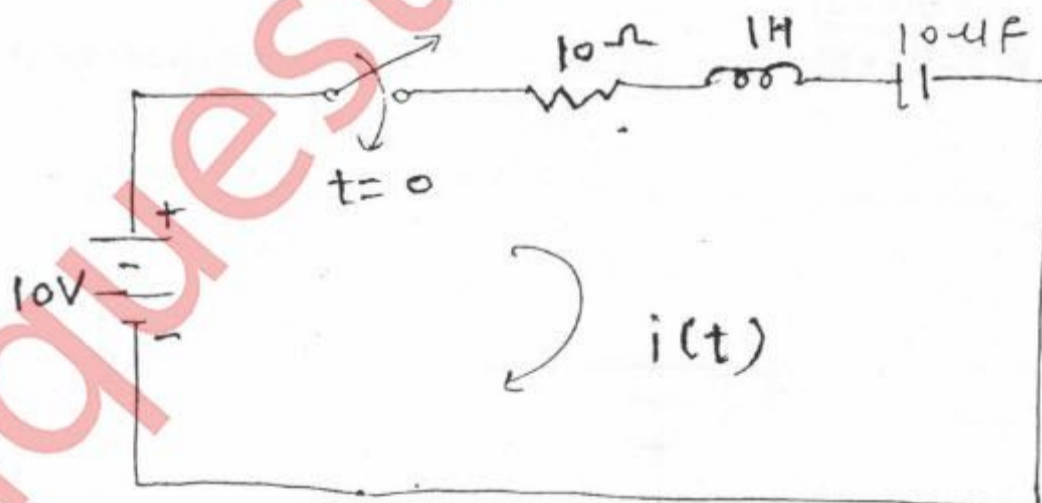

TURN OVER


5. (a) In the network shown below, determine  $Z_{11}(s)$ ,  $G_{12}(s)$  and  $Z_{12}(s)$ .

10

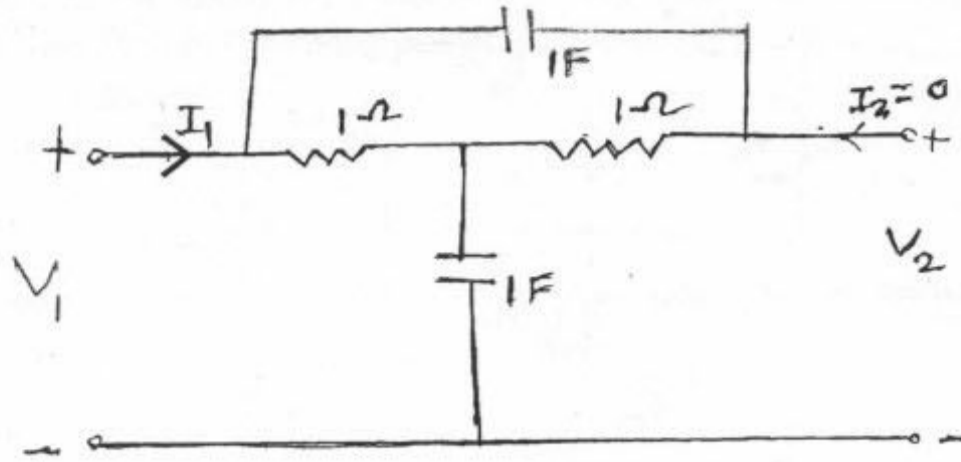

- (b) Determine A, B, C and D parameter using interconnection :-

10

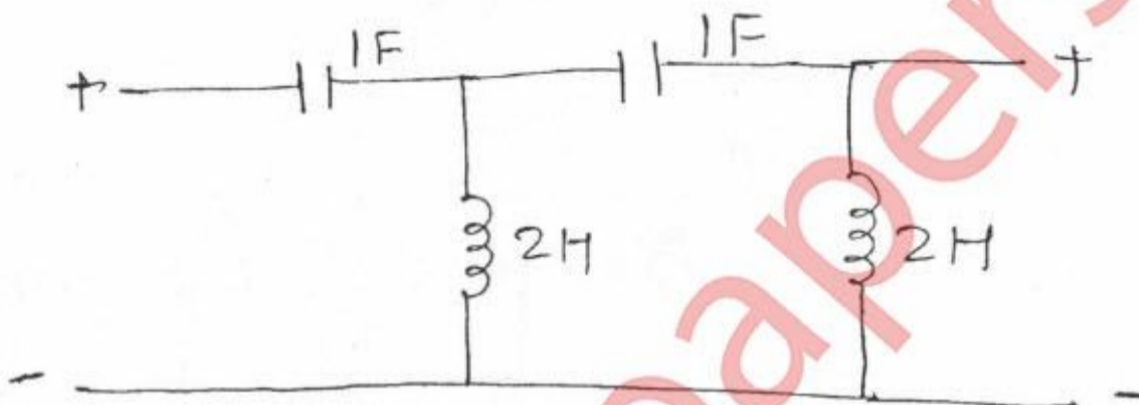

6. (a) Check whether the function is positive real :-

10

$$F(s) = \frac{s^2 + 4}{s^3 + 3s^2 + 3s + 1}$$

- (b) Synthesize the following RL impedance function in Foster I and Foster-II forms :-

10

$$Z(s) = \frac{2(s+1)(s+3)}{(s+2)(s+6)}$$

-----