

(3 Hours)


[Total Marks : 80

- N.B. :** (1) Question No. 1 is Compulsory.
 (2) Attempt **any three** questions from remaining **five** questions.


1. Attempt any **four** :

- (a) Find
- V_x
- in the circuit shown using superposition theorem.

20

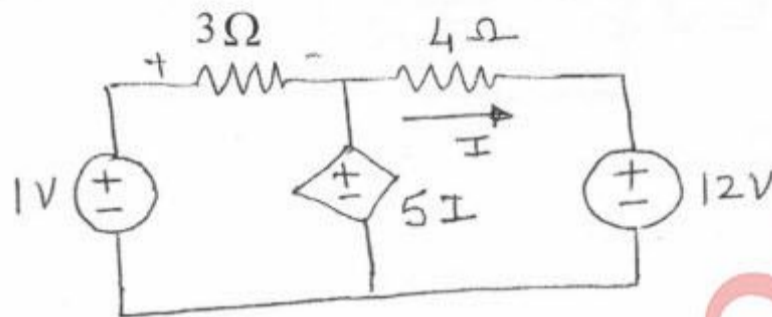


- (b) Obtain dual of given network

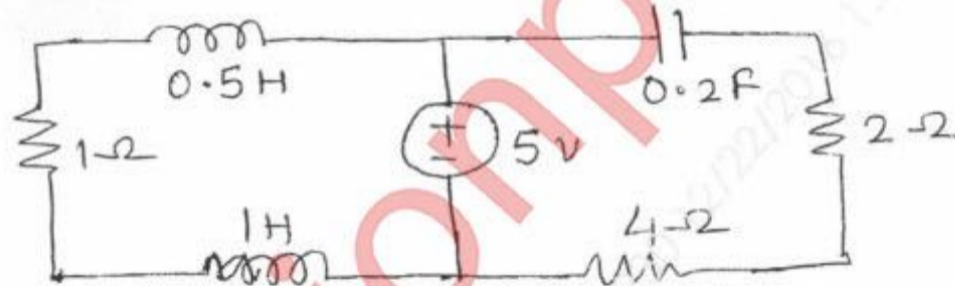

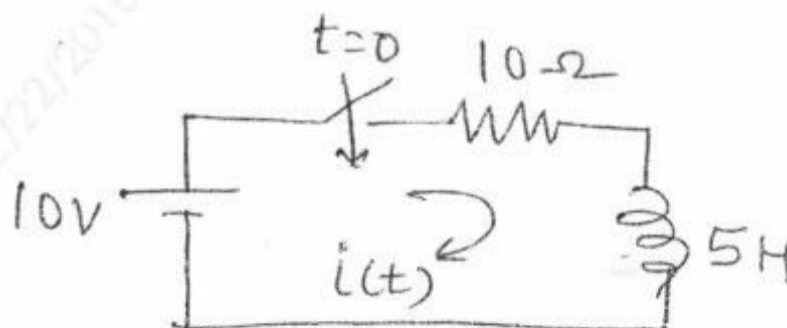- (c) Test whether Hurwitz or not
 $P(s) = s^5 + 12s^4 + 45s^3 + 60s^2 + 44s + 48$
- (d) In the given network, switch is closed at $t = 0$, with initial conditions = 0 ;
 find


$$i, \frac{di}{dt}, \frac{d^2i}{dt^2} \text{ at } t = 0^+$$



[TURN OVER]


2

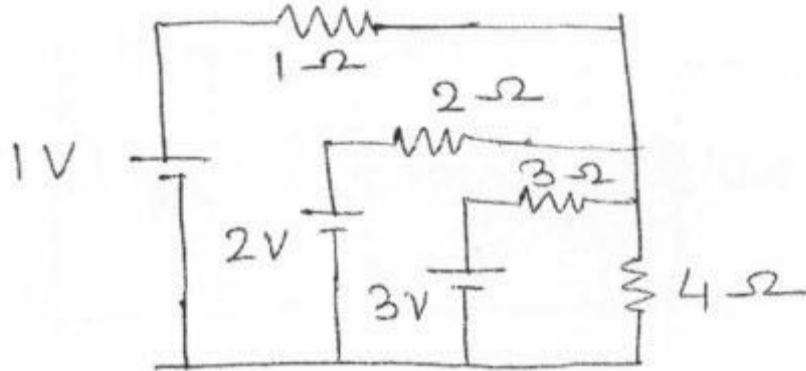(e) Find $I_{4\Omega}$ using Nodal Analysis.




2. (a) Find thevenin's equivalent network for the shown network.

10

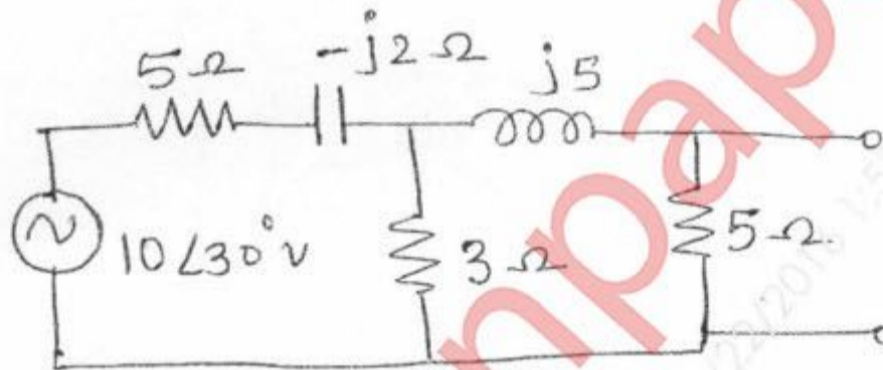

(b) Find Y - parameters for the given network.

10

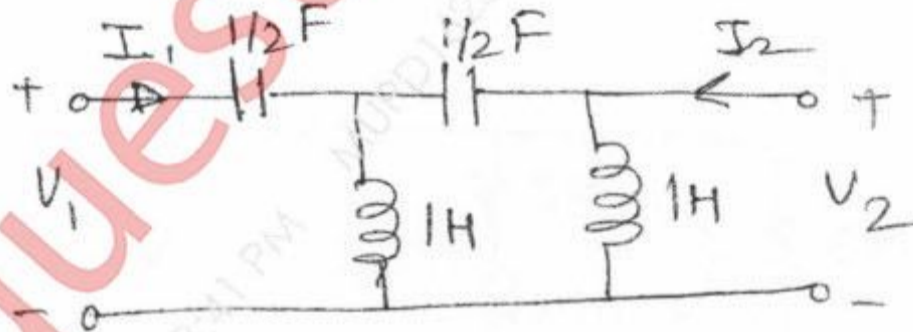


3. (a) For the network given below, switch is opened at $t = 0$ with initial conditions as shown. find the values of

10

$$V_1, V_2, \frac{dv_1}{dt}, \frac{dv_2}{dt} \text{ at time } t = 0^+$$


[TURN OVER]

3

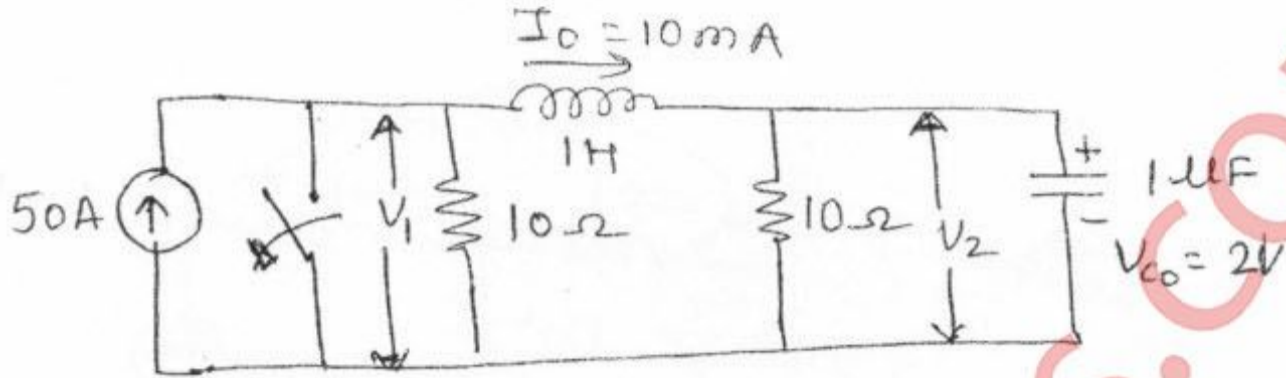


(b) Find V_x

10

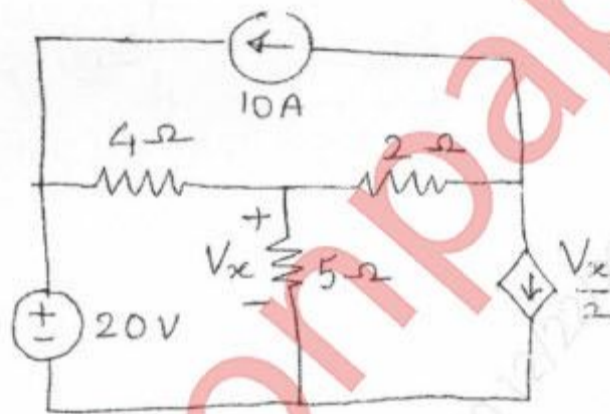

4. (a) In the network ; the switch is opened at $t = 0$; find $i(t)$.


10

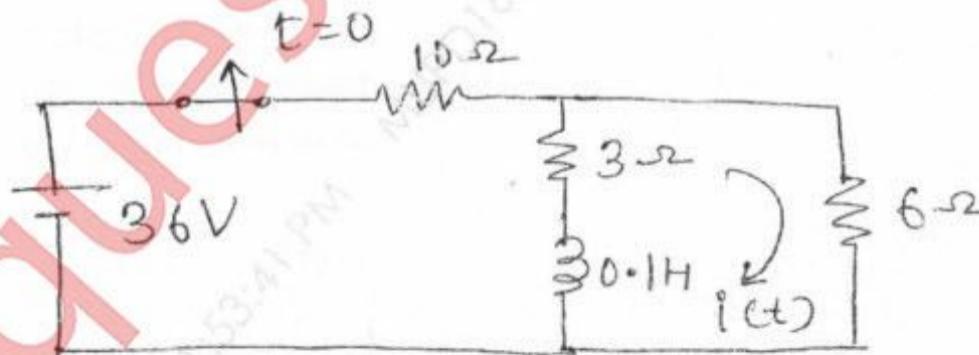


[TURN OVER]

4


(b) For the network det. I_1 and I_2

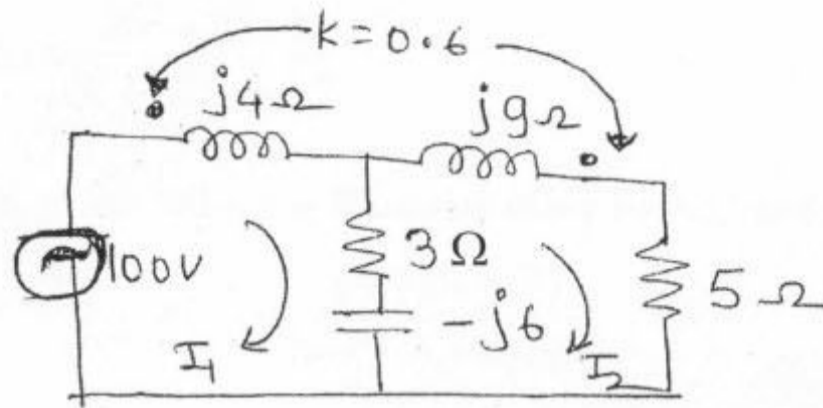

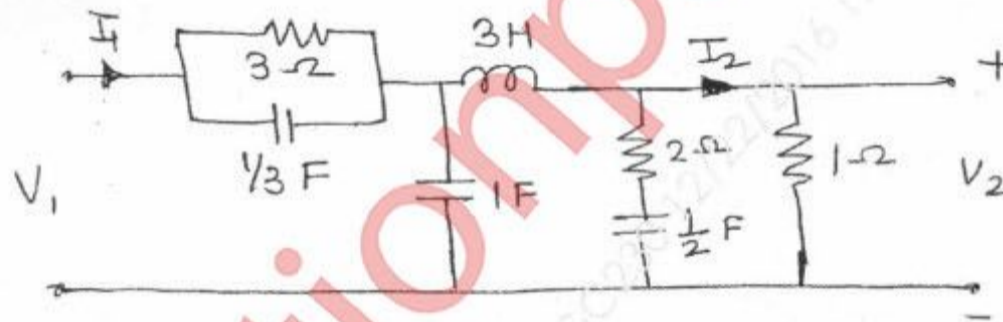5. (a) Determine, $\frac{V_2}{V_1}$, and $\frac{I_2}{I_1}$



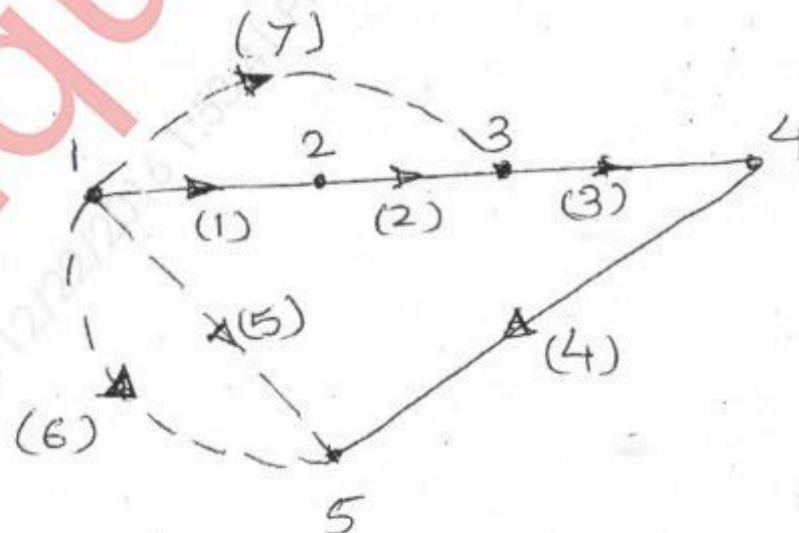(b) For the given tree find
 (i) Incidence matrix and
 (ii) Cutset Matrix



[TURN OVER]

6. (a) Check for positive realness

$$F(S) = \frac{2S^2 + 2S + 1}{S^3 + 2S^2 + s + 2}$$

- (b) Realize the following functions using Foster I and Foster -II forms

$$z(s) = \frac{(s+1)(s+3)}{S(s+2)(s+4)}$$

10

10

muquestionpapers.com