


Q. P. Code: 37653

[Time: Three Hours]


[Marks:80]

- N.B:
1. Question.No.1 is compulsory.
 2. Attempt any three questions from remaining five questions.
 3. Assume suitable data wherever necessary.

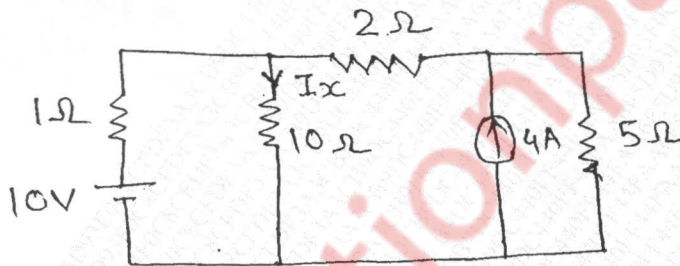- 1 Attempt any following . 20
- a What is series resonance? Explain
 - b Explain Digital Voltmeter (DVM).
 - c What are the advantages of an A.C. Bridge?
 - d What is Q-meter? Explain in brief.
- 2 a Find the current I_x using Superposition 10



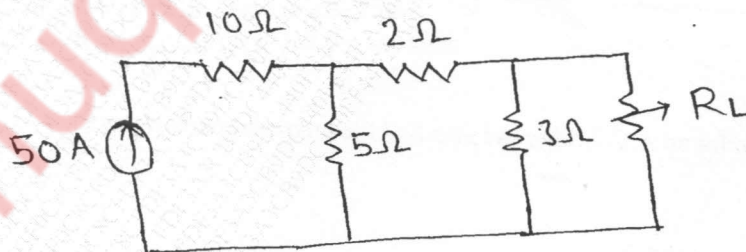
- b Find the open-circuit impedance parameters with equivalent circuit diagram and also derive the condition for Reciprocity and Symmetry. 10
- 3 a What will be the value of R_L to get maximum power delivered to it? 10




TURN OVER

Q. P. Code: 37653

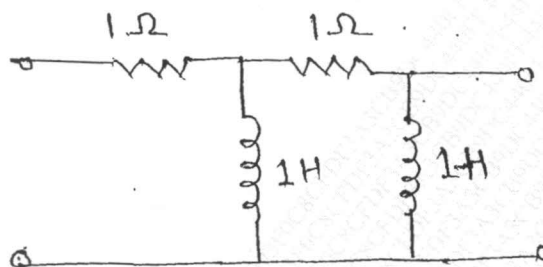- b Explain the transient condition for a series R-L circuit for D.C. conditions. 10
- 4 a Determine the Z parameters for the network shown. 10



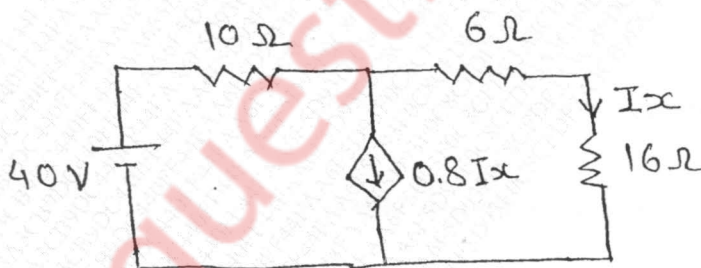- b Test whether $F(s) = \frac{s^3 + 6s^2 + 7s + 3}{s^2 + 2s + 1}$ is positive real function. 10
 - 5 a Realize Foster forms of the following LC impedance function. 10
- $$Z(s) = \frac{(s^2 + 1)(s^3 + 3)}{s(s^2 + 2)(s^2 + 4)}$$
- b Explain the working of PMMC instruments. 10
 - 6 a Find the current through the 16 Ω resistor. 10



- b Derive the balancing condition for an A.C. bridge and also find the unknown parameters for Hay's Bridge. 10
