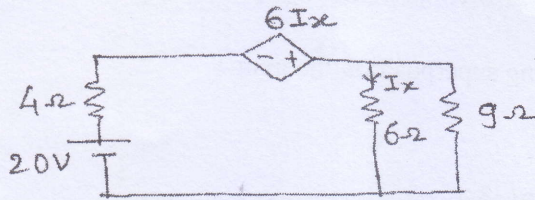


- N.B:
1. Question.No.1 is compulsory.
 2. Attempt any three questions from remaining five questions.
 3. Assume suitable data wherever necessary.


1. Attempt the following.

(20)


a) Find current in 9Ω resistor of the network.



b) Find Z parameters

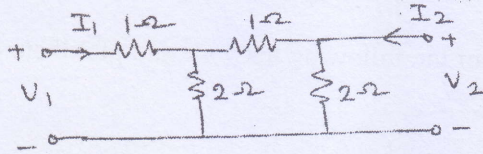

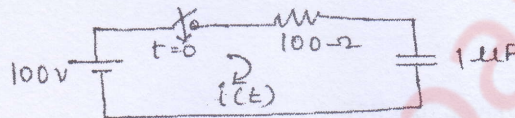c) Find I and $\frac{di}{dt}$ at $t = 0^+$ with capacitor uncharged and switch is closed at $t = 0$




d) Write the properties of positive real function.

e) Write the working principle of D'Arsonval galvanometer.

2. a) Use superposition theorem to find V_x


(10)

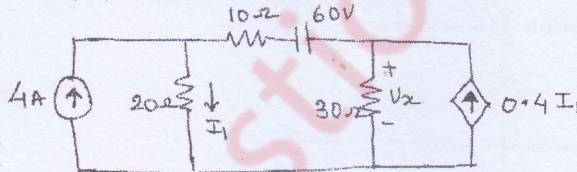

b) Explain the method to measure very high resistance.

(10)

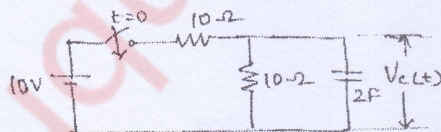3. a) Switch is closed at $t = 0$. Find $V_c(t)$



b) Explain an a.c. bridge used for measurement of capacitance.

(10)


e.p. code

68663

Page 1 of 2


S.E. (sem-III) (Choice Base) (Instn.) (30/08/2019)

4. a) Determine ABCD parameters. (10)

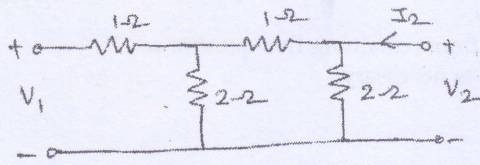


- b) Explain construction and working of PMMC instrument. (10)

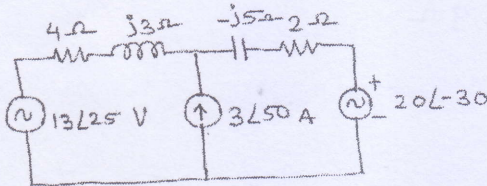5. a) Find current flowing through 4Ω using superposition theorem. (10)



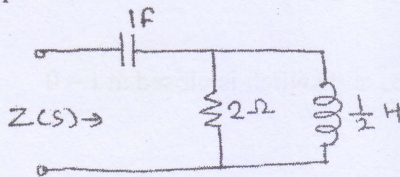- b) Find poles and zeros of the impedance of the following network and plot them on S-plane (10)



6. a) Realize foster forms of the impedance function (10)

$$Z(s) = \frac{2(s+2)(s+4)}{(s+1)(s+3)}$$

- b) Test whether the polynomial is Hurwitz $p(s) = s^5 + s^3 + s$ (5)

- c) Test positive realness of the function $F(s) = \frac{s^3 + 6s^2 + 7s + 3}{s^2 + 2s + 1}$ (5)

Q. P. Code.

68663