

Duration: 03 Hours.

Total marks: 80

Instructions to the candidates if any:-

- N. B. (1) Question No. 1 is compulsory.
(2) Answer any Three out of remaining questions.
(3) Assumptions made should be clearly stated.



| Q. No. | Marks |
|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-------|
| Q. 1 Solve any Four | 20 |
| a) What is Back emf? Explain significance of back emf? | |
| b) Explain power flow diagram for an Induction Motor | |
| c) Differentiate between D C Motor and Single phase induction motor. | |
| d) What are the sources of error in case of wheatstone bridge? | |
| e) What is power factor? Explain basic Voltmeter and Ammeter | |
| Q. 2) a) A 400 volts shunt motor develops an output of 18.5 kw when taking 22.5 kw Field resistance is 200 Ω and armature resistance is 0.4 Ω . What is the efficiency and power input when output is 9 kw. | 10 |
| b) Explain speed control methods of DC motor | 10 |
| Q. 3) a) Explain losses those takes place in Induction motor | 10 |
| b) Explain torque slip characteristics of 3 phase induction motor | 10 |
| Q.4) a) What is Q factor? Explain its measurement in detail | 10 |
| b) Explain the construction and working of PMMC instrument? | 10 |
| Q. 5) a) Explain the operation of shunt and series type ohm meters | 10 |
| b) Explain Capacitance Comparison Bridge and derive its bridge balance equation | 10 |
| Q.6) a) Explain difficulties in measurement of high resistance? Explain use of guard circuits | 10 |
| b) Draw and explain block diagram of DMM | 10 |