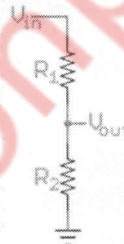


Time: 3 Hours

Total Marks: 80

- N. B.1) Question No. 1 is compulsory (Any Four).  
2) Answer any 3 questions from the remaining 5 questions.  
3) Assume suitable data wherever necessary.

- Q1 (a) Write a short note on zero crossing detector. 20  
(b) Describe the term loading effect with suitable example.  
(c) The resistors in a bridge are given by  $R_1=R_2=R_3=120\ \Omega$  and  $R_4 = 121\ \Omega$ . If the supply voltage is 10V. Find the offset voltage.  
(d) Draw and explain Sample and Hold circuit.  
(e) Design a  $\pm 12V$  power supply using IC 78xx.
- Q2 (a) Define multivibrator? Explain astable multivibrator using IC 555 and also design astable multivibrator for 50% duty cycle. 20  
(b) Draw and explain circuit for ideal integrator with waveforms. Discuss the problems associated with ideal integrator and draw the circuit diagram for practical integrator.
- Q3 (a) A thermistor is to monitor room temperature. It has a resistance of  $3.5\ K\Omega$  at  $20^\circ C$  with a slope of  $-10\%/^\circ C$ . The dissipation constant is  $P_D=5mW/^\circ C$ . It is proposed to use the thermistor in the divider as shown below to provide a voltage of 5.0V at  $20^\circ C$ . Evaluate the effect of self-heating. ( $R_2=$  Thermistor;  $R_1=3.5K\Omega$ ) 20



- (b) Draw and explain the principle and construction of metal strain gauges. What is the signal conditioning associated with it.
- Q4 (a) Explain successive approximation analog to digital converter. Find ADC output for a 4-bit converter to a 2.87V input, if the reference is 5V. 20  
(b) Design a second order high pass filter for cutoff frequency equal to 1.5 KHz.
- Q5 (a) A potentiometric displacement sensor is to be used to measure work-piece motion from 0 to 10 cm. The resistance changes linearly over this range from 0 to  $1K\Omega$ . Develop signal conditioning to provide a linear, 0- to 10-V output. 20  
(b) Explain the absolute value circuit with labelled circuit diagram and its waveform.
- Q6 (a) Draw and explain the principle and construction of RTD. What is the signal conditioning associated with it. 10  
(b) Phase Locked loop 5  
(c) SMPS 5

\*\*\*\*\*