

Total Marks : 80


( 3 Hours)

- Note: (1) Q1 is compulsory  
 (2) Attempt any three from the remaining  
 (3) Assume suitable data wherever necessary

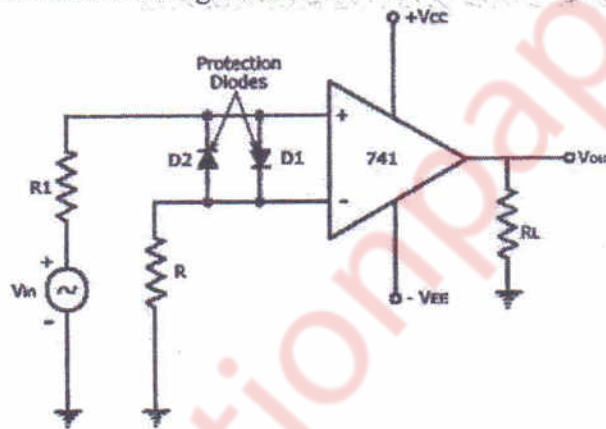Q1 Answer any four from the following

20

- An amplifier outputs a voltage that is 10 times the voltage on its input terminals. It has an input resistance of  $10k\Omega$ . A sensor outputs a voltage proportional to temperature with a transfer function of  $20mV/^\circ C$ . The sensor has an output resistance of  $5k\Omega$ . If the temperature is  $50^\circ C$ , find the amplifier output considering the effect of loading.
- Draw the absolute value circuit using Op Amp and sketch its input output waveform
- Explain the block diagram of a SMPS.
- Discuss the different types of filters with their input output characteristics.
- Sketch the output of the following circuit:



What could be the function of the circuit?

Q2.

- Derive the expression for output voltage for an Instrumentation amplifier with a transducer bridge. Also list the applications of the same. 10
- A Solid-state pressure sensor that outputs  $25mV/kPa$  for a pressure variation of  $0.0$  to  $25kPa$  will be used to measure the level of a liquid with a density of  $1.3 \times 10^3 Kg/m^3$ . What voltage output will be expected for level variations from  $0$  to  $2.0m$ ? What is the sensitivity for level measurement expressed in  $mV/cm$ ? 10

Q3.

- a. Describe typical R-2R ladder type Digital to Analog converter for 4 bits data. 10  
Determine its step size when  $R_f=20k\Omega$ . Also calculate the output voltage if  $b_0=b_1=b_2=0$  and  $b_3=5V$ .
- b. Explain how Op-Amp can be used as a voltage to current convertor with (a) floating 10  
load and (b) grounded load

Q4.

- a. What is a RTD? Explain its construction and the signal conditioning circuitry 10  
associated with it.
- b. Explain monostable multivibrator using IC 555 with neat input output waveforms. 10  
Also design a monostable multivibrator to have an output pulse width of 100ms.

Q5.

- a. Design a general signal conditioning circuit to convert sensor output i.e. LDR output 10  
to 0 volt (Dark) to 5 volt (Light) for resistance range  $90K\Omega$  to  $5.1K\Omega$  respectively.
- b. What is a voltage regulator? What are its types? Design an adjustable voltage 10  
regulator using IC 7805 to obtain an output of 12V.

Q6.

- a. List the different types of analog to digital convertors. Explain one of them with a 10  
neat diagram.
- b. What is operating principle of photovoltaic cell. Give its equivalent circuit and 10  
hence discuss the signal conditioning circuit associated with it.